

Q<sub>1</sub>: Let bus voltage  $V_b(t) = V_m \sin(\omega_b t)$   
 generator voltage  $V_g(t) = V_m \sin(\omega_g t + \phi)$   
 $\phi$  : Initial phase difference.

for phase A;

$$V_{\text{lamp}}(t) = V_g(t) - V_b(t) \\ = V_m \sin(\omega_g t + \phi) - V_m \sin(\omega_b t)$$

$$\text{using } \sin A - \sin B = 2 \cos\left(\frac{A+B}{2}\right) \sin\left(\frac{A-B}{2}\right)$$


$$V_{\text{lamp}}(t) = 2 V_m \cos\left(\frac{\omega_g t + \omega_b t + \phi}{2}\right) \sin\left(\frac{\omega_g t + \phi - \omega_b t}{2}\right)$$

So, the lamp voltage oscillates at the beat frequency.

$$f_{\text{beat}} = |f_g - f_b|$$

And the brightness of the lamp varies periodically, cycling b/w bright and dark.

- All the three lamps blink simultaneously.
- The blinking rate = twice the slip frequency  $2 \times |f_g - f_b|$ .
- Maximum brightness is when phase difference is  $180^\circ$ .
- Darkness when the phase difference is  $0^\circ$ .
- Phase sequence is correct all 3 lamps blink together.

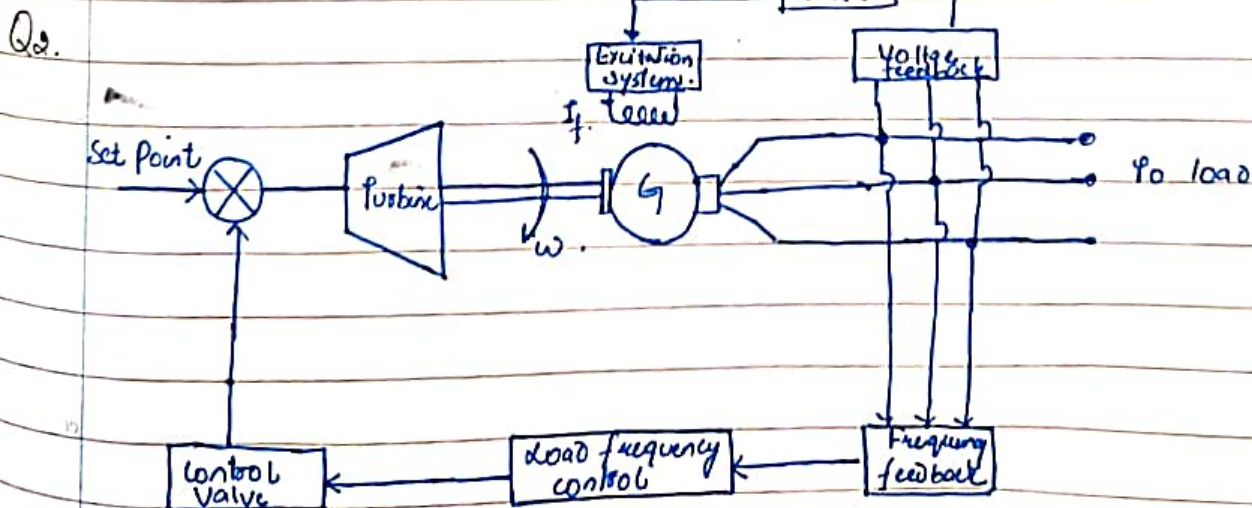

Excitation System :-


- Controls the field current  $I_f$  of the generator
- Affects the terminal voltage of the generator

AVR :-

- Uses voltage feedback to regulate the terminal voltage
- Adjusts the excitation system accordingly
- Load frequency control
- Uses feedback frequency feedback to maintain system frequency
- Adjusts the control valve to modify the input to the turbine
- Ensure active power balance and stabilizes frequency

Voltage feedback  $\rightarrow$  AVR  $\rightarrow$  Excitation  $\rightarrow$  Controls terminal voltage

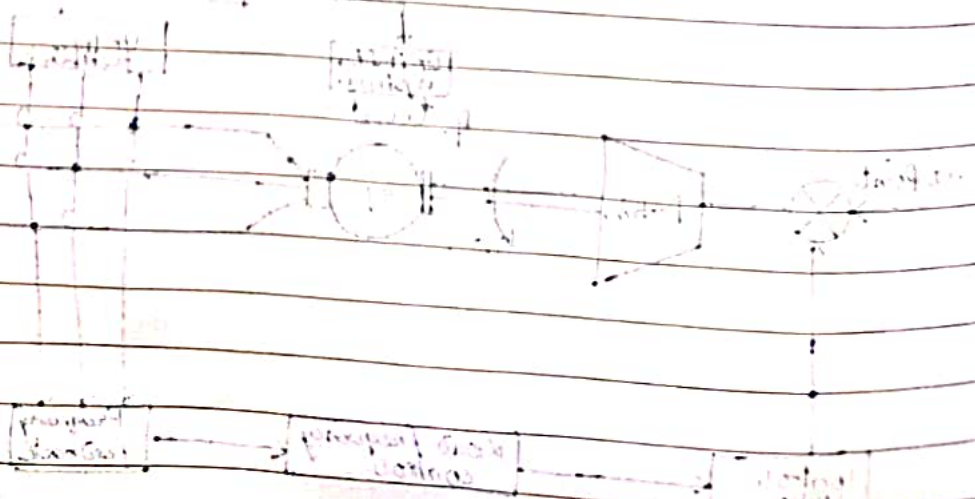Frequency feedback  $\rightarrow$  LFC  $\rightarrow$  Turbine Control valve  $\rightarrow$  Controls Generator Speed





$$S_b = 10 \text{ MVA}$$

$$E_f = 11 \text{ kVA}$$

$$X_s = 1.2 \text{ pu}$$

$$X_L = 0.6 \text{ pu}$$

$$X_t = j1.8 \text{ pu}$$

$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{(11000)^2}{(10 \times 10^6)} = 12.1 \Omega$$

(a) Star Connected  $R = 24 \Omega$

$$Z_{load}(\text{pu}) = \frac{24}{12.1} = 1.9835 \text{ pu}$$

Let Generator Voltage be  $E_f = 1 \angle 0^\circ \text{ pu}$

$$\begin{aligned} Z_{total} &= X_s + X_{line} + Z_{load} \\ &= j1.8 + 1.935 \text{ pu} \end{aligned}$$

$$\begin{aligned} |Z| &= \sqrt{1.935^2 + 1.8^2} \\ &= 2.688 \end{aligned}$$

$$\theta = \tan^{-1} \left( \frac{1.8}{1.935} \right) = 42.38^\circ$$

$$I = \frac{E}{Z} = \frac{1 \angle 0^\circ}{2.688 \angle 42.38^\circ}$$

$$I = 0.372 \angle -42.38^\circ \text{ pu}$$

Voltage across Load:

$$V_{load}^{pu} = I \times R = 0.372 \angle -42.38^\circ \times 1.9835$$

$$= 0.738 \angle -42.38^\circ \text{ pu}$$

$$V_{load, \text{Phase}} = 0.738 \times \frac{11000}{\sqrt{3}} = 4682 \text{ V}$$

⑥ C load  $X = 24 \Omega$

$$X_C = \frac{1}{j24}$$

$$X_C = -j1.985$$

$$\begin{aligned} Z_{\text{total}} &= -j1.9835 + j1.8 \\ &= -j0.1835 \end{aligned}$$

$$I = \frac{1 \angle 0^\circ}{-j0.1835} = j5.45 \text{ pu.}$$

$$\begin{aligned} V_{\text{load}} &= I \cdot Z_{\text{load}} \\ &= j5.45 (-j1.9835) \\ &= 5.45 \times 1.9835 \\ &= 10.81 \text{ pu} \end{aligned}$$

$$V_{\text{pu}} = \frac{V_{\text{act}}}{V_{\text{base}}}$$

$$\begin{aligned} V_{\text{act.}} &= V_{\text{pu}} \times V_{\text{base}} \\ &= 10.81 \times \frac{11 \text{ k}}{\sqrt{3}} \end{aligned}$$

$$\begin{aligned} V_{\text{Load Phase}} &= 68.643 \text{ V} \\ &= 68.643 \text{ kV} \end{aligned}$$