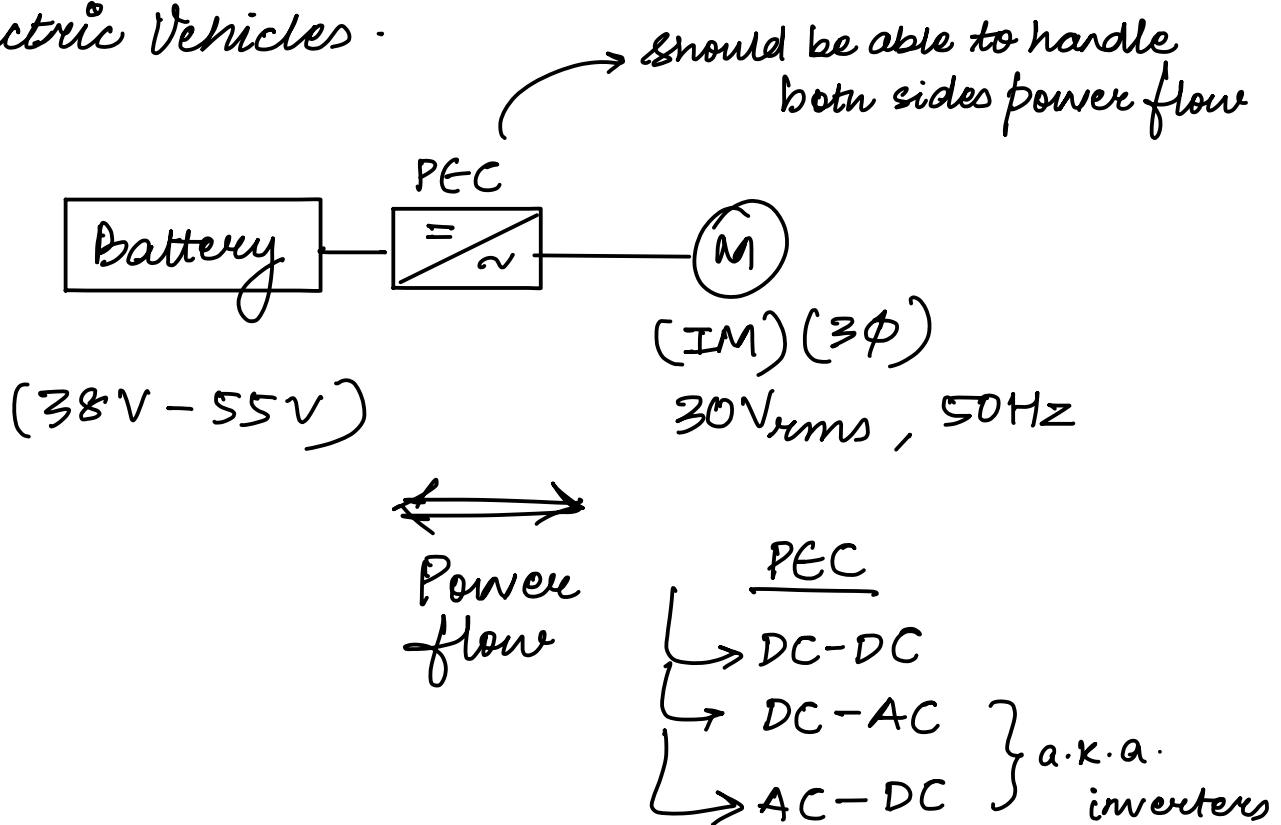



Power Electronics

PEC is usually static (no moving parts)


Eg Electric Vehicles -



Eg Solar Photovoltaic

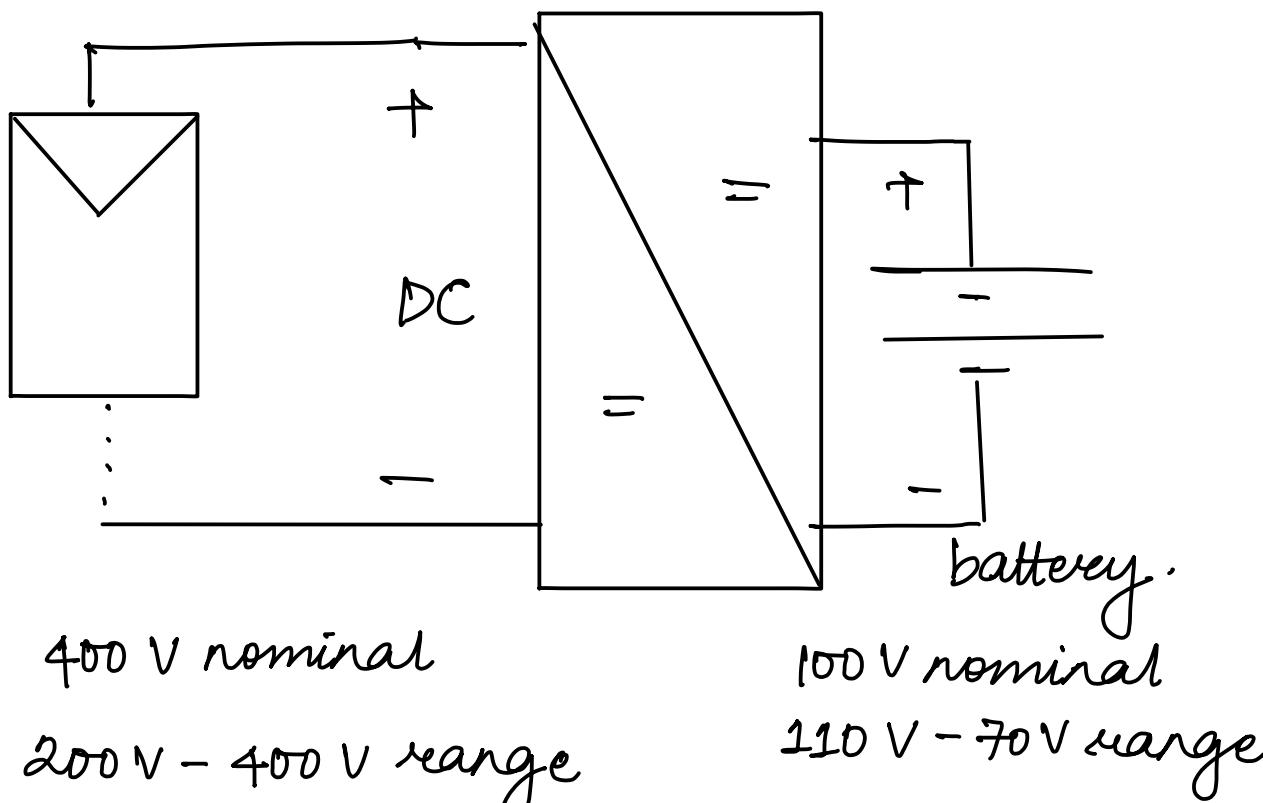


Cof Mobile Phones

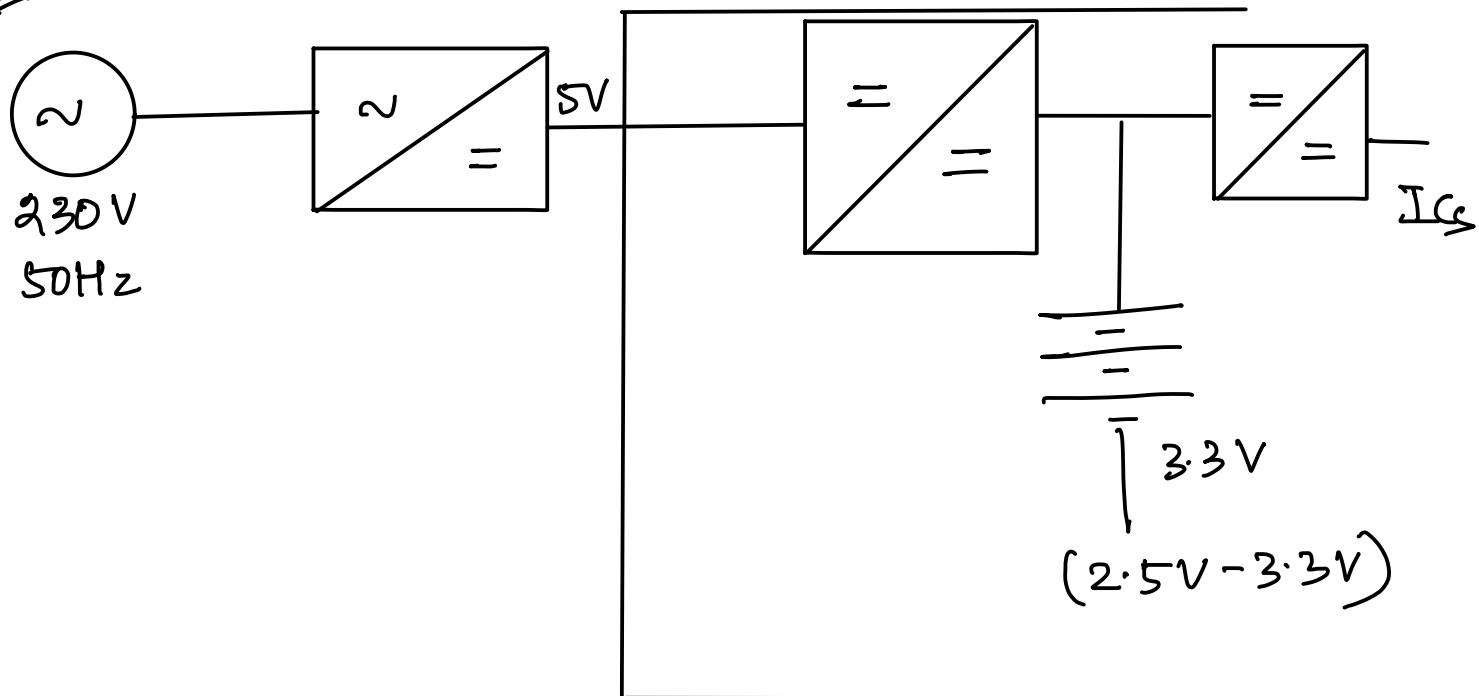

DC- DC Conversion

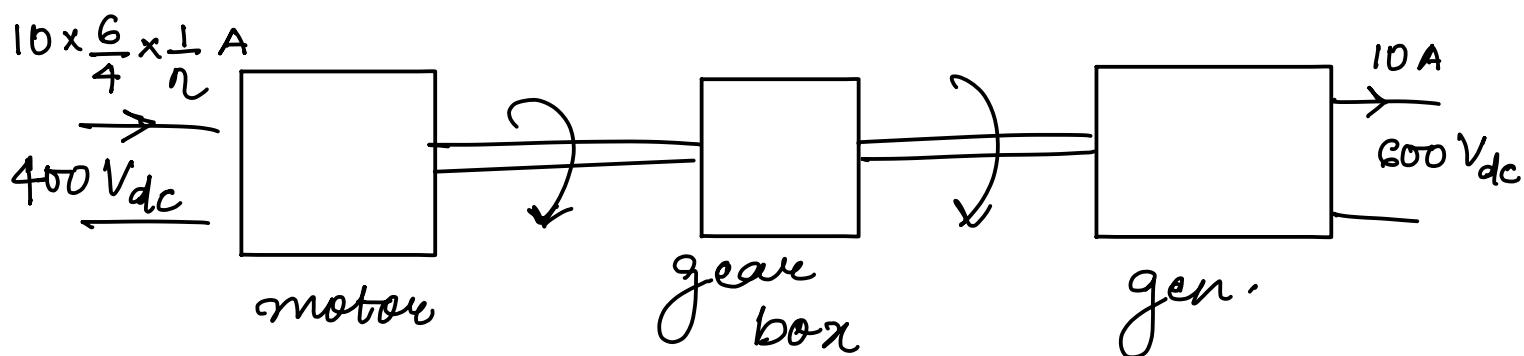
1) Using Motor-Generator Set
late 19th century and early 20th century.

$$400 \text{ V}_{\text{dc}} \rightarrow 600 \text{ V}_{\text{dc}}$$



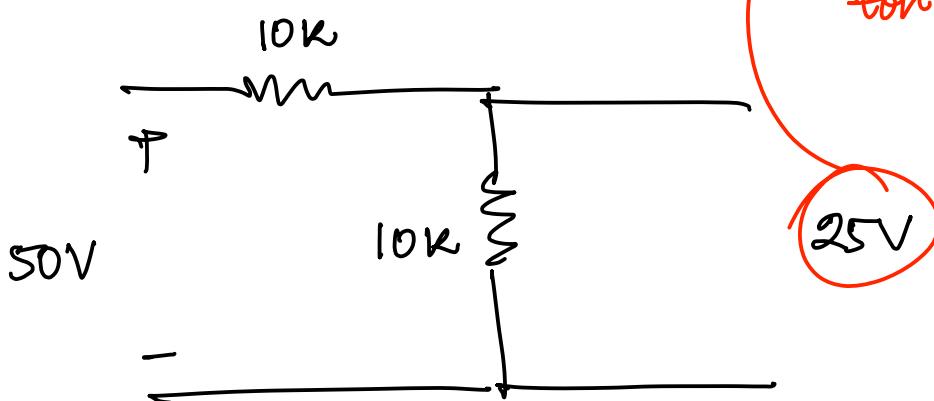2) Voltage Divider Circuit

$$50 \text{ V}_{\text{dc}} \rightarrow 25 \text{ V}_{\text{dc}}$$




This 25V is only at no load. Agar R_L raagya toh the V_{out} will change


Partly solves \downarrow with variable R_L .



Disadvantages

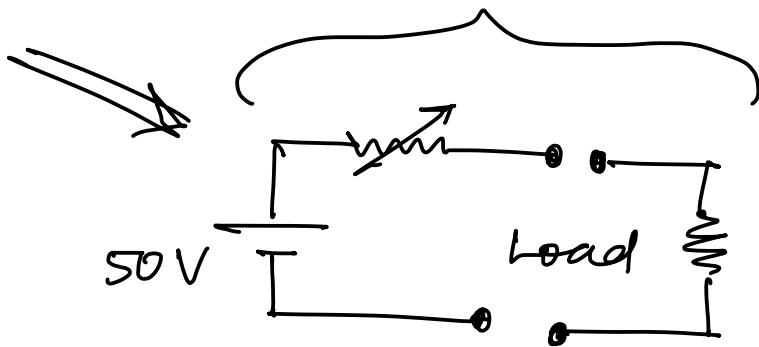- Poor η ($\frac{P_{\text{out}}}{P_{\text{in}}}$)
- Heat loss
- No step up
- Output voltage drastically depends on output load. Unacceptable voltage regulation.



3) Linear Regulators

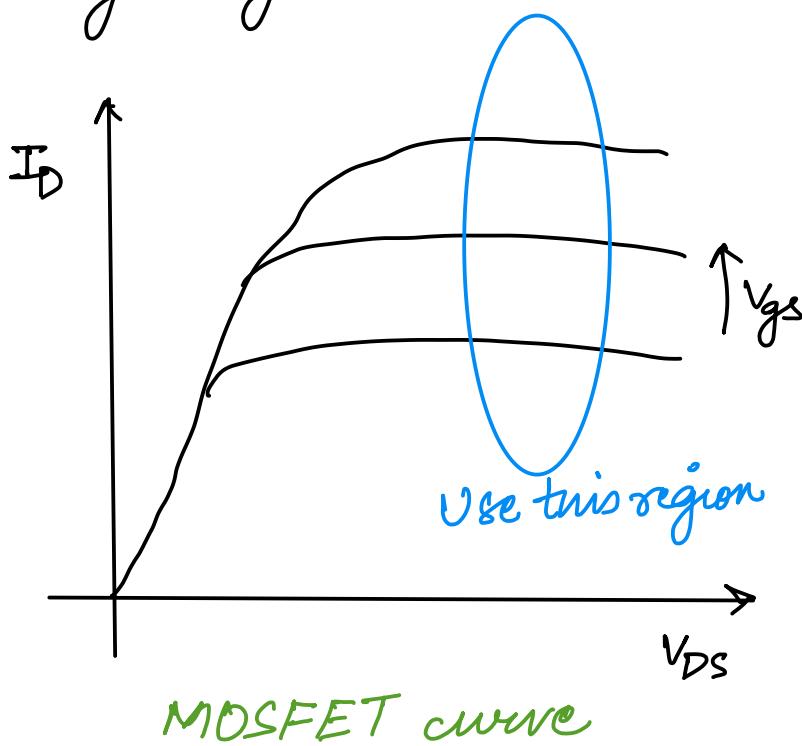

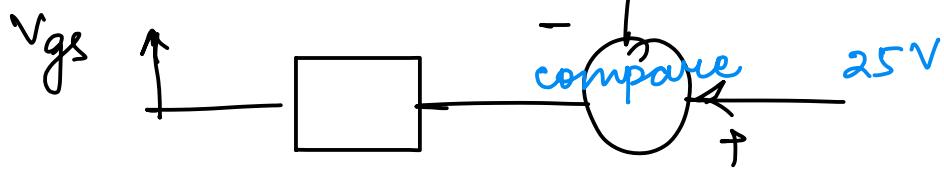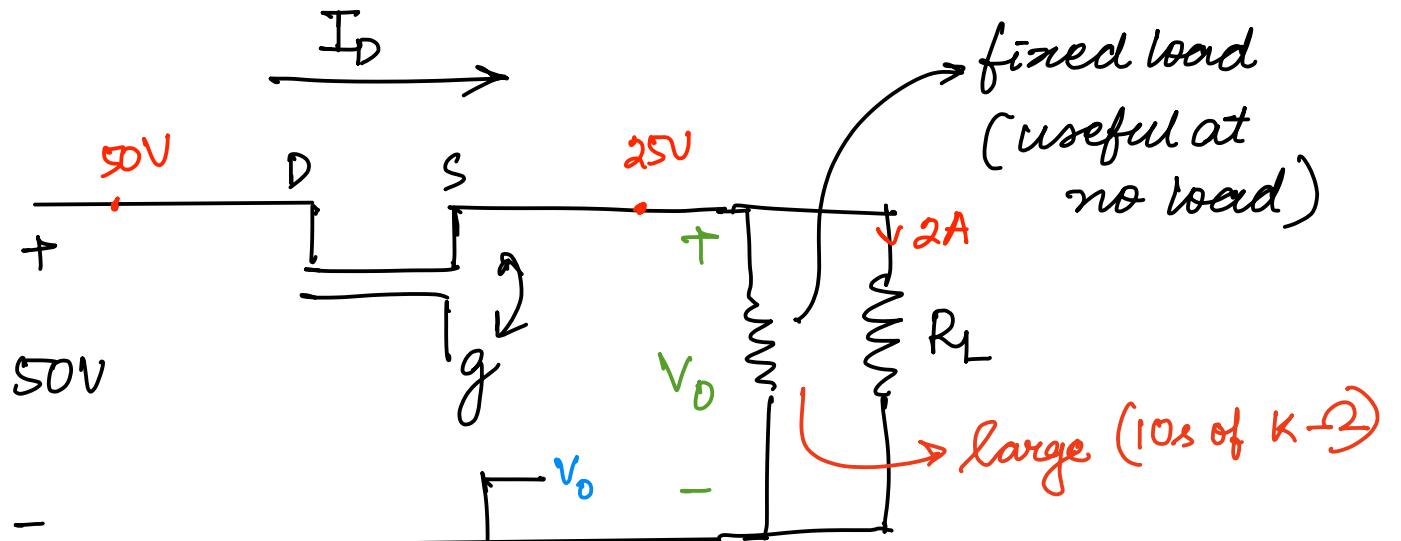

(operation, efficiency)

$$50V \rightarrow 25V$$

$$I_o = 2A$$





$$P_o = 50W$$

$$P_{loss} = (50 - 25) \times 2 \\ = 50W$$

Still have scope of improvement.

good load voltage regulation -

4) Switching Regulators

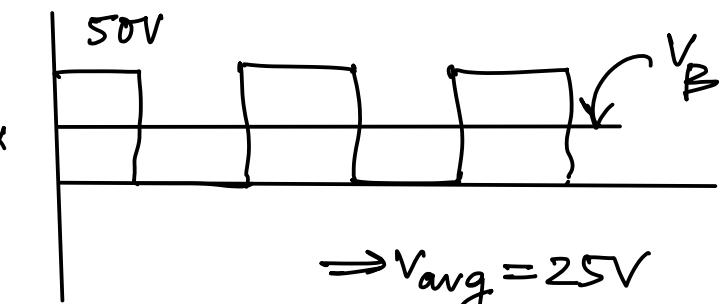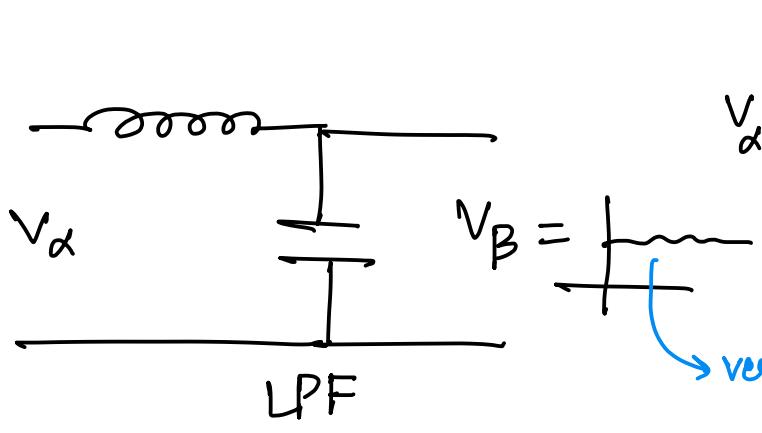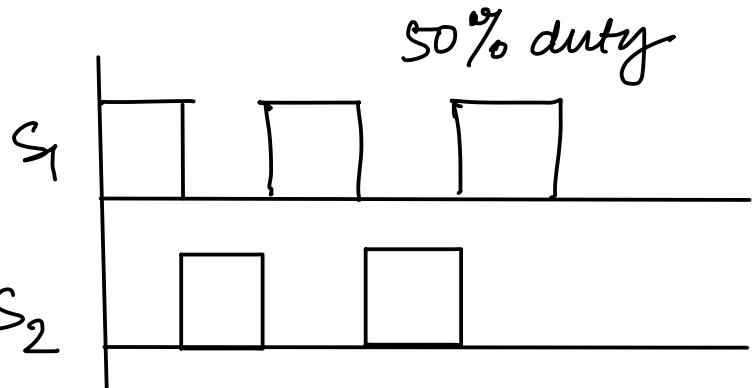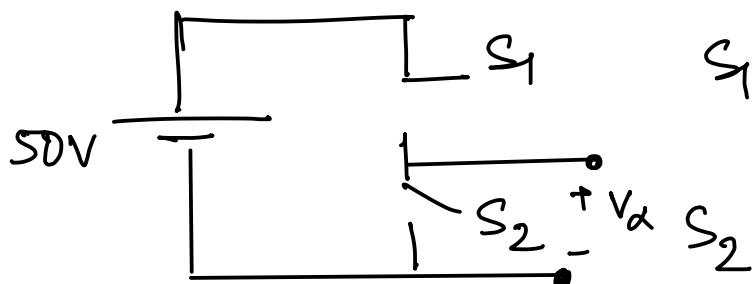

Step 1 → PWM

Step 2 → Low pass filter -
(To filter out high
frequency comp
and retain only
the avg)

no load \Rightarrow infinite resistance
heavy load \Rightarrow low resistance.

$S_1, S_2 \rightarrow$ can't be mechanical

\hookrightarrow could be MOSFET (different operating region)

When using MOSFET as Linear Regulator \rightarrow operate in saturation region.

When using as Semiconductor Switch \rightarrow operate in ohmic region and cut-off region.


Mercury Arc Valve

\rightarrow Grid (Mesh) with a -ve charge is placed for turning off


\rightarrow Can turn it on, cannot turn it off through grid voltage.

\hookrightarrow Semi Controlled Devices


Uncontrolled Rectifier

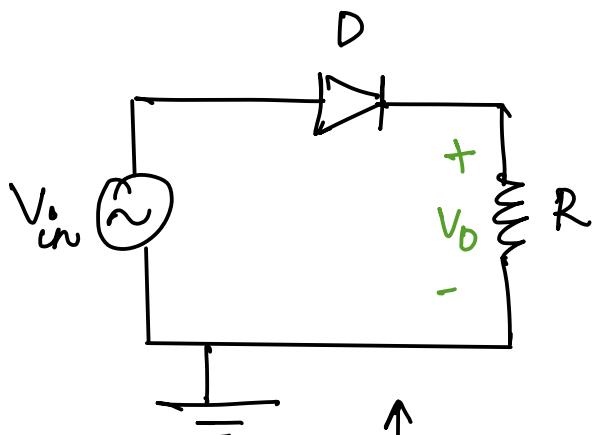

• Half Wave with R load .

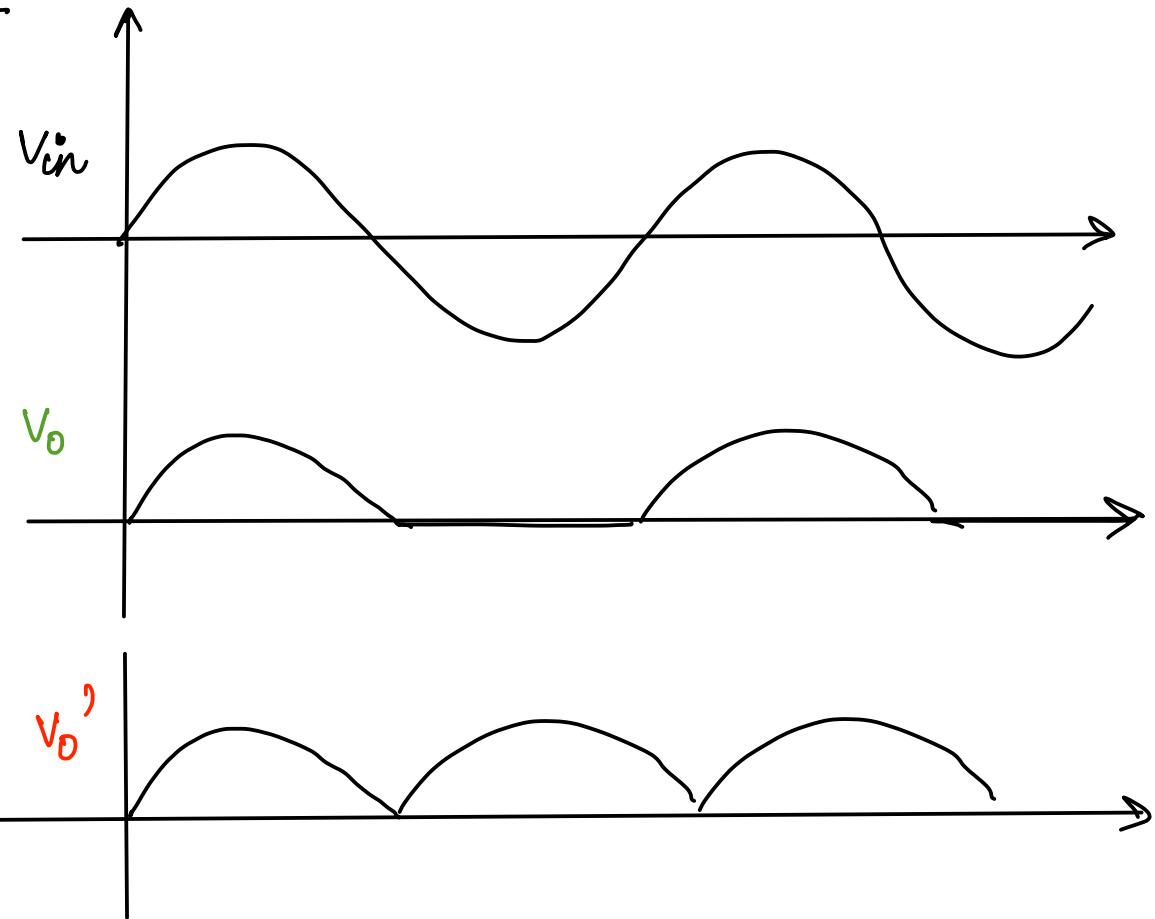

Full Bridge

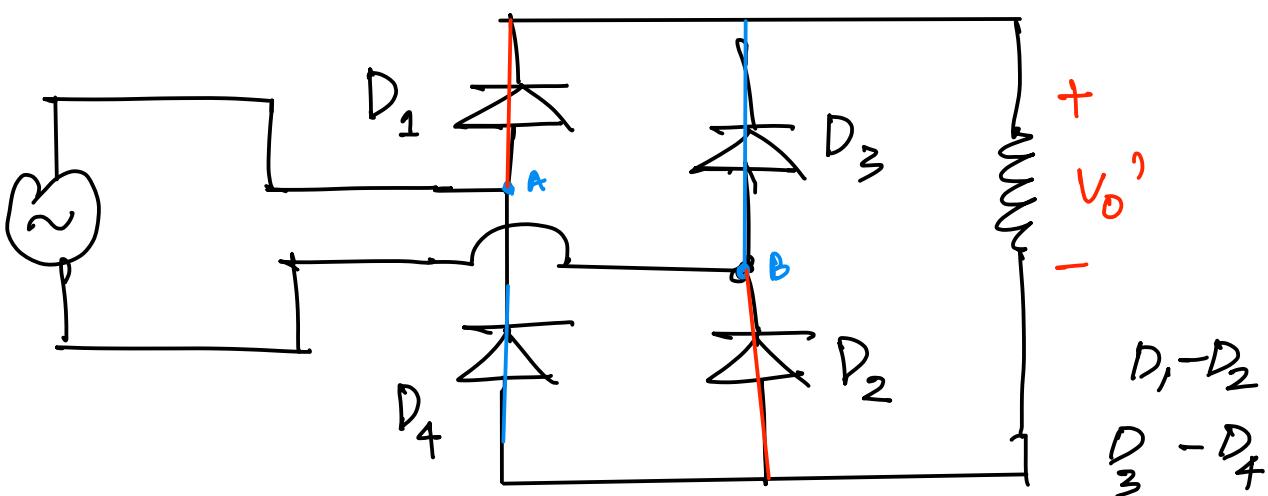

Negative half cycle :


$$V_{D_1} = V_A - V_B = V_{in} \quad V_{D_2} = V_A - V_B = V_{in}$$

$$V_{D_3} = 0 \quad V_{D_4} = 0$$


Positive half cycle

$$V_{D_3} = V_B - V_A = -V_{in} \quad V_{D_4} = V_B - V_A = -V_{in} \quad V_{D_1} = 0, V_{D_2} = 0$$


Common Cathode Configuration

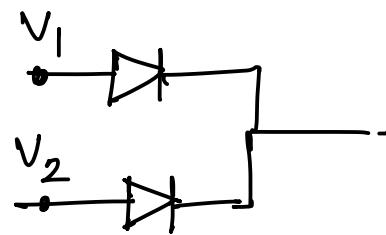

Common Anode Configuration

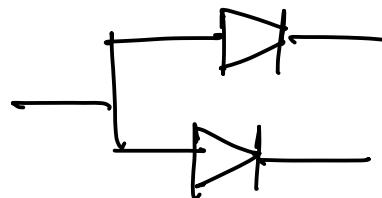


Half wave with R-L load


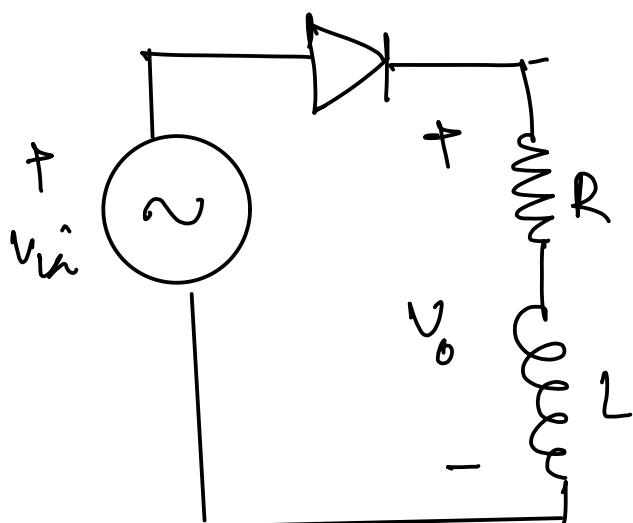


$$v_o = i_0 R + \frac{L di_0}{dt}$$

$$v_o - i_0 R = \frac{L di_0}{dt}$$

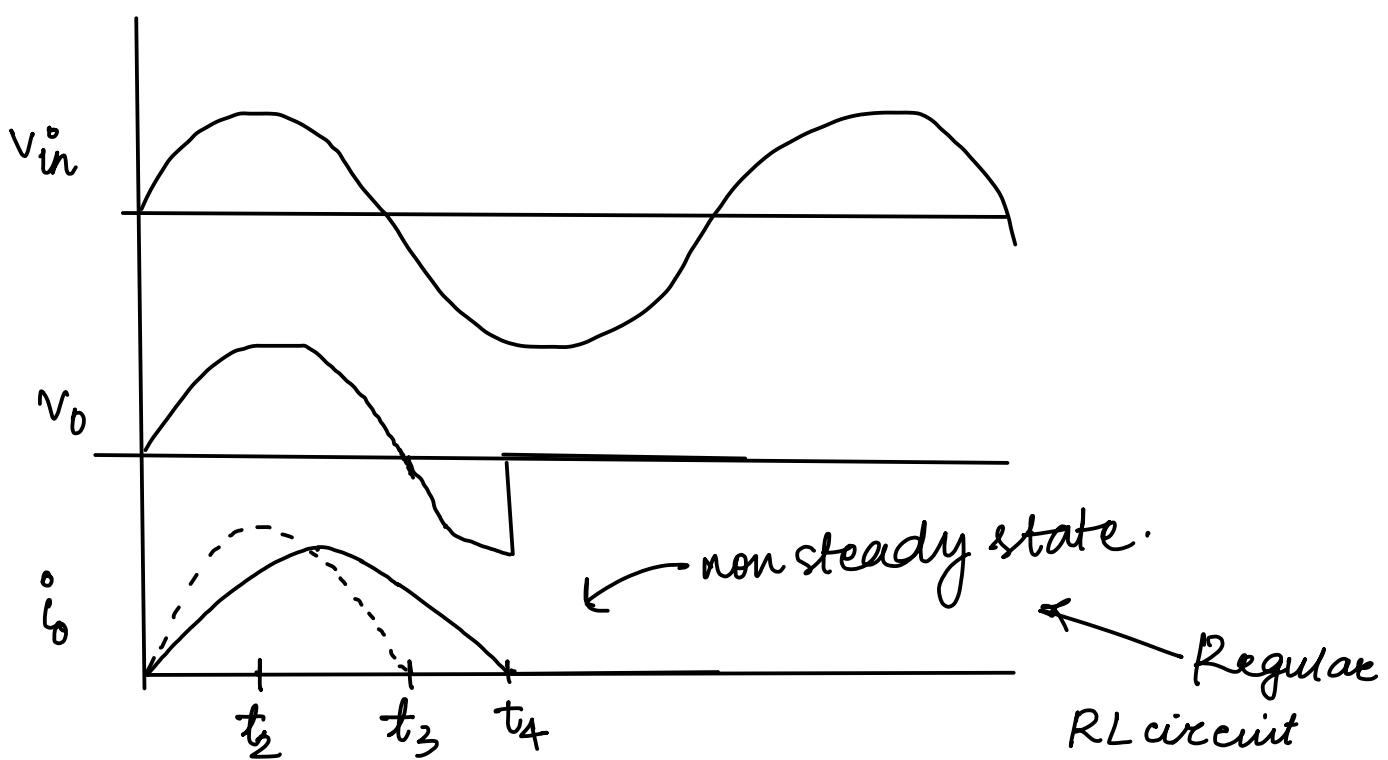



(lagging peak)

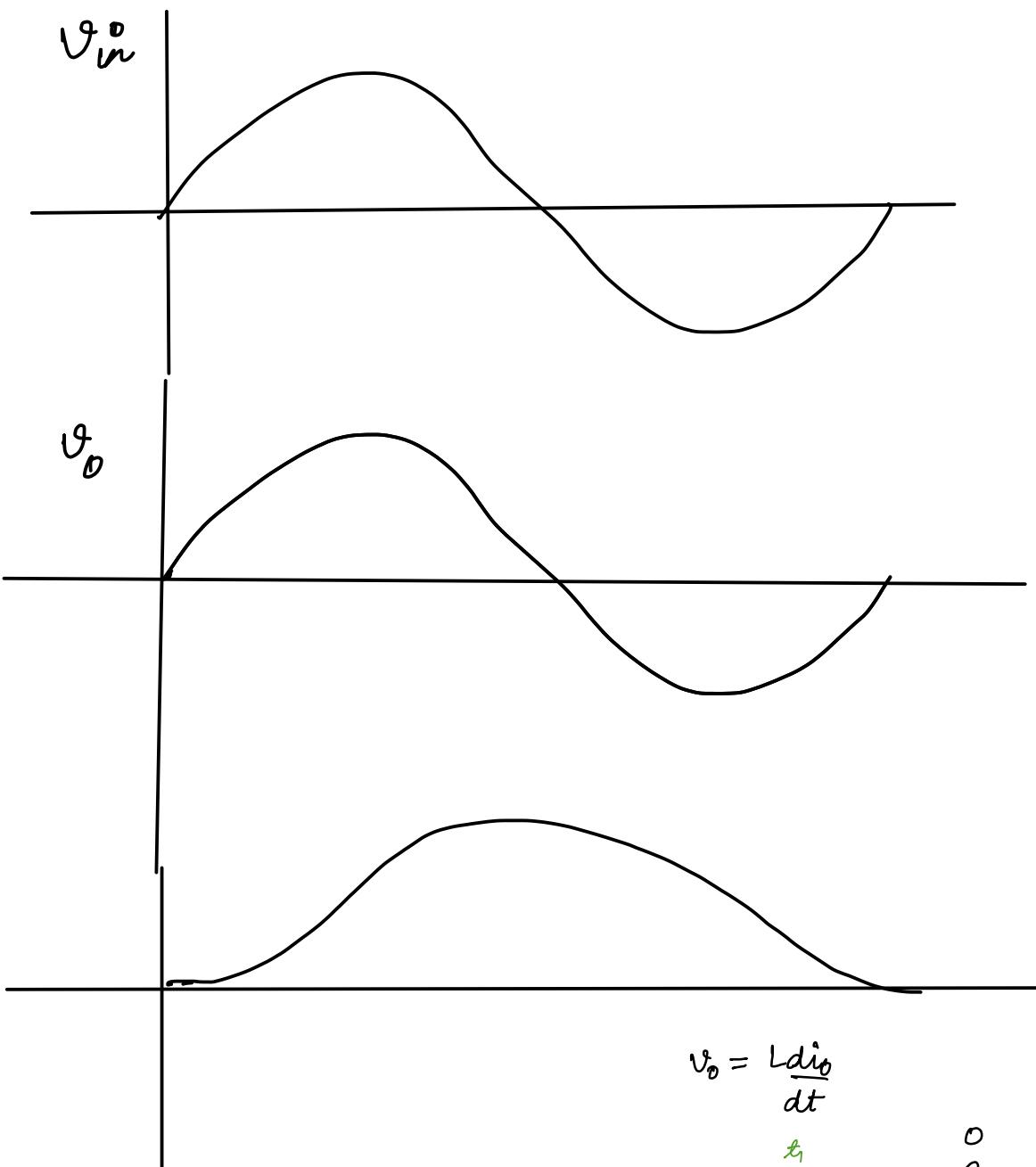
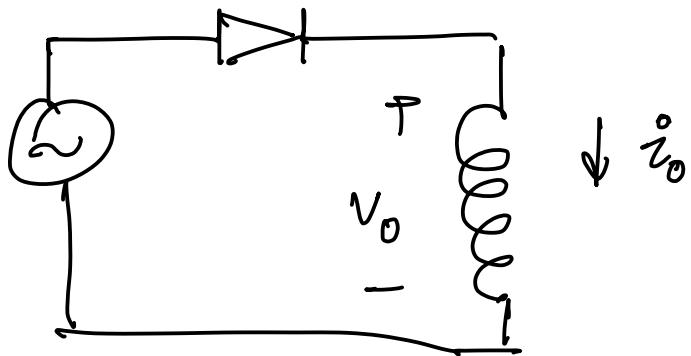


$$v_o = L \frac{d\dot{i}_o}{dt}$$



$$= \int_0^t v_o dt = L \int_0^t \dot{i}_o$$

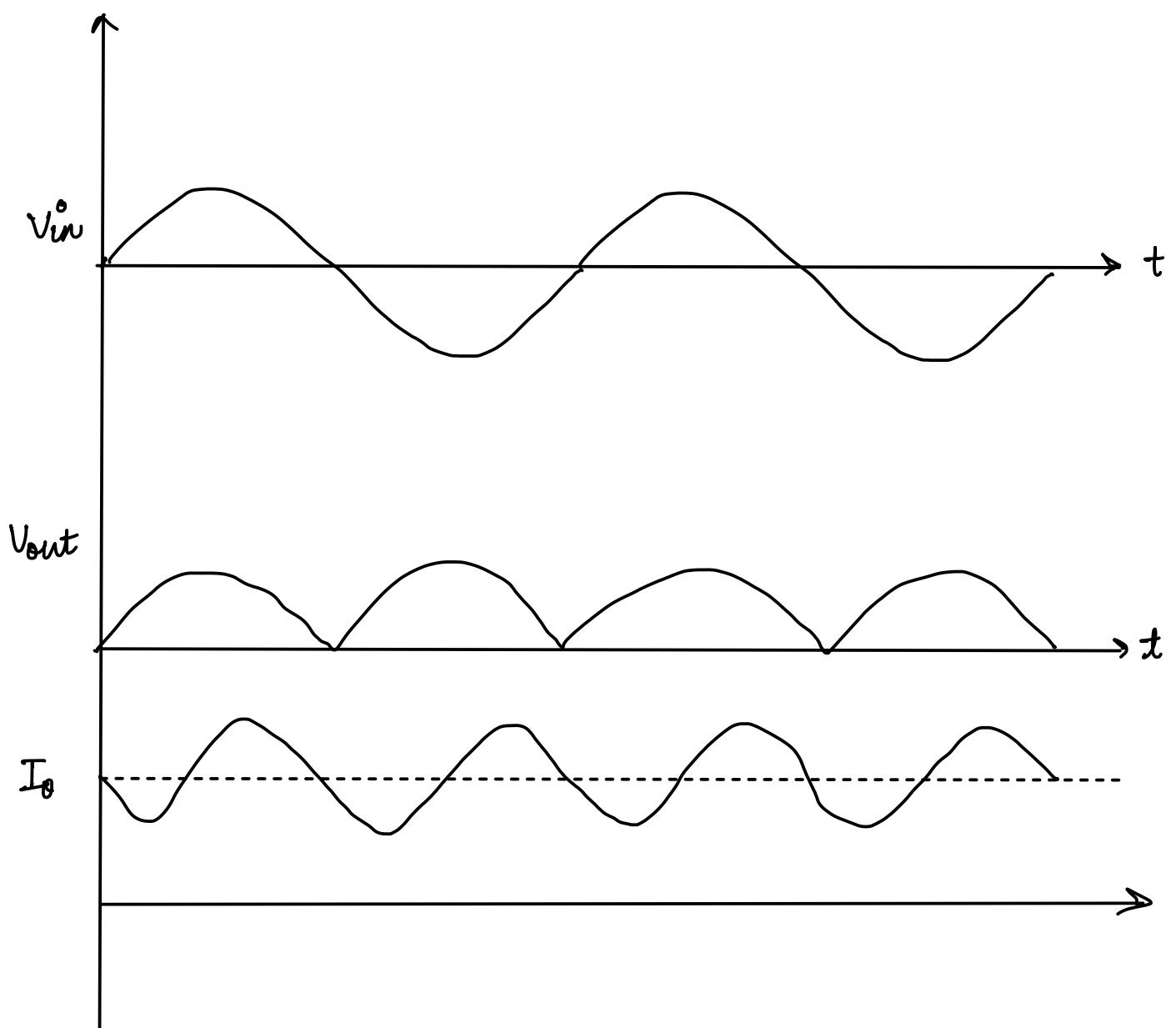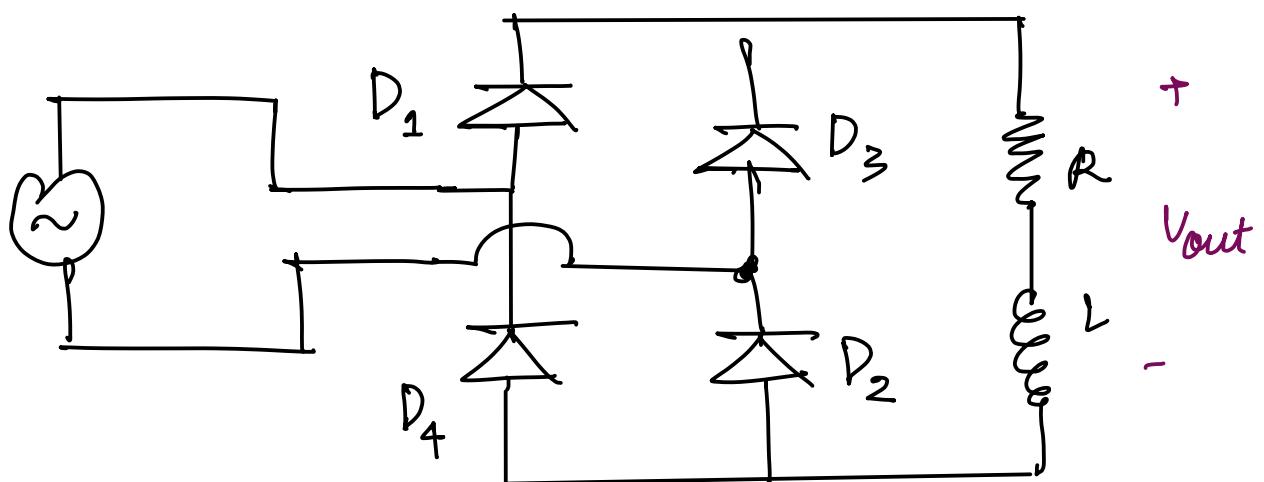Q Do both these for full bridge rectifier



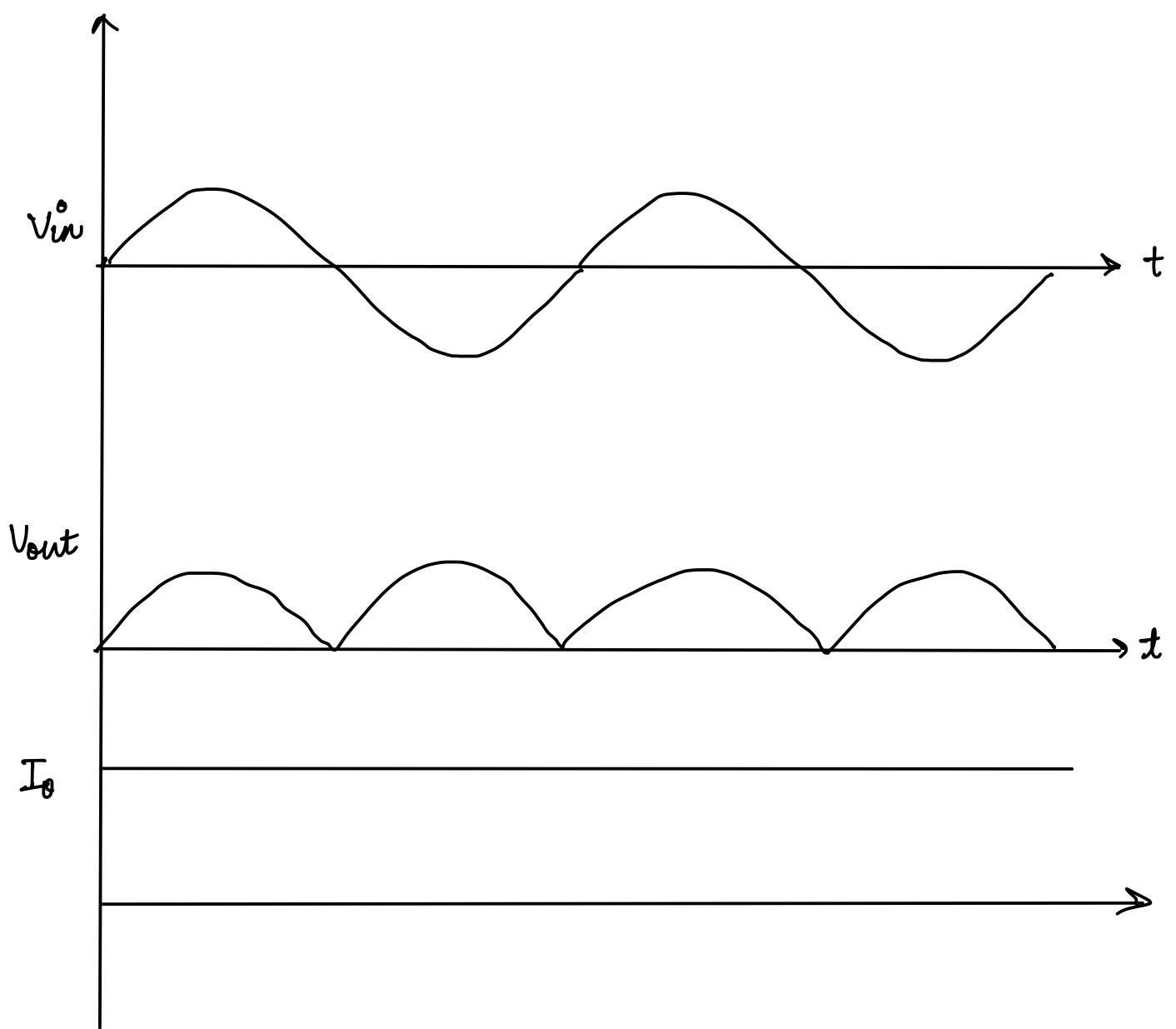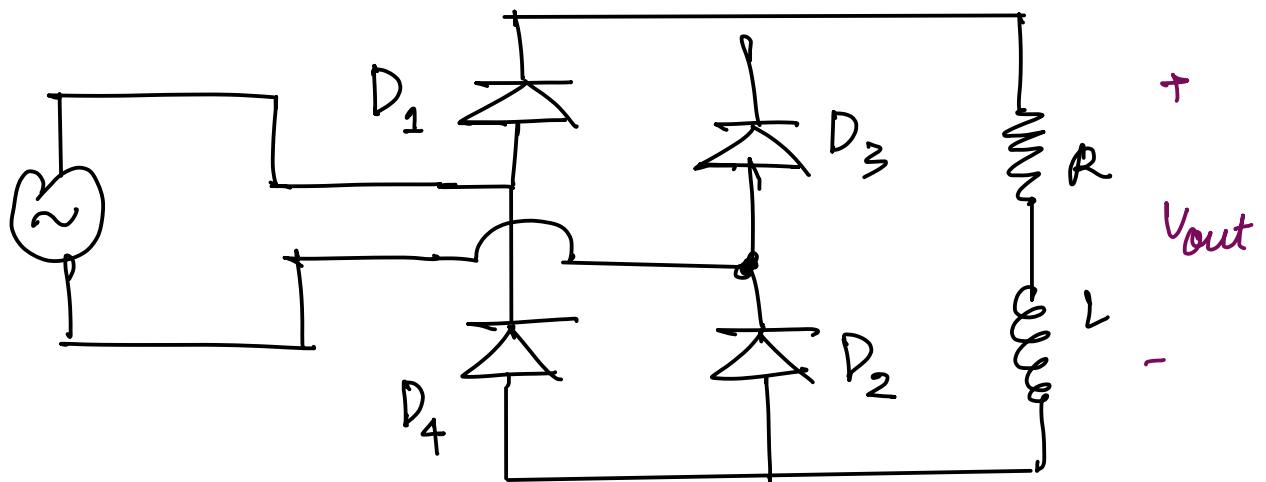



Half-Wave, Full Bridge with C-R load.

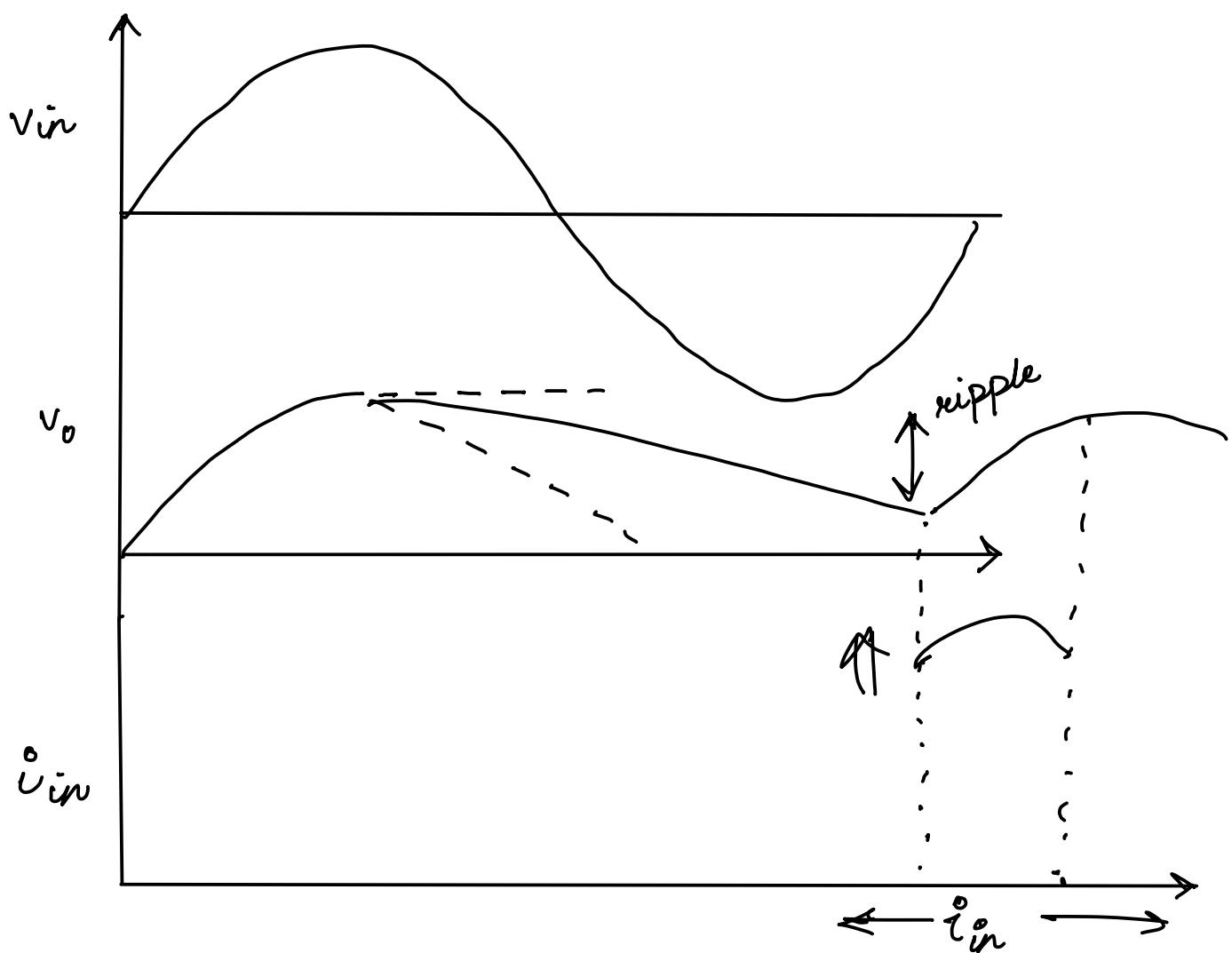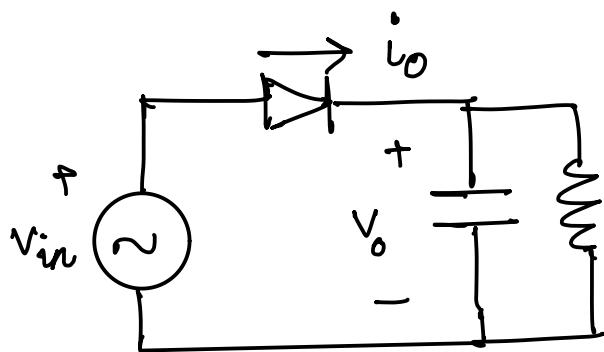


If C is large, diode may be damaged
power quality drops -


$$\langle V_o \rangle \approx 325 \text{ V}$$

- Semi-Controlled Device Based Rectifier

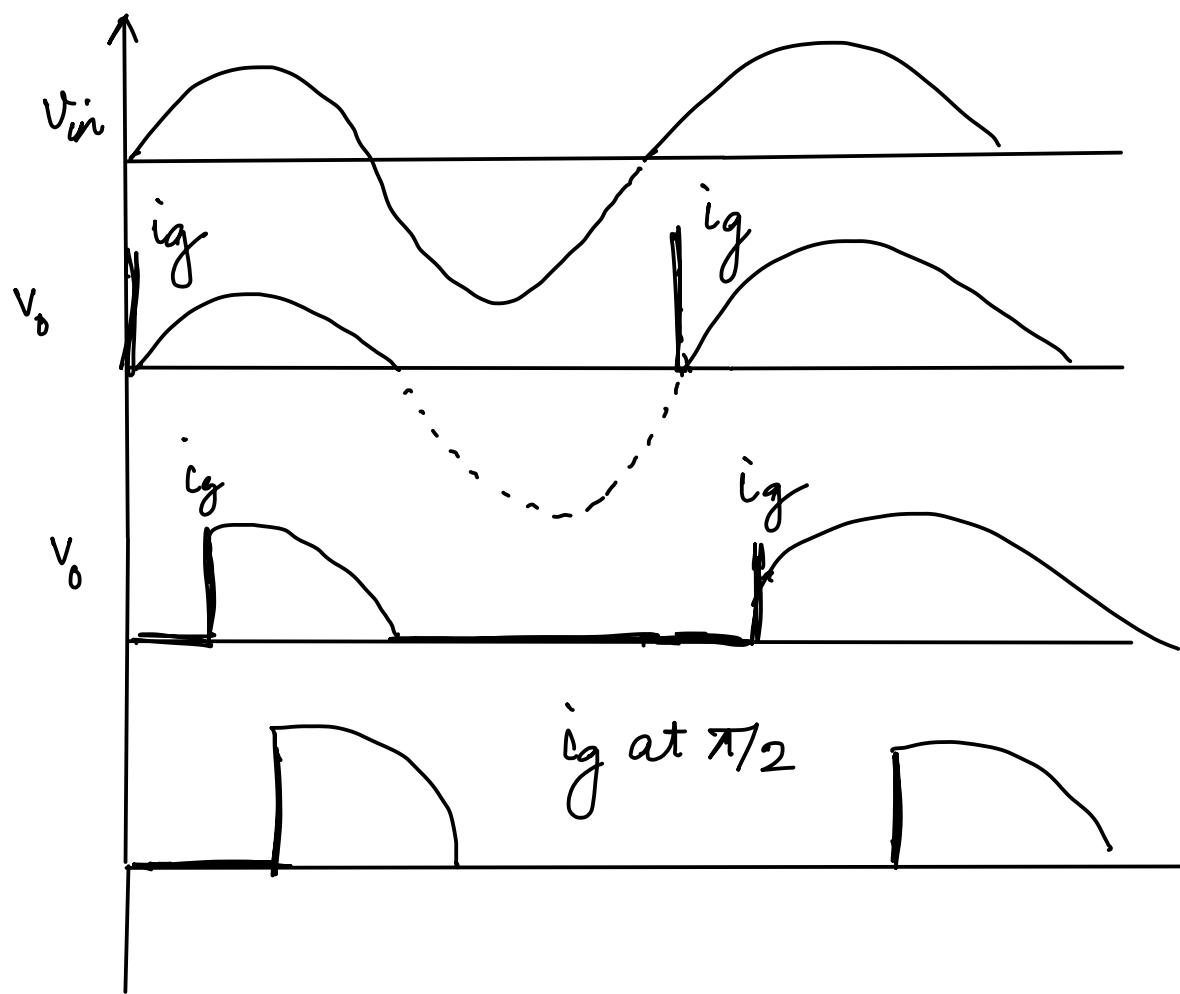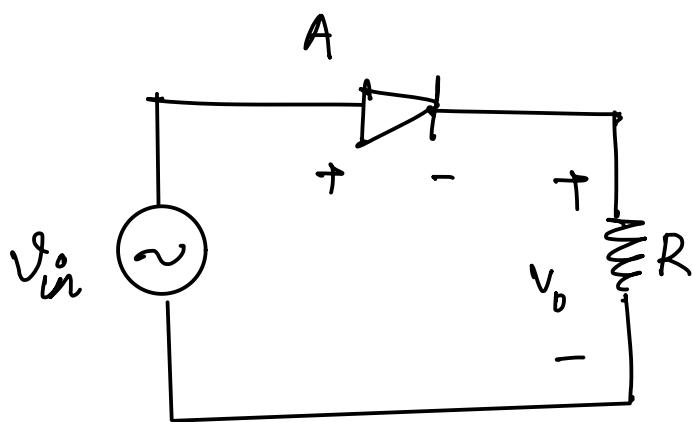

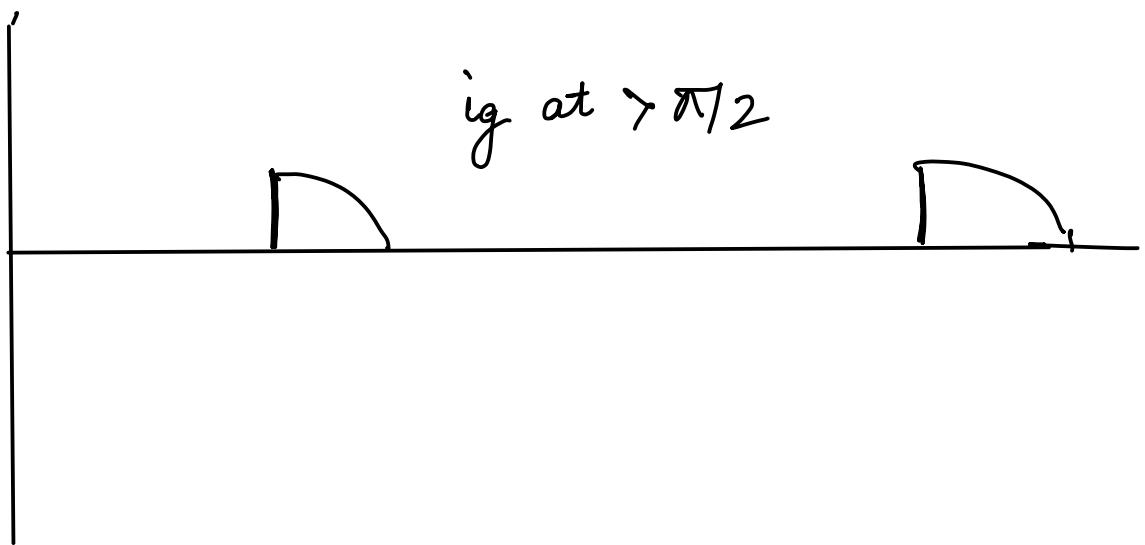



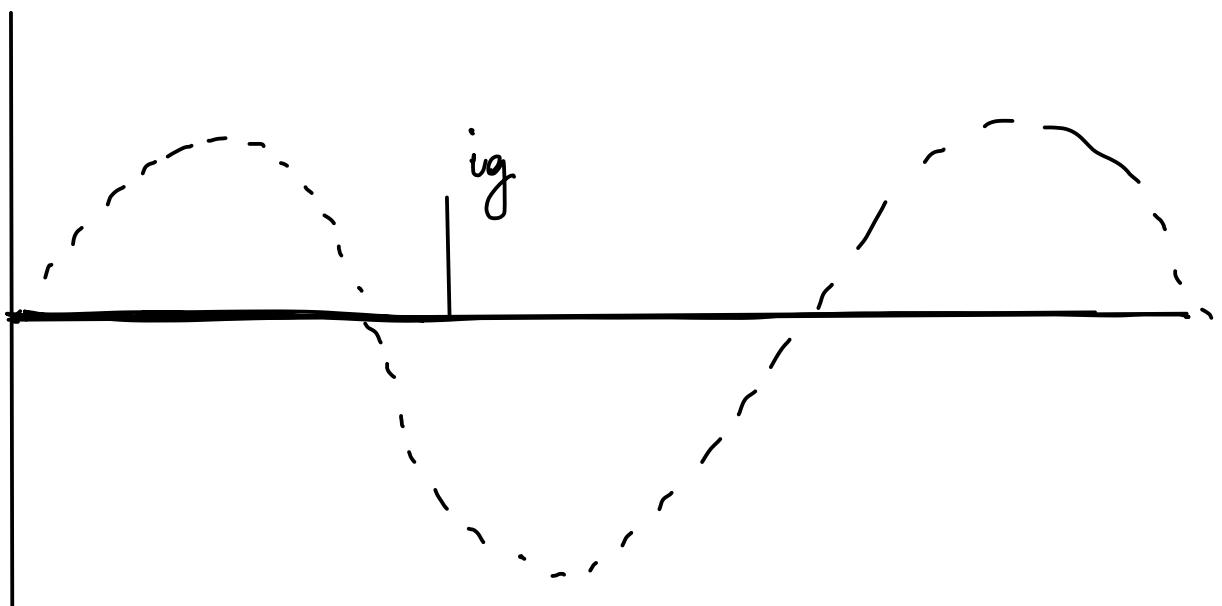
by varying i_g avg. output voltage can be varied.



For arc to be formed

- anode - cathode potential should be +ve ($V_{AK} > 0$)
- $i_g > 0$

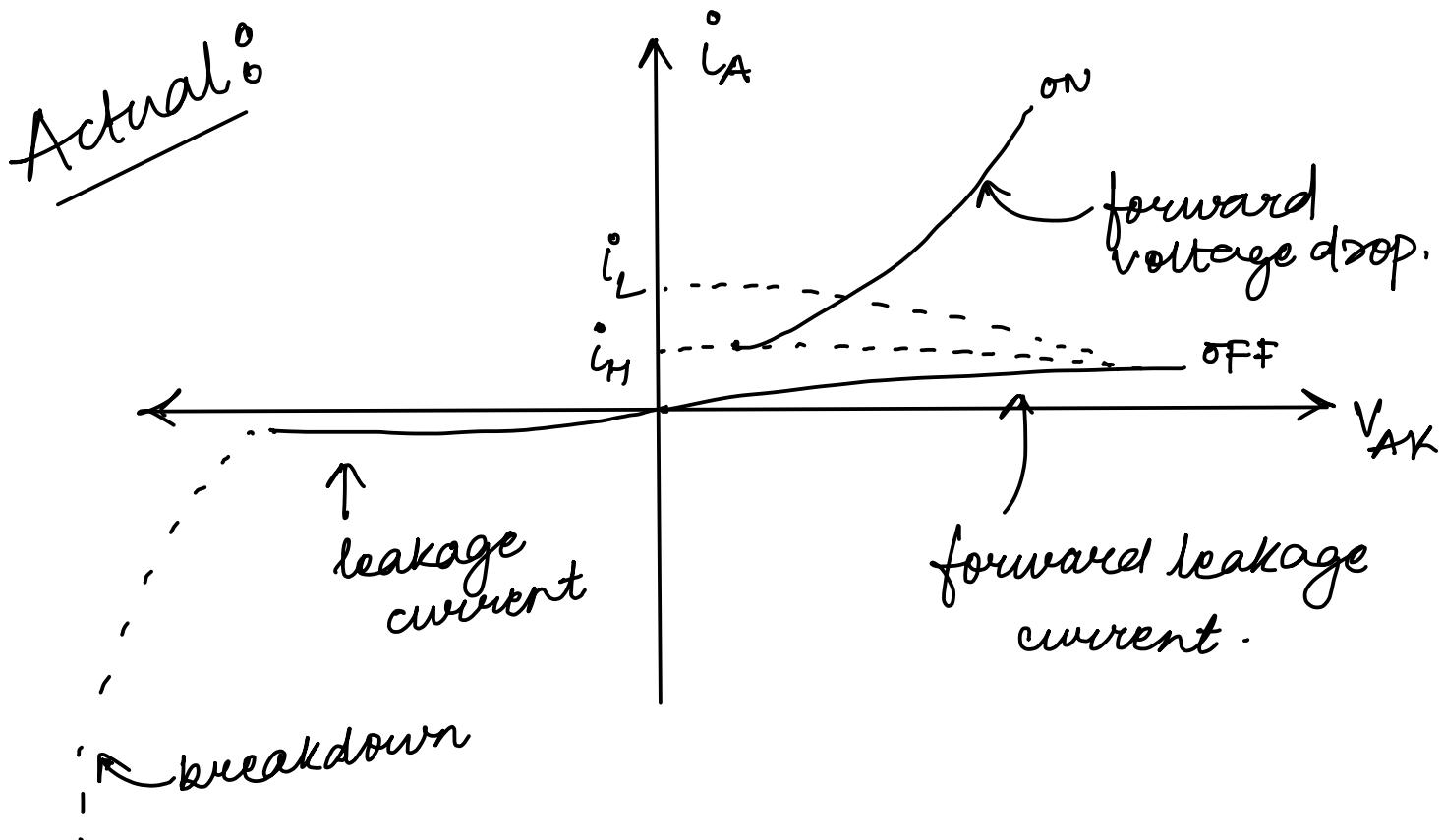
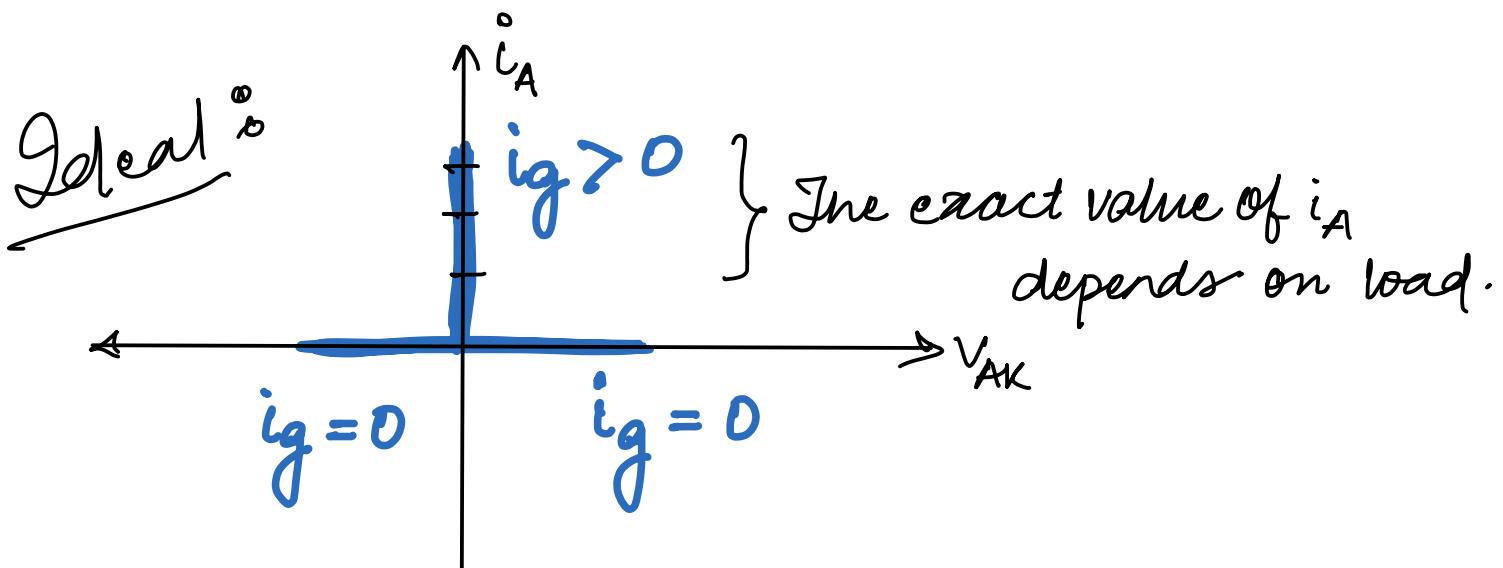
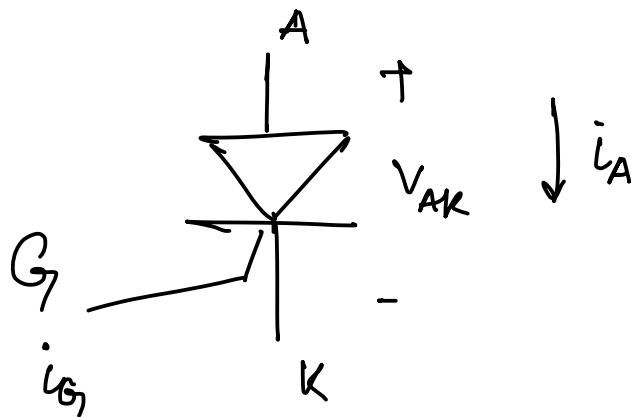
Thyristor (aka Silicon controlled Rectifiers)



i_L : Latching Current for device to turn off

i_H : Holding Current for device to remain on-

Power MOSFET

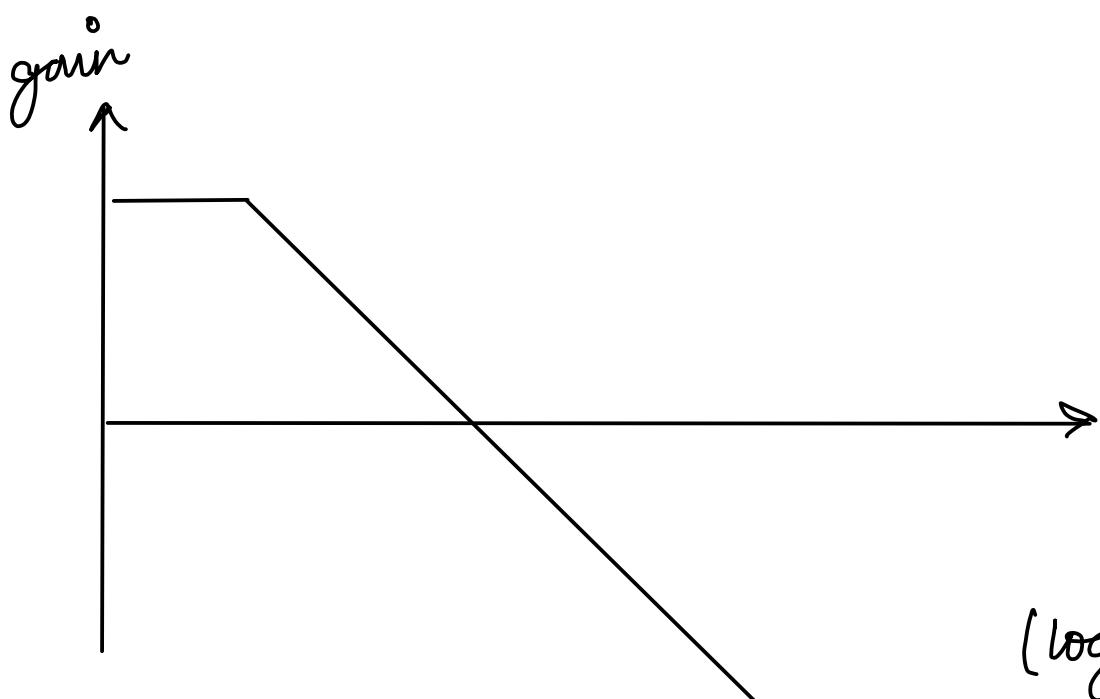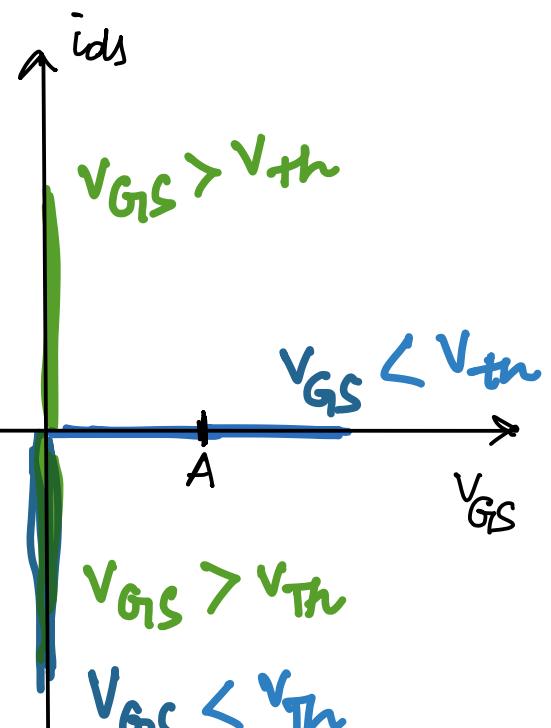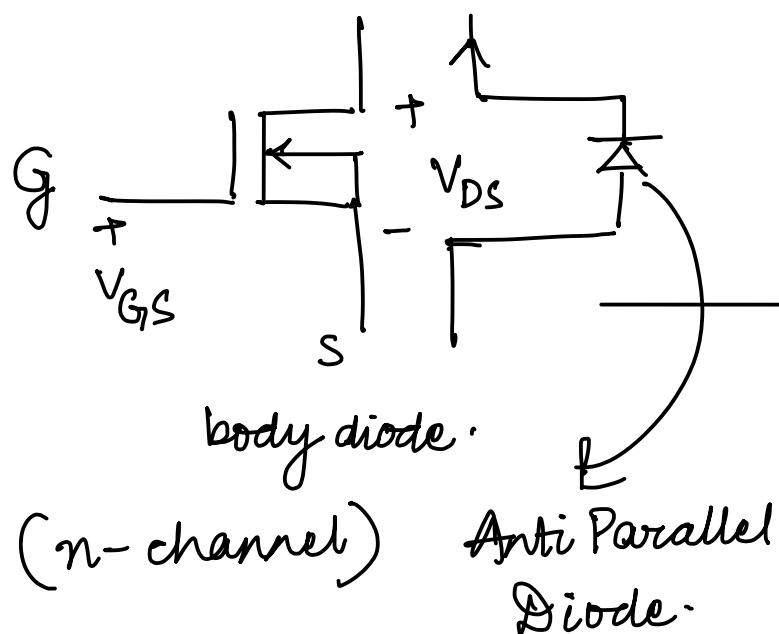

(log scale)

We want higher frequency to filter out the high frequency component easily

Higher frequency $\Rightarrow L, C$.

MOSFET \Rightarrow 100s kHz

IGBT \Rightarrow 10s kHz

IGCT \Rightarrow kHz


GTO \Rightarrow

Increasing
Blocking
Voltage.


→ Trade off between efficiency & size
due to F_s .

(switching frequency)

IGBT

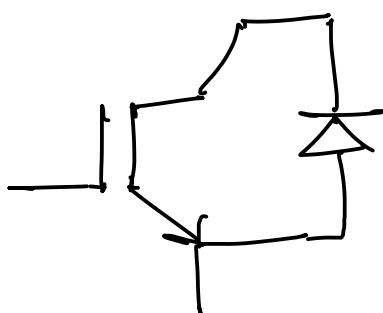

Diode

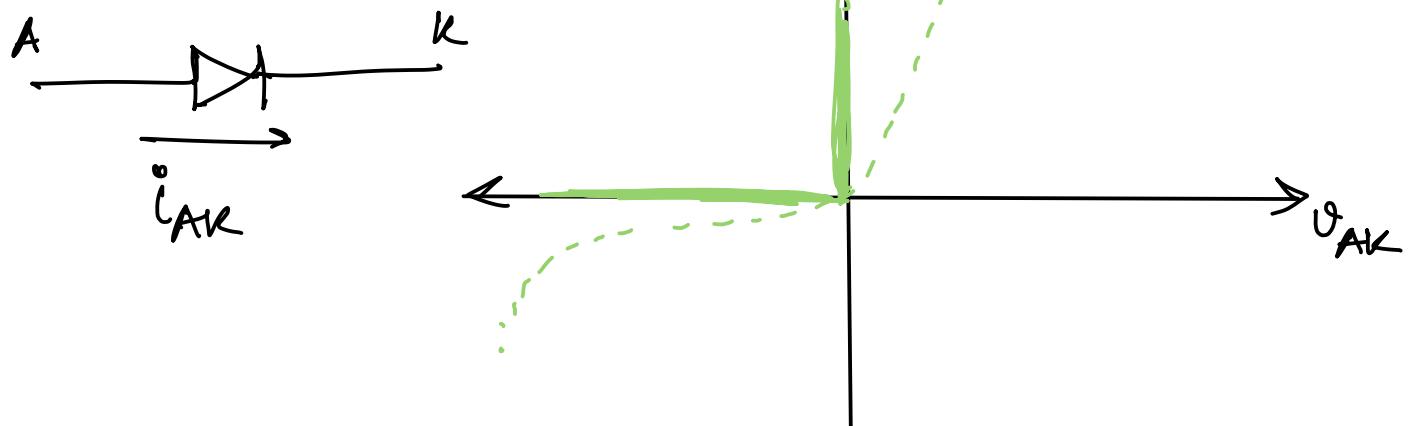



Uncontrolled \rightarrow Diode

Semi controlled \rightarrow Thyristor, Mercury Arc

Fully controlled \rightarrow MOSFET

Chargers \rightarrow Si \rightarrow GaN, SC

Buck Converters

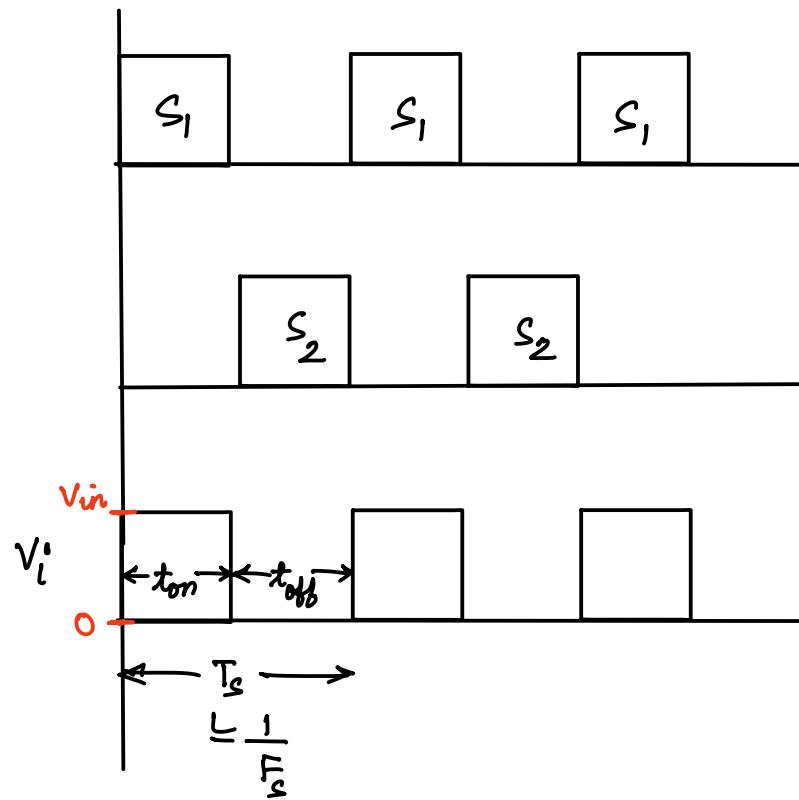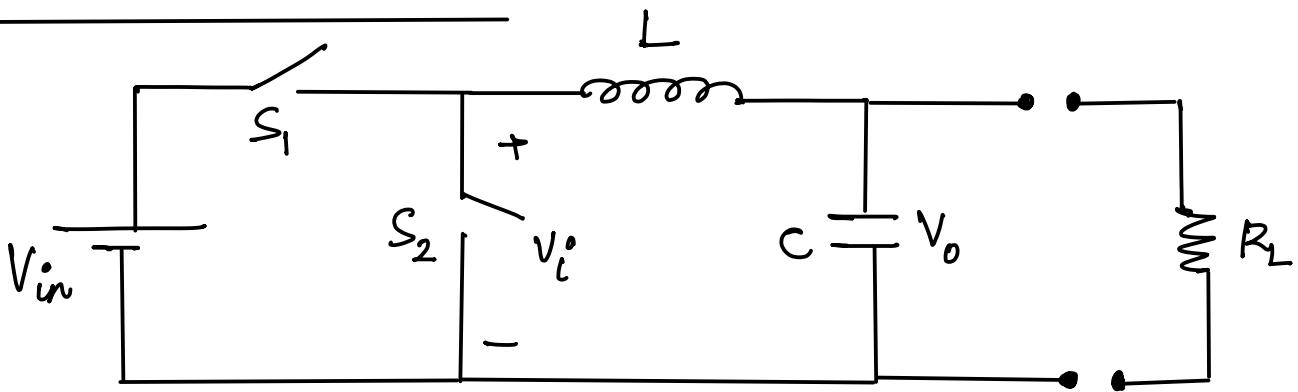


$$\begin{aligned} \langle v_i \rangle &= \frac{1}{T_s} \int_0^{T_s} v_i dt \\ &= \frac{1}{T_s} \left[\int_0^{t_{on}} V_{in} dt + \int_{t_{on}}^{T_s} 0 dt \right] \end{aligned}$$

$$= \frac{t_{on}}{T_s} V_{in} = D V_{in} (\langle v \rangle)$$

$$D = \frac{t_{on}}{T_s} = \text{Duty Cycle}$$



Fundamental defⁿ
of duty cycle.

Modulation Signal Generation

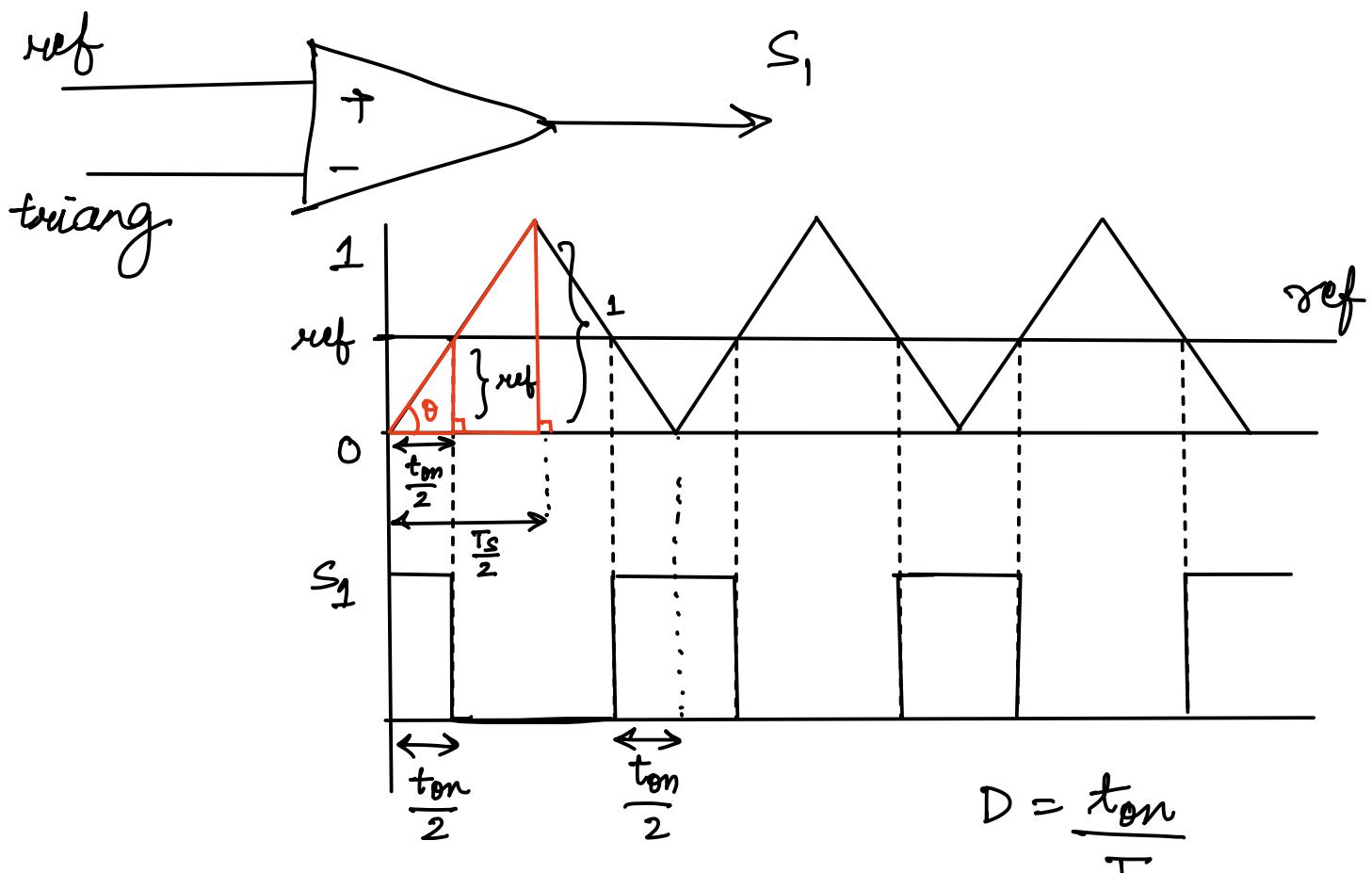

$$\tan\theta = \frac{1}{T_s/2} = \frac{(\text{ref})}{(t_{on}/2)}$$


$$\Rightarrow D = \text{ref}.$$

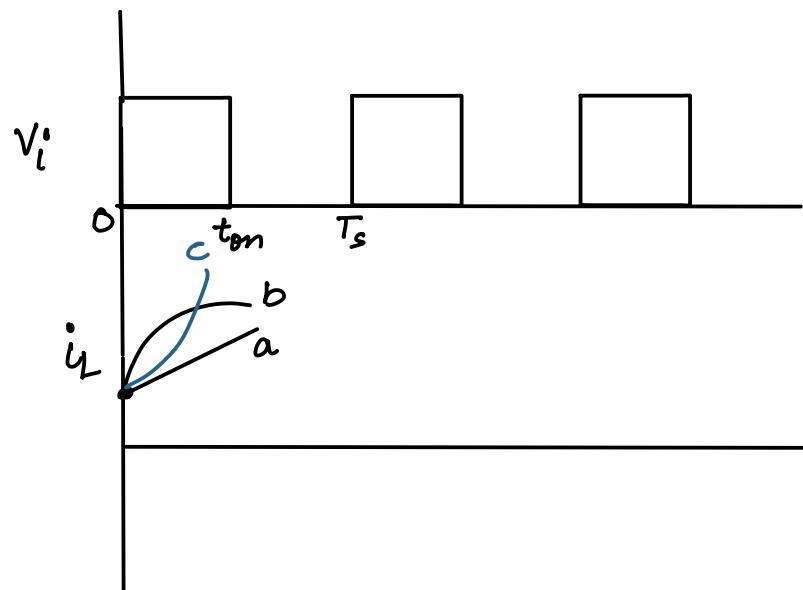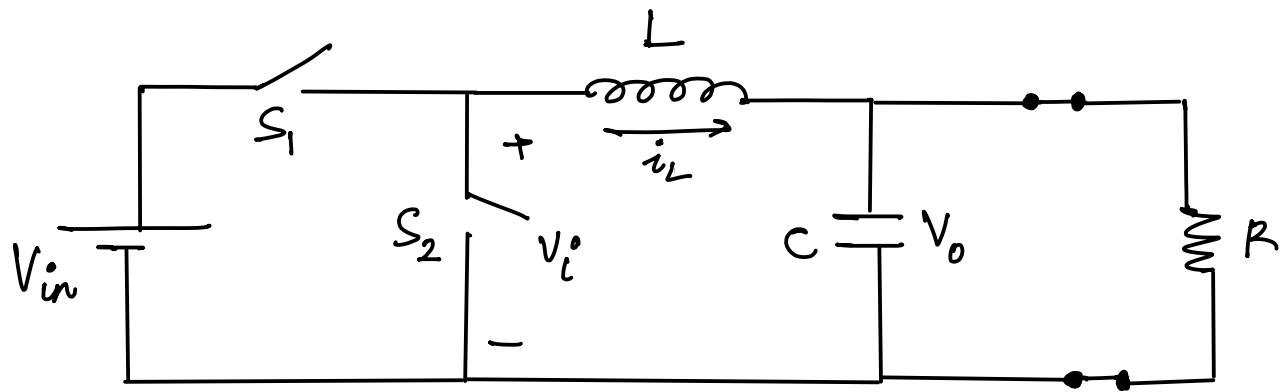

$a \rightarrow$ Ideal
 $b \rightarrow$ Real ($R + L$)
 $c \rightarrow$ If core is
 Saturable

For first part : $V_{in} - V_o = L \frac{di_L}{dt}$


For second part :

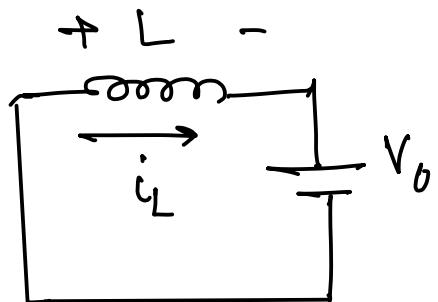

$$\rightarrow V_o = L \frac{di_L}{dt}$$

Average Output Voltage

Define voltage second balance

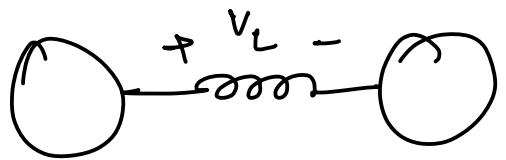

At sinusoidal steady state (S-SS)

$$f(x) = f(x+T)$$

Periodic Steady State


$$V_L = \frac{L di}{dt}$$

$$\int_{t=x}^{t=x+T} V_L dt = L \int_{i_L(x)}^{i_L(x+T)} di$$

$$\Rightarrow \frac{1}{T_S} \int_0^{T_S} V_L dt = L (i_L(x+T) - i_L(x)) = 0$$

$\Rightarrow \boxed{\langle V_L \rangle_{T_S} = 0} \rightarrow$ voltage second balance
 switching time period

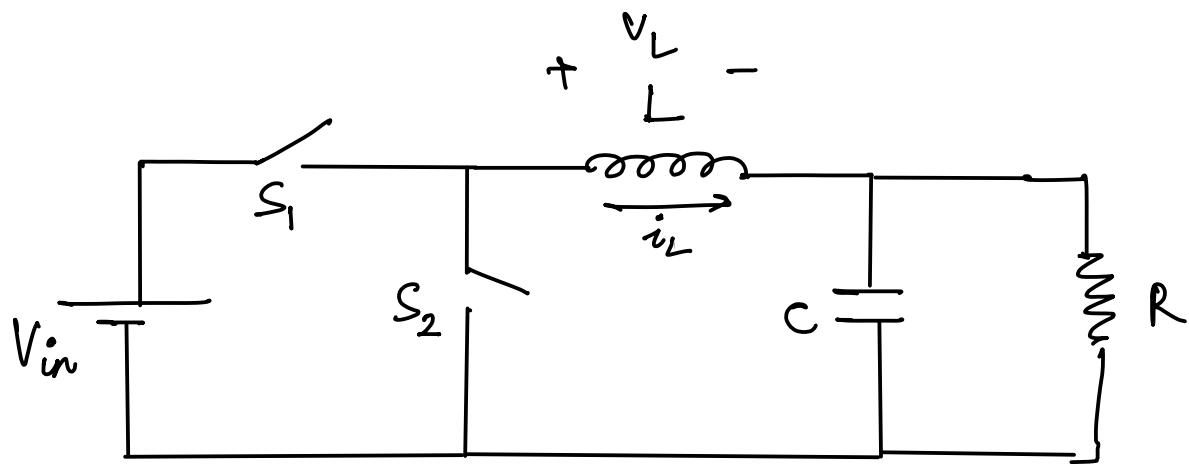
For capacitor: $\boxed{\langle i_C \rangle_{T_S} = 0}$



$$1) \quad 0 \leq t \leq DT_S$$

$$V_L = V_{in} - V_o$$

$$i_L(0) = i_L(T_S)$$

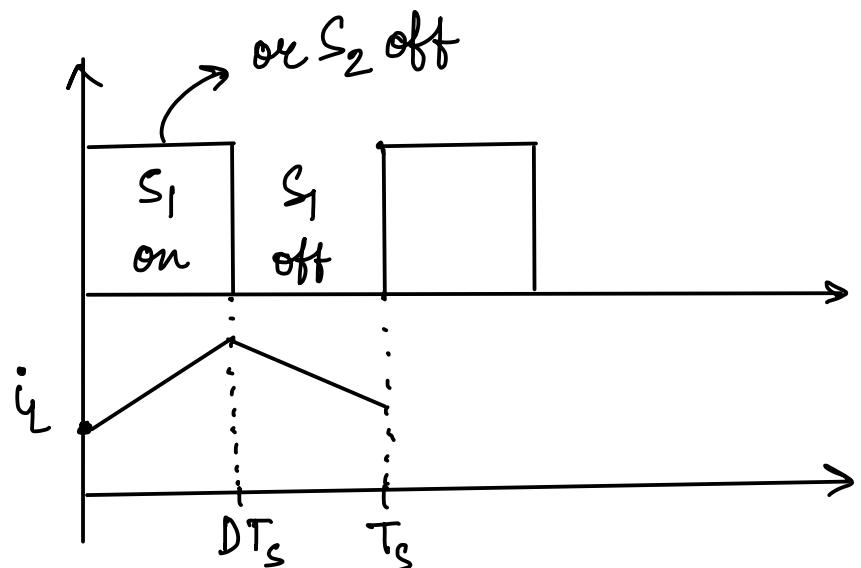

$$2) \quad DT_S \leq t \leq T_S$$

Voltage second balance:

$$\int_0^{T_S} V_L dt = 0$$

$$\int_0^{DT_S} (V_{in} - V_o) dt + \int_{DT_S}^{T_S} (-V_o) dt = 0$$

$$\Rightarrow (V_{in} - V_o) DT_S - V_o (T_S - DT_S) = 0$$


$$\Rightarrow V_o = V_{in} D$$

for buck in CCM

(graph of i_L is above time axis)

Current Ripple

Inductor ripple current

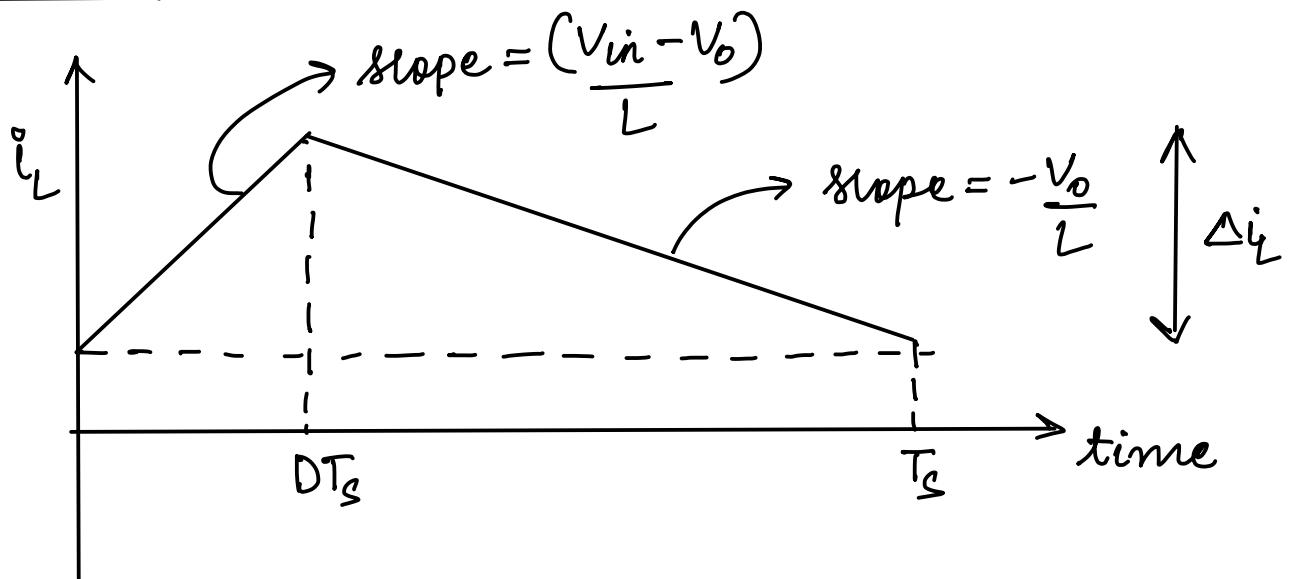

Δi_L : Inductor ripple current

$$V_L = L \frac{di}{dt}$$

$$\Rightarrow \int_{0}^{DT_S} V_L dt = \int_{i_{min}}^{i_{max}} L di$$

$$\Rightarrow (V_{in} - V_o) DT_S = L \Delta i_L$$

$$\Rightarrow \Delta i_L = \frac{(V_{in} - V_o) DT_S}{L}$$

$$\Rightarrow \Delta i_L = \frac{(V_{in} - D V_{in}) DT_S}{L} \quad (\text{only for ccm})$$

$$\Rightarrow \Delta i_L = \frac{(1-D)D V_{in} T_S}{L} \rightarrow \text{for ccm}$$

\uparrow inductance, ripple \downarrow

$\uparrow F_S \Rightarrow T_S \downarrow \Rightarrow$ ripple \downarrow


For a given Δi_L , how to reduce L (because we want to reduce size of L)

$F_S \uparrow\uparrow$ (but switching losses increase)

- Δi_L max happens at $D = 0.5$

$D \rightarrow$ usually fixed by V_{in} and V_o


Capacitor Voltage Ripple

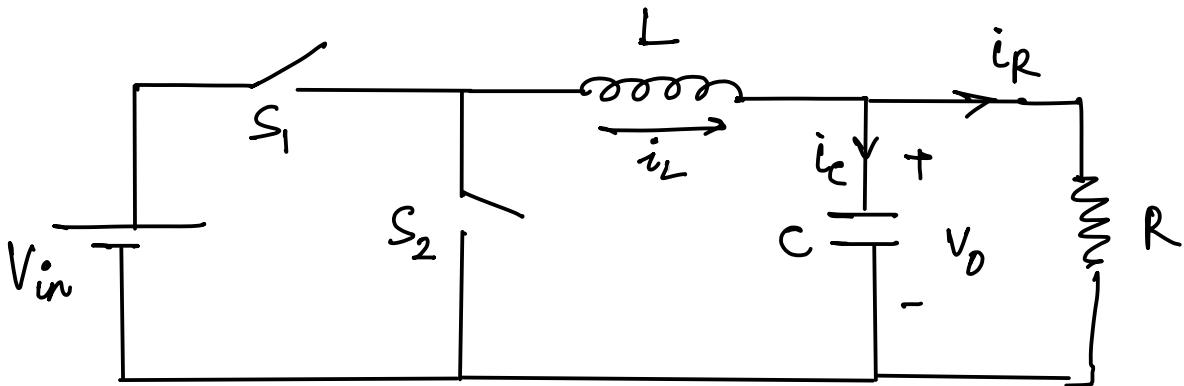

$$i_L = i_C + i_R$$

↘
 ripple ↗ avg
 ↘
 ripple ↗ avg.
 ↘
 → avg.

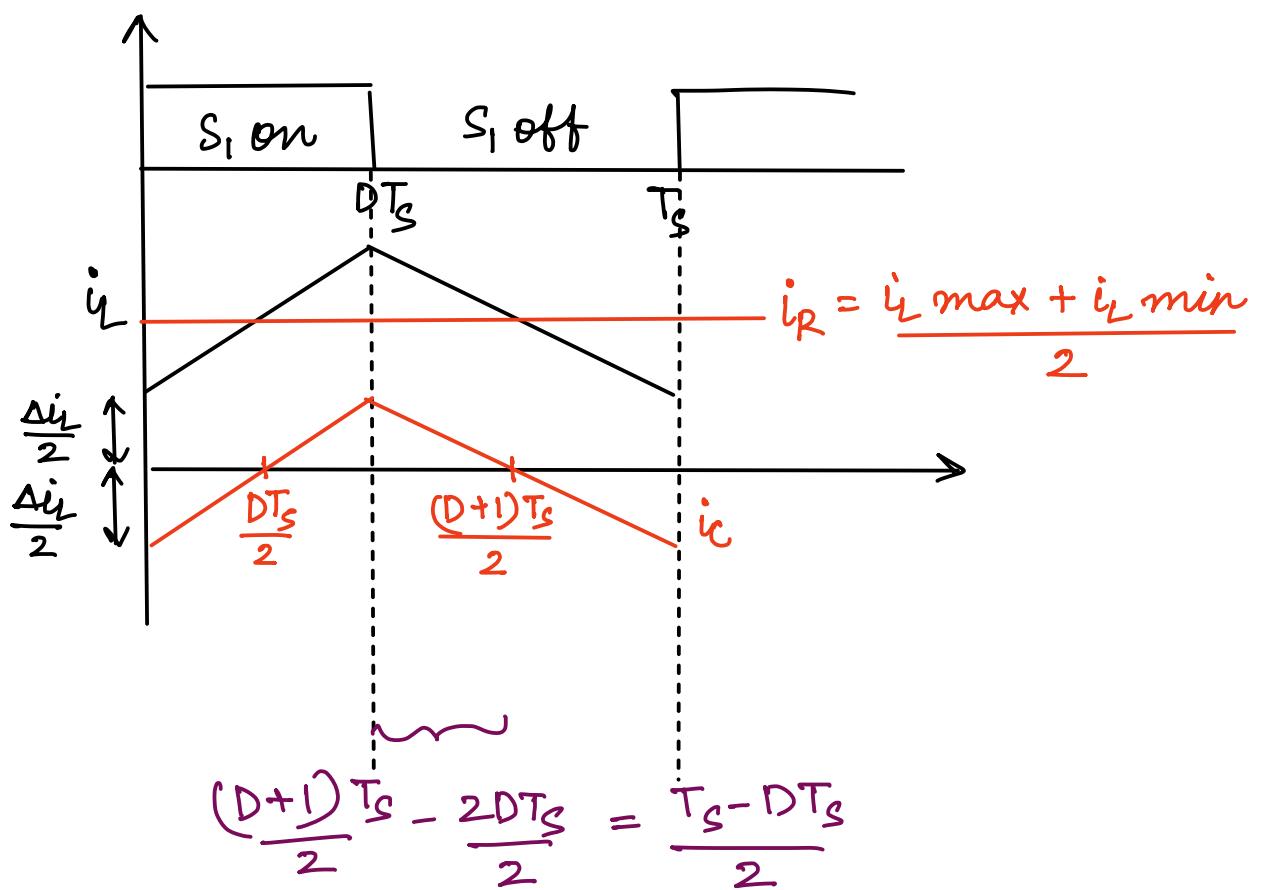(Because avg. current of capacitor is zero and as i_R is dc no ripple will go to i_R)



"Amperie-Second Law"


$$i_c = \frac{cdv_c}{dt}$$

Or assuming S-SS

$\int i_c dt = \int cdv_c$

$$\Rightarrow \int_{0}^{T_S} i_c dt = 0 \quad \Rightarrow \text{Average capacitor current} = 0$$

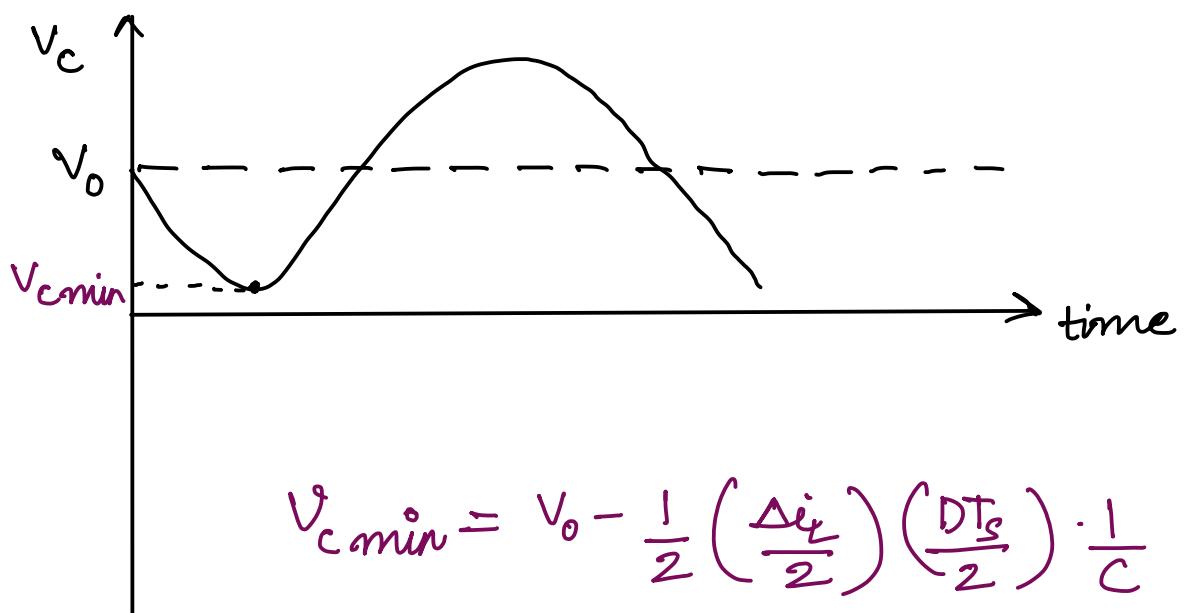This circuit is linear $v_c = \frac{\int i_c dt}{C}$



$$v_{c\min} = v_0 - \frac{1}{2} \left(\frac{\Delta i_c}{2} \right) \left(\frac{DT_S}{2} \right) \cdot \frac{1}{C}$$



$$= v_0 - \frac{(1-D)D^2 V_{in} T_S^2}{8LC}$$

$$V_{C\max} = V_0 + \frac{1}{2} \left(\frac{\Delta i_L}{2} \right) \frac{T_S (1-D)}{2} \cdot \frac{1}{C}$$

$$= V_0 + \frac{(1-D)^2 D V_{in} T_S^2}{8LC}$$

$$\therefore \text{Voltage ripple of capacitor} = \frac{(1-D)D V_{in} T_S^2}{8LC}$$

Q How do the horns of vehicles work?

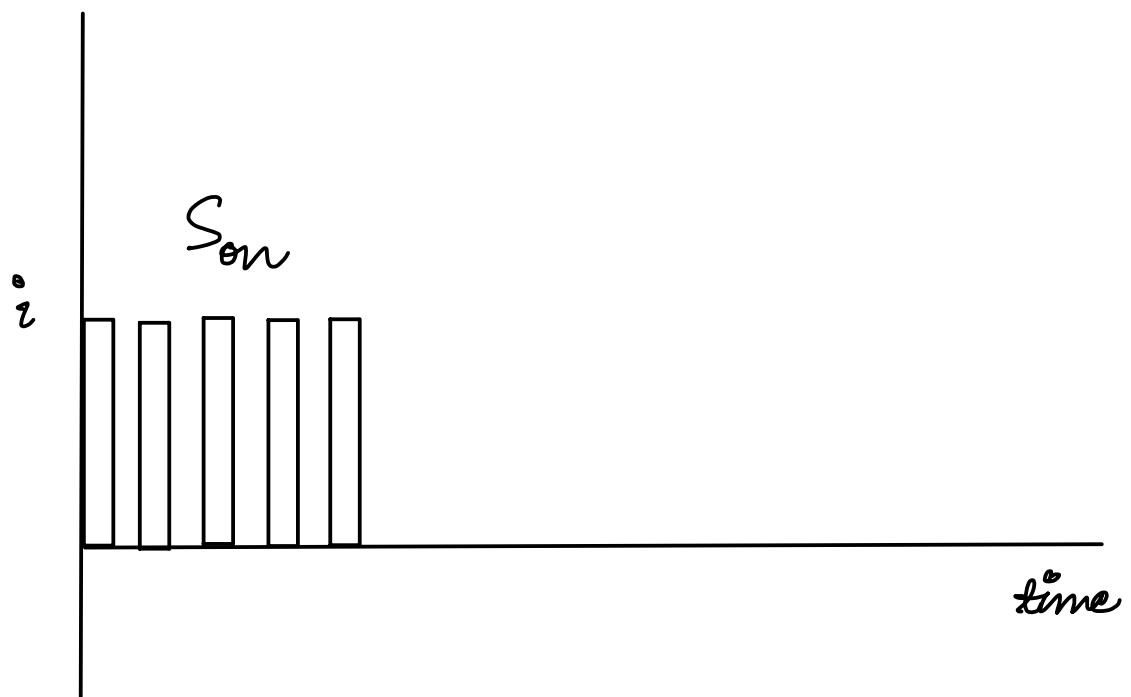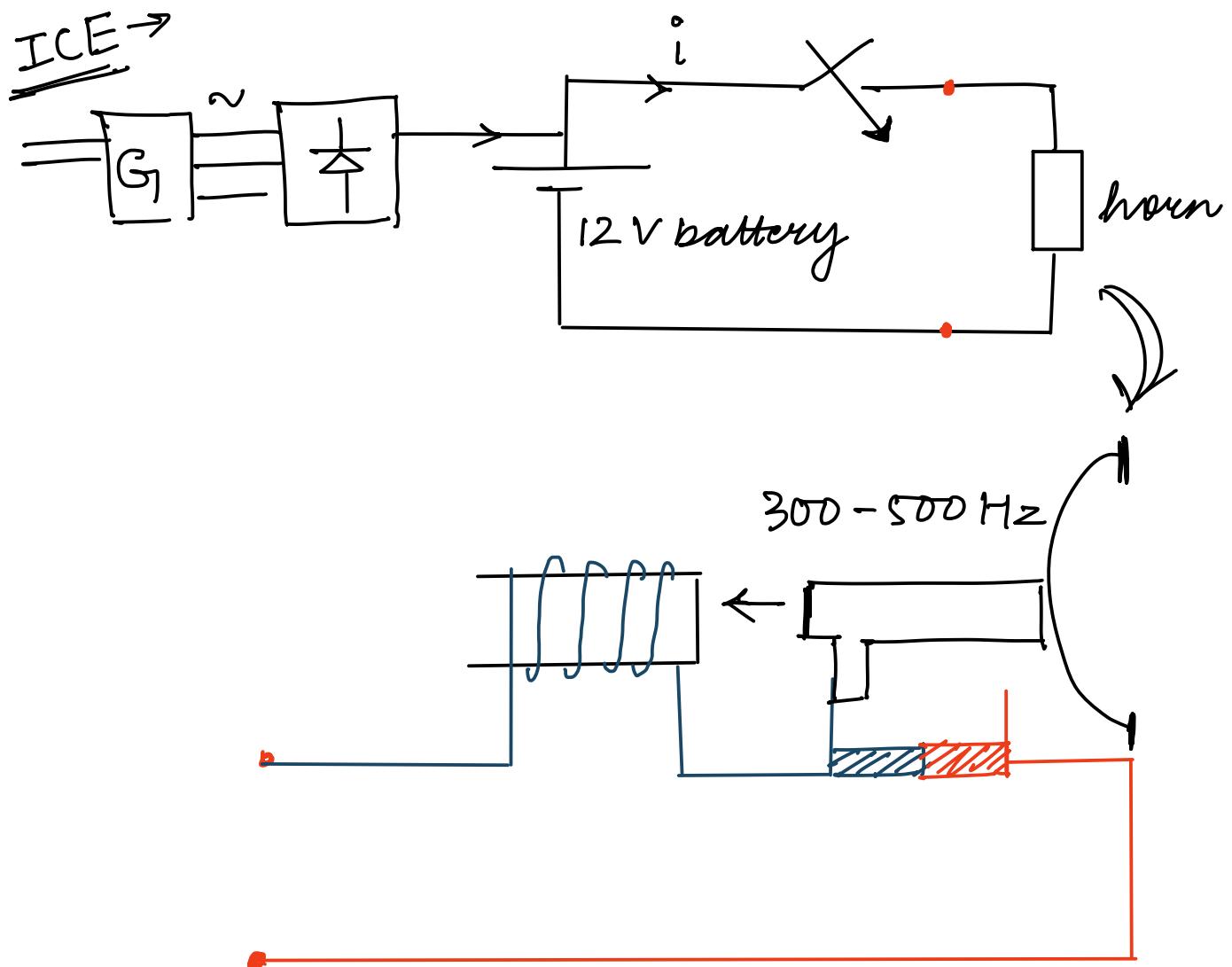


EV

48V battery - EV two wheeler


400V battery - EV four wheeler

EV 2 wheeler

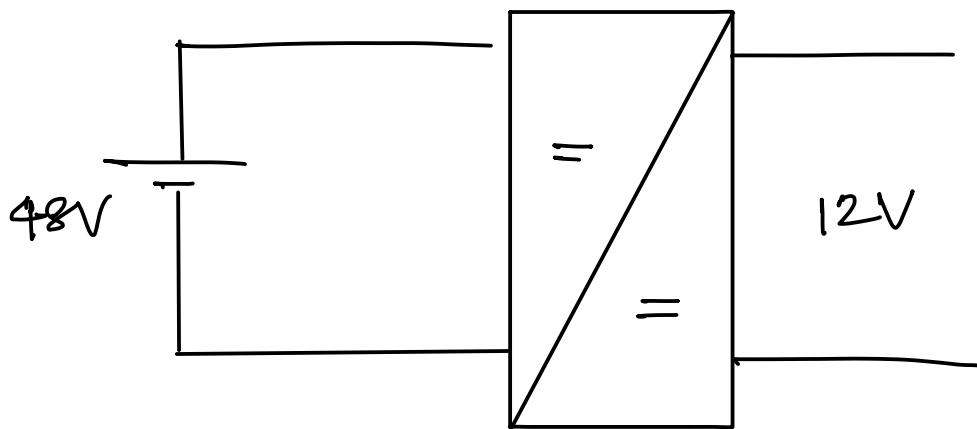


We could have changed other parameters (n of solenoid) to make the horn work with 48V - But that is not cost economic .

So we use DC-DC buck converter.

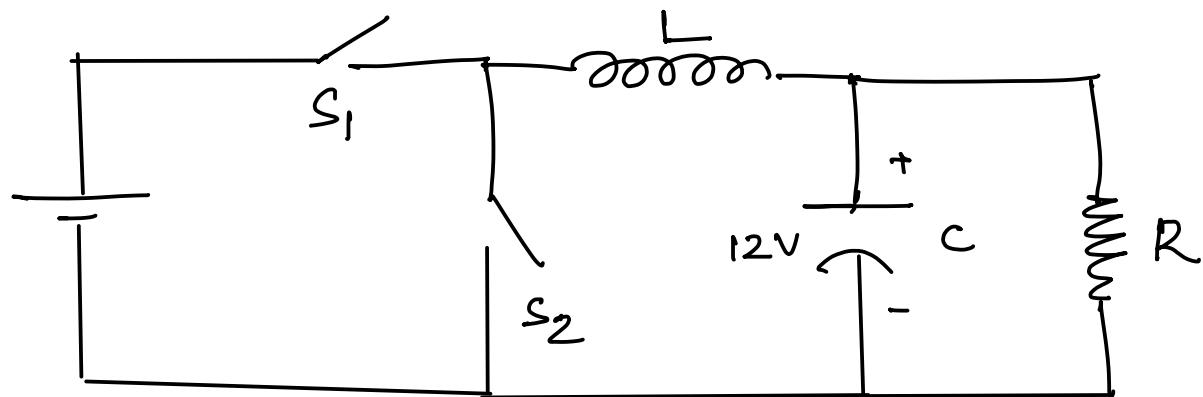
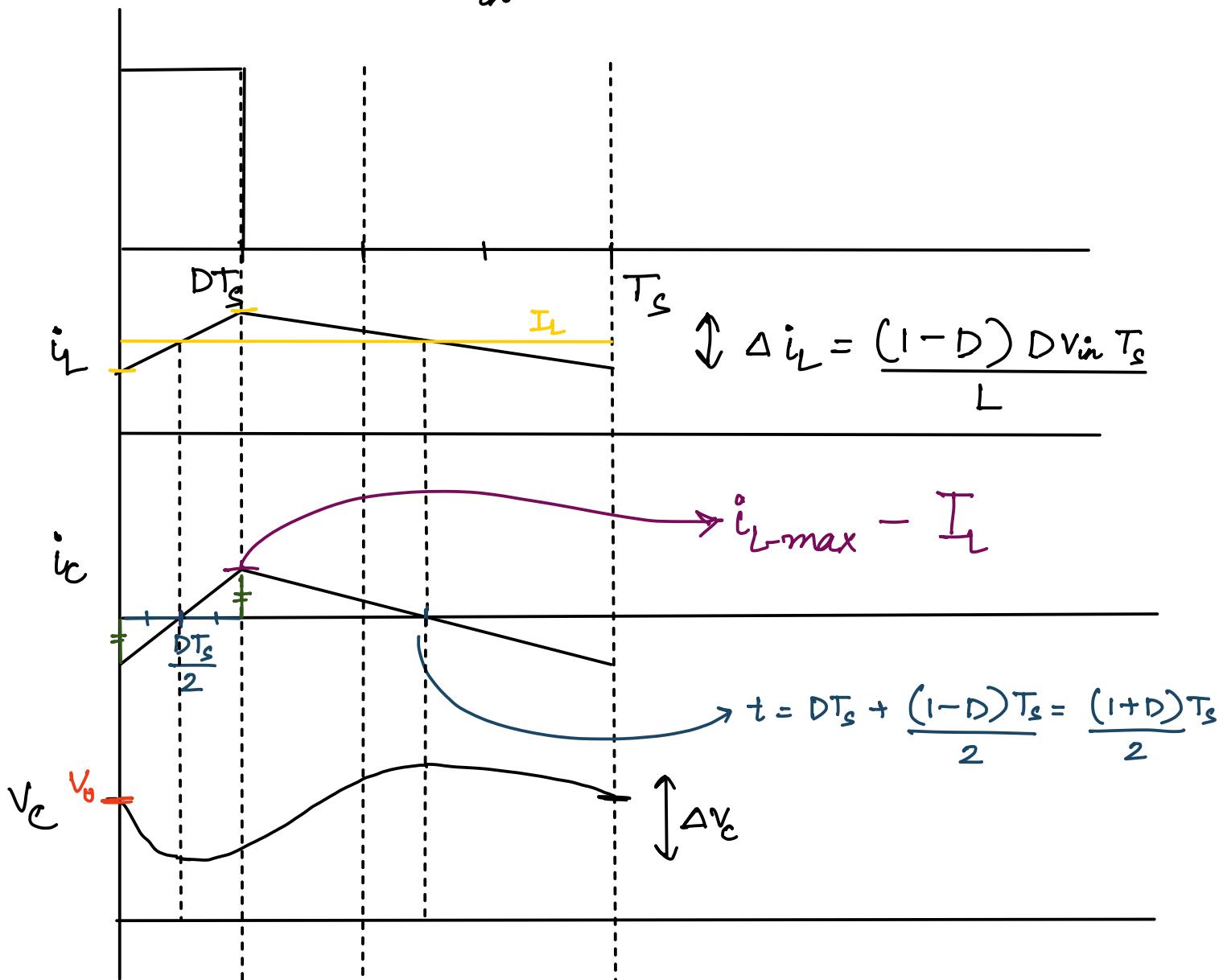
$$\text{Duty cycle of } S_1 = \frac{V_o}{V_{in}} = 0.25$$



$$i_C = i_L - i_R$$

$$i_C = i_L - I_L$$

$$i_C = C \frac{dV_C}{dt}$$

$$\dot{i}_c = C \frac{dV_c}{dt}$$

$$\int_{\frac{DT_S}{2}}^{\frac{(1+D)T_S}{2}} \dot{i}_c dt = C \int_{V_{c \min}}^{V_{c \max}} dV_c = \frac{1}{2} \left(\frac{T_S}{2} \right) \left(\frac{\Delta i_L}{2} \right)$$


↑ ↑
 base height

$$\Delta V_c = \frac{\Delta I_L T_S}{8C} = \frac{(1-D) D V_{c \min} T_S^2}{8LC}$$

Reduce ripple: 2% → 1%

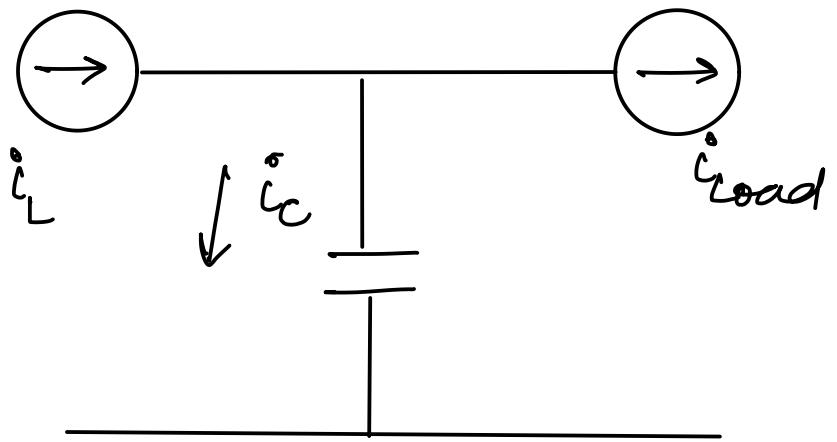- $C \uparrow$] size issue
- $L \uparrow$]
- $T_S \downarrow = \frac{1}{F_S \uparrow}$] efficiency issue







$$\dot{i}_c = \dot{i}_L - \dot{i}_{\text{load}}$$

$$= [I_L + \Delta i_L(t)] - [I_{\text{load}} + \Delta i_{\text{load}}(t)]$$

$$\langle \dot{i}_c \rangle = 0$$

Hence will actually increase the ripple.

Switches

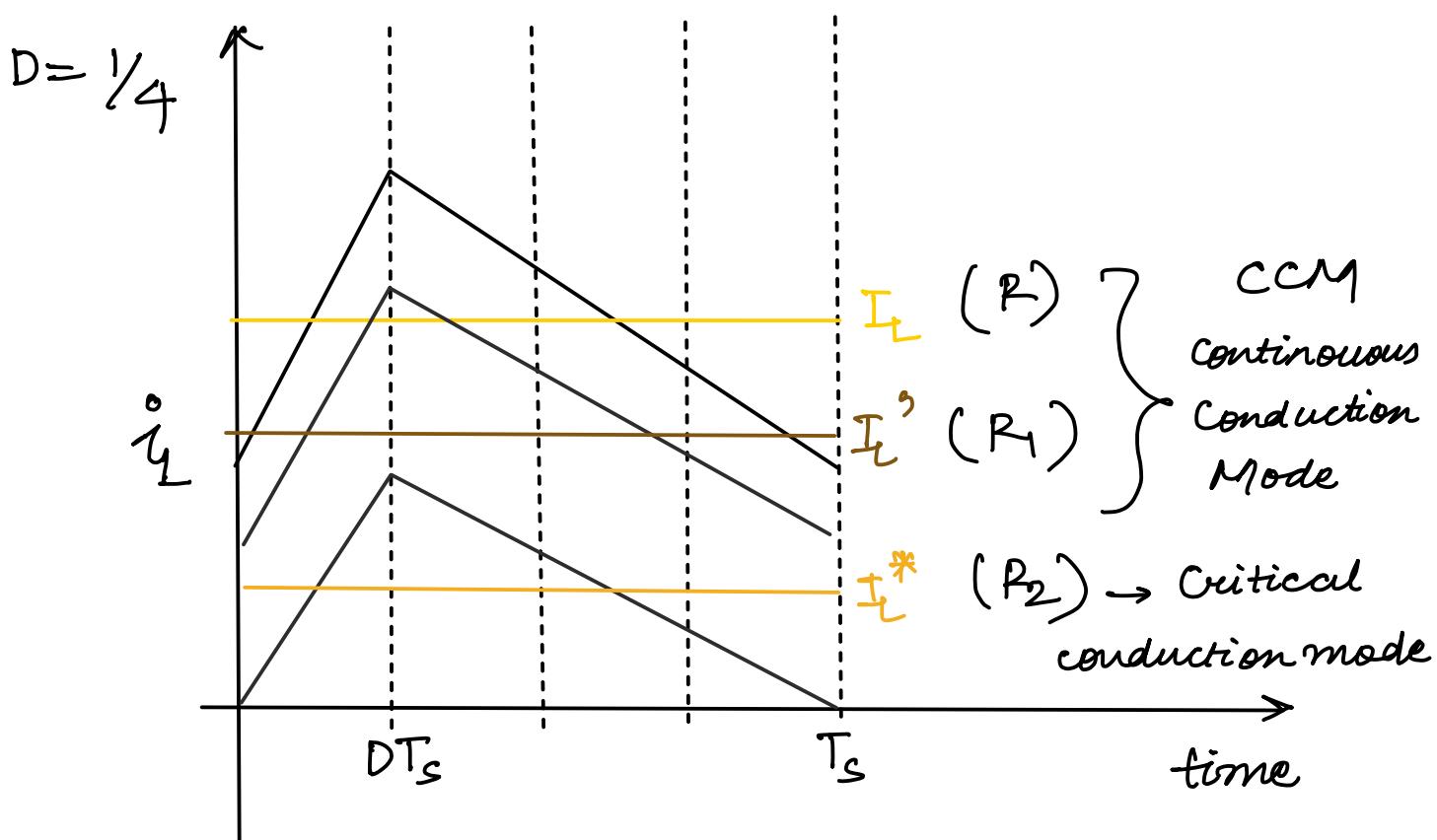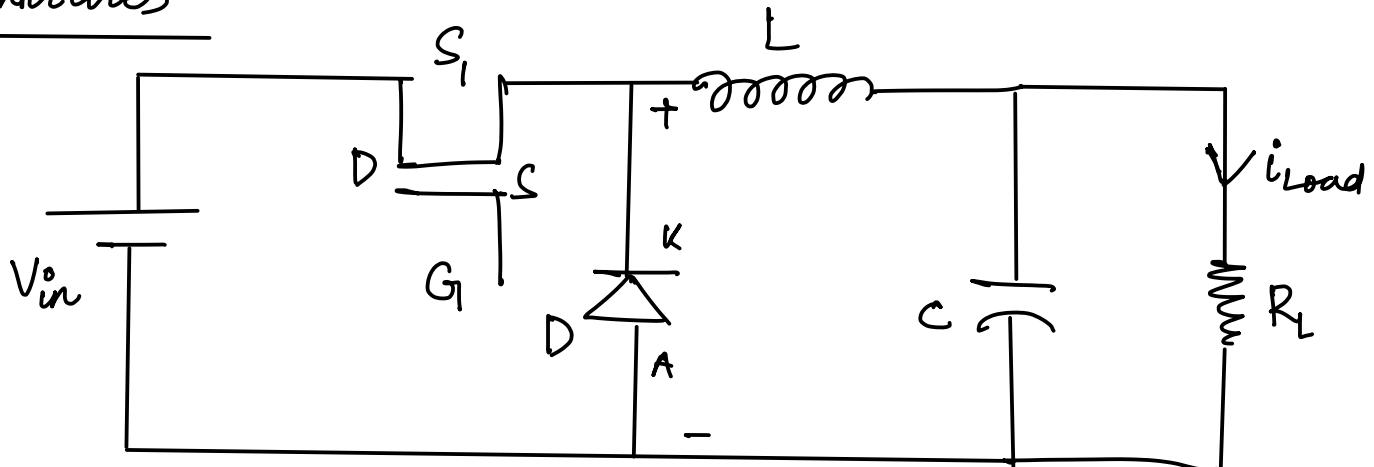



Q What would happen if R_L increases?

$$i_{\text{load}} \downarrow \Rightarrow I_{\text{load}} \downarrow \Rightarrow I_L \downarrow \quad (V_o \rightarrow \text{constant})$$

Reduce Load \rightarrow Reduce Load Current.
(Increase Resistance)

$$R \rightarrow R_1 \rightarrow R_2 \longrightarrow R_3$$

(very large value)

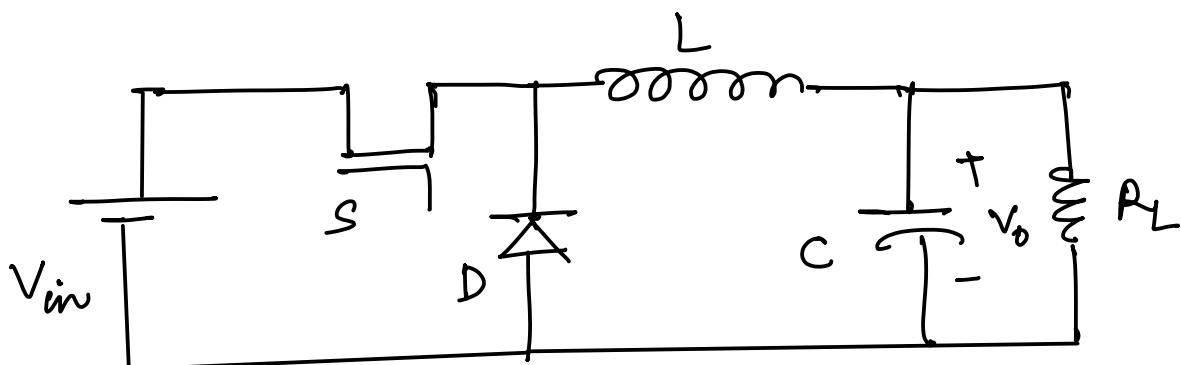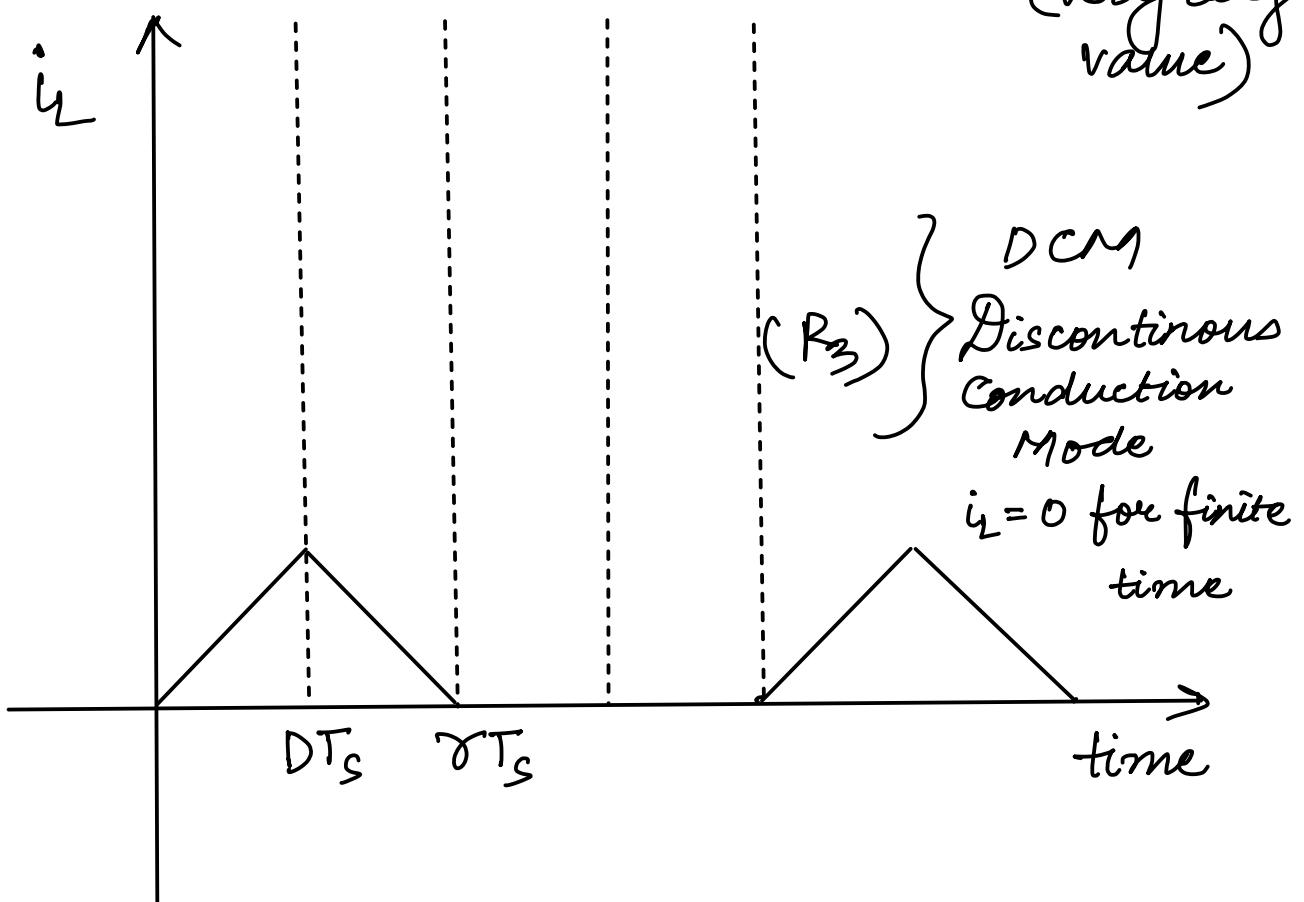

$$I_L > \frac{\Delta i_L}{2} \rightarrow CCM$$

$$\Rightarrow \frac{V_o}{R_L} > \frac{(V_{in} - V_o) D T_S}{2L}$$

$$\Rightarrow R_L < \frac{2L}{(1-D) T_S} \rightarrow CCM$$

$$R_{critical} = \frac{2L}{(1-D)T_S}$$


DCM

$0 - DT_S$: switch S is on

$$V_L = V_{in} - V_0$$

$DT_S \rightarrow \gamma T_S$: S "OFF" ; D "ON"

$$V_L = -V_0$$

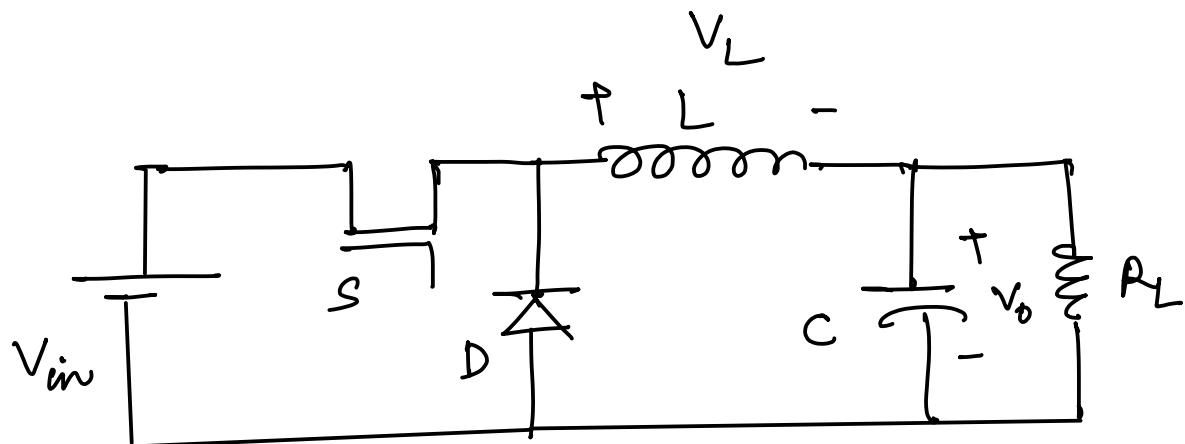

$\gamma T_S \rightarrow T_S$: S "OFF" ; D "OFF"

$$V_L = 0$$

$$\langle V_L \rangle = 0 \quad (\text{since circuit is in S-SS})$$

$$\Rightarrow (V_{in} - V_0) DT_S + (-V_0)(\gamma - D)T_S + 0 (1 - \gamma)T_S = 0$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = \frac{D}{\gamma}} \quad \text{--- } \textcircled{1}$$

O/P Voltage does not remain constant on varying R_L

$$\langle I_L \rangle = \frac{V_o}{R_L}$$

$$\Rightarrow \frac{1}{2} \times \frac{\cancel{\tau T_S} \times i_{peak}}{\cancel{T_S}} = \frac{V_o}{R_L} \quad \text{--- } \textcircled{2}$$

$$(V_{in} - V_o) = L \frac{(i_{peak} - 0)}{DT_S} \quad \text{--- } \textcircled{3}$$

$$\Rightarrow \text{From } \textcircled{2} \text{ we have: } V_o = \frac{R_L \gamma i_{peak}}{2} = \frac{DV_{in}}{\gamma}$$

$$\frac{1}{2} \left(\left(V_{in} - \frac{DV_{in}}{\gamma} \right) \frac{DT_S}{L} \right) R_L \gamma = \frac{DV_{in}}{\gamma}$$

from $\textcircled{1}$

$$\Rightarrow \frac{(\gamma - D)T_S R_L \gamma}{2L} = 1$$

$$\Rightarrow (\gamma - D)\gamma = \frac{2L}{R_L T_S}$$


$$\Rightarrow \gamma^2 - D\gamma - \frac{2L}{R_L T_S} = 0$$


$$\gamma = \frac{D \pm \sqrt{D^2 + \frac{8L}{R_L T_S}}}{2}$$

reject γ which is more than D



$$\Rightarrow \boxed{\gamma = \frac{D - \sqrt{D^2 + \frac{8L}{R_L T_S}}}{2}}$$

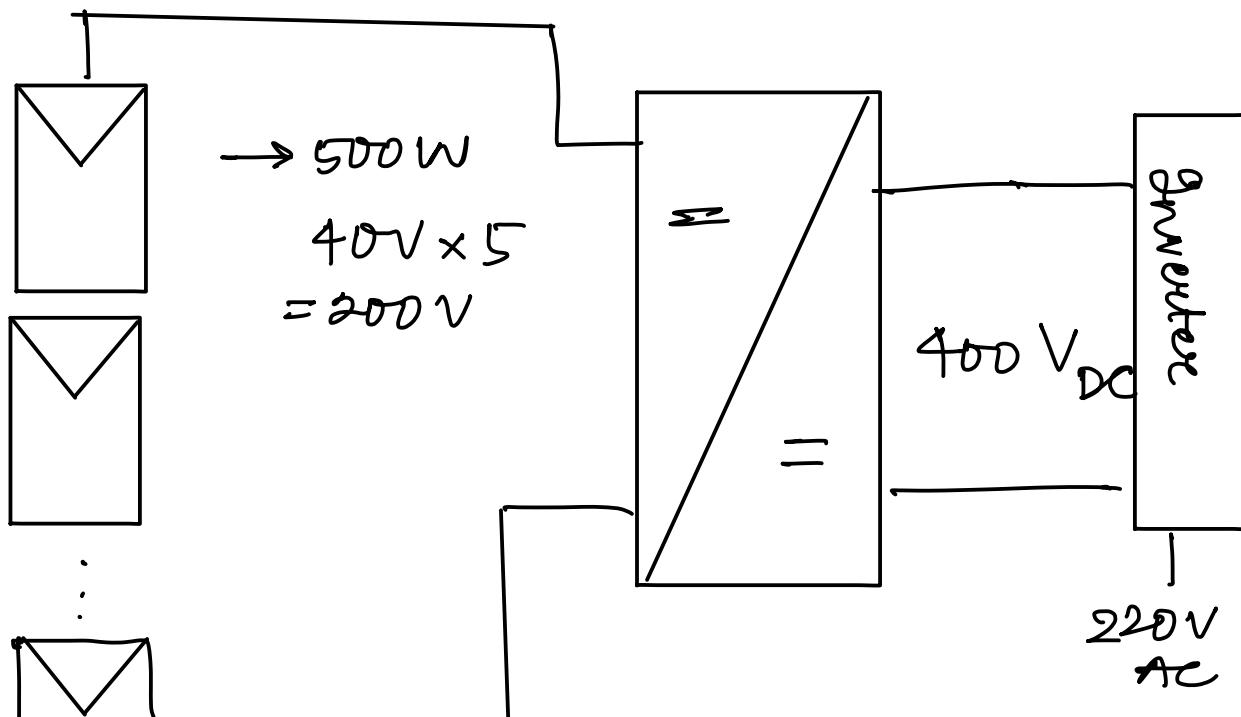$V_o > V_{in} \rightarrow$ Boost Converter.



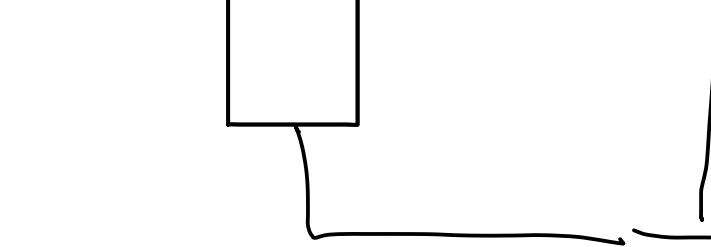

DC-DC Boost Converter

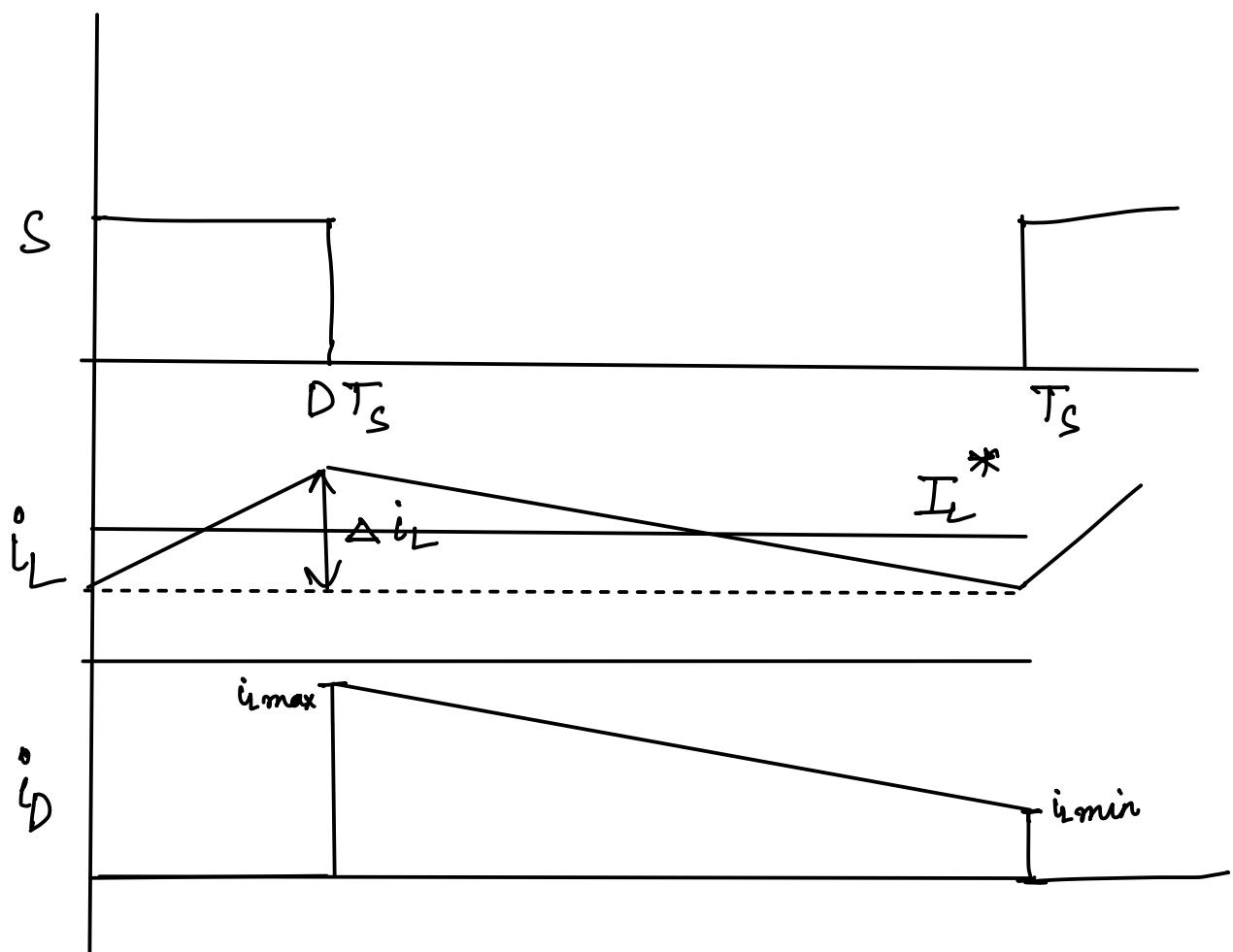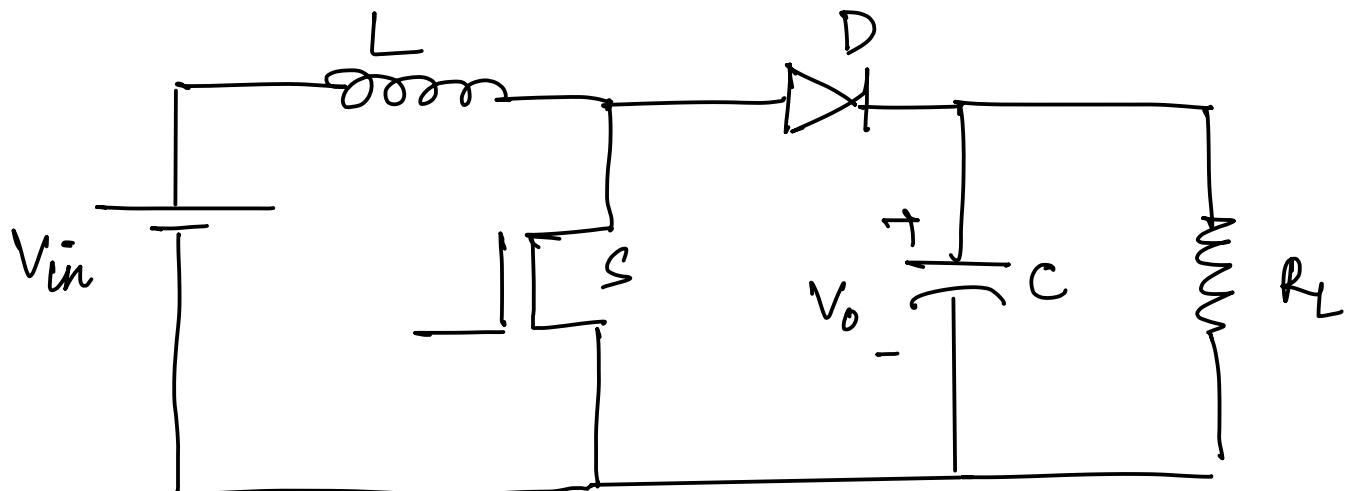

$$\frac{0 \rightarrow DT_S}{V_L = V_{in}^o}$$

$$\frac{DT_S \rightarrow T_S}{V_L = V_{in} - V_0}$$

$$\langle V_L \rangle = 0$$

$$\Rightarrow V_{in}^o (DT_S) + (V_{in} - V_0) T_S (1-D) = 0$$

$$\Rightarrow \cancel{V_{in}^o DT_S} + V_{in} T_S - \cancel{V_{in} DT_S} - V_0 T_S + V_0 DT_S = 0$$

$$\Rightarrow V_{in}^o T_S = V_0 (T_S - DT_S)$$

$$\Rightarrow \boxed{\frac{V_0}{V_{in}^o} = \frac{1}{1-D}}$$

$$\langle i_D \rangle = \frac{V_0}{R_L}$$

$$\langle i_L \rangle = \frac{i_{L\max} + i_{L\min}}{2}$$


$$\Rightarrow \left(\frac{i_{L\max} + i_{L\min}^o}{2} \right) (1-D) = \frac{V_0}{R_L}$$

$$\Rightarrow (1-D) \langle i_L \rangle = \langle i_D \rangle = \frac{V_0}{R_L} = \langle I_o \rangle$$

Ideal Converter \Rightarrow no losses.

$$\Rightarrow \langle V_{in} \rangle \times \langle I_{in} \rangle = V_o \langle I_o \rangle \\ = \langle i \rangle$$

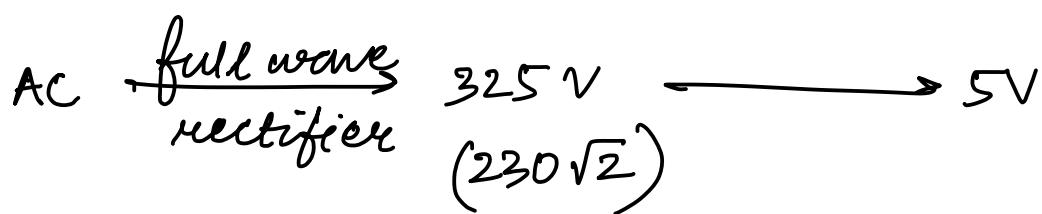CCM and DCM are always defined in context
of inductor current





$$\frac{325}{5} = 65 \text{ times } \downarrow$$

$$\Rightarrow D = \frac{5}{325} = 0.0154$$

$$f_1 = 1 \text{ MHz}$$

$$DT_s = 15.4 \text{ ns}$$

Resolution of PWM is a problem.

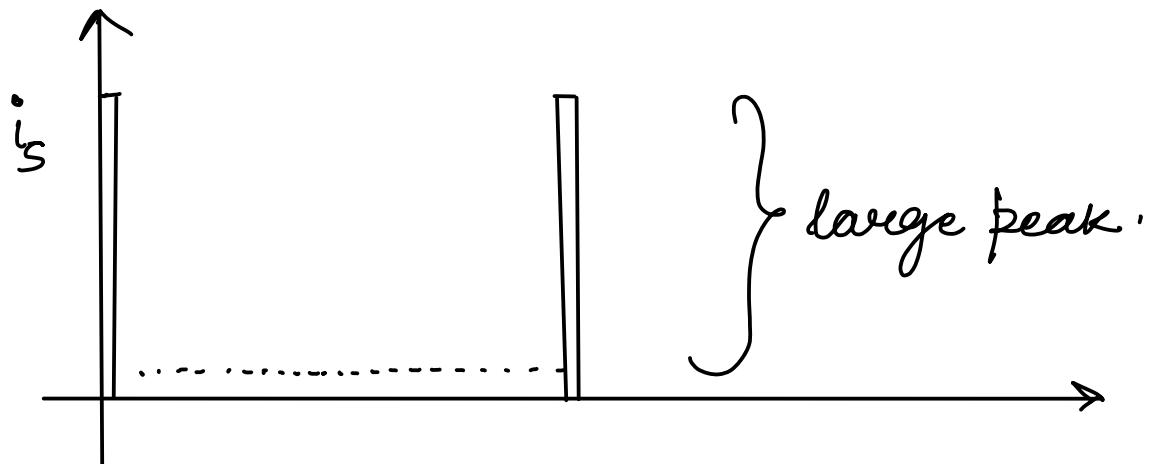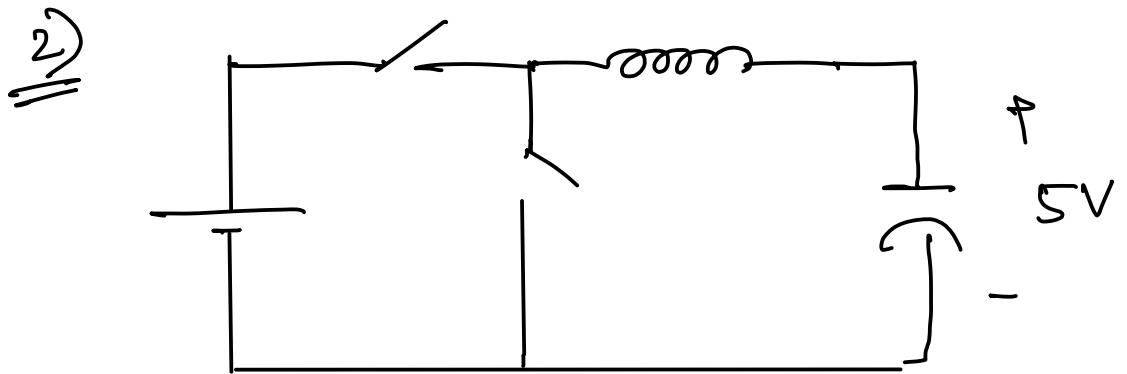

peak current requirement of switch is high
 I_{ams} of switch (semi-conductor) is also high


3) Efficiency reduces $\eta \downarrow$ (heat dissipation \uparrow)

Similar problems with boost converter.

Boost


5V \rightarrow 500V

DC-DC Boost converter: \times

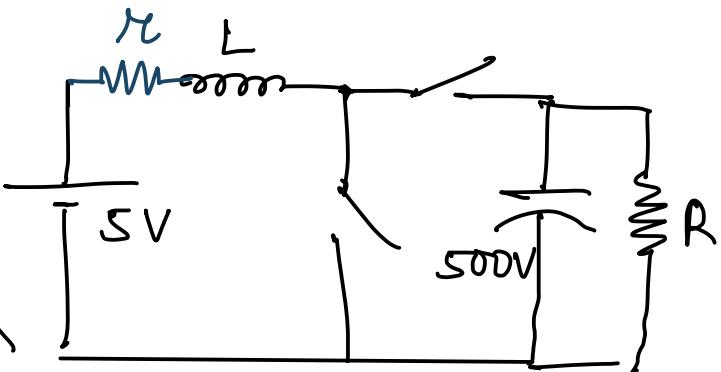

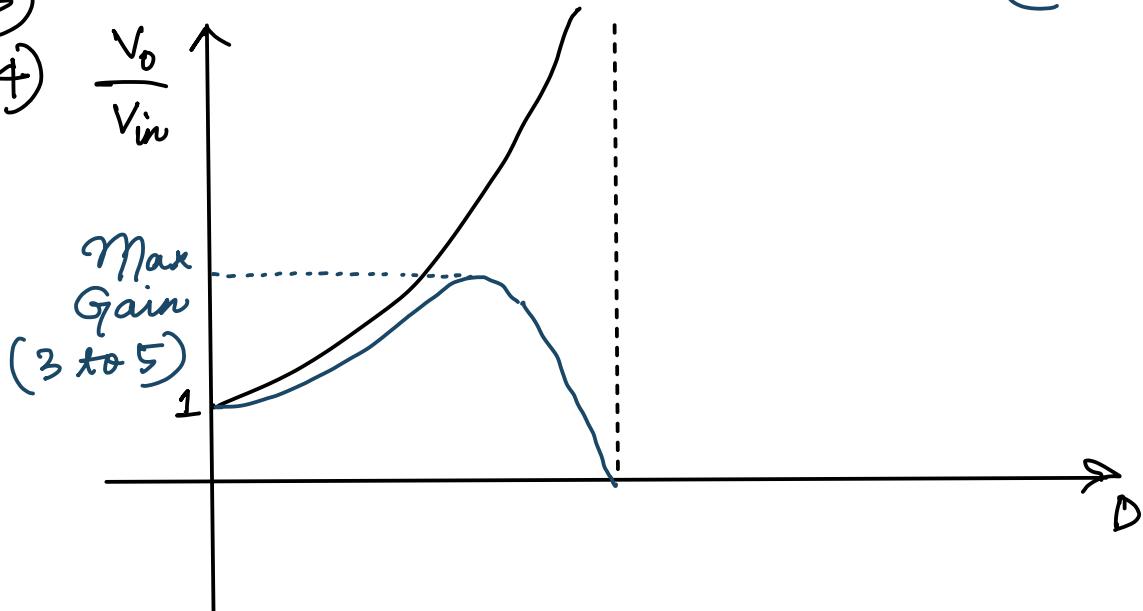- 1)
- 2)
- 3)
- 4)

$$V_o = \frac{V_{in}}{\left[1 - D + \frac{R}{L} \right]}$$



\therefore In real life, gain of boost converter is limited


Solution - 1

1) Use transformer in i/p AC

$$E = 4.44 N f \Phi_m$$

Very big, flux $\uparrow \uparrow$


2) High frequency transformer

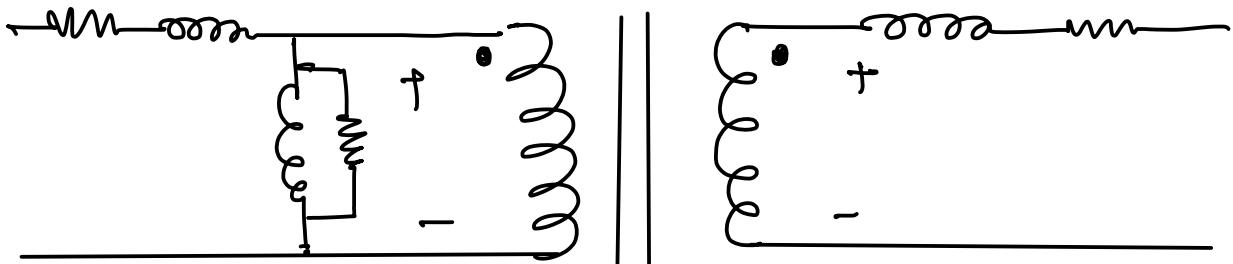


Ideal

Flyback Converter

s on
S off

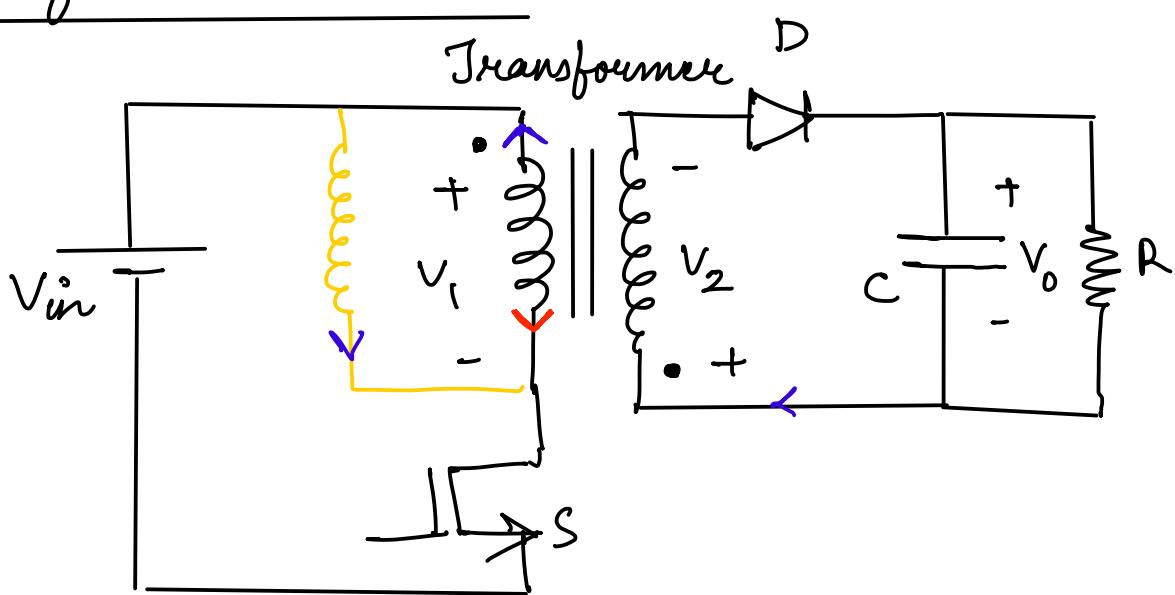


$$V_D = -V_2 - V_0$$

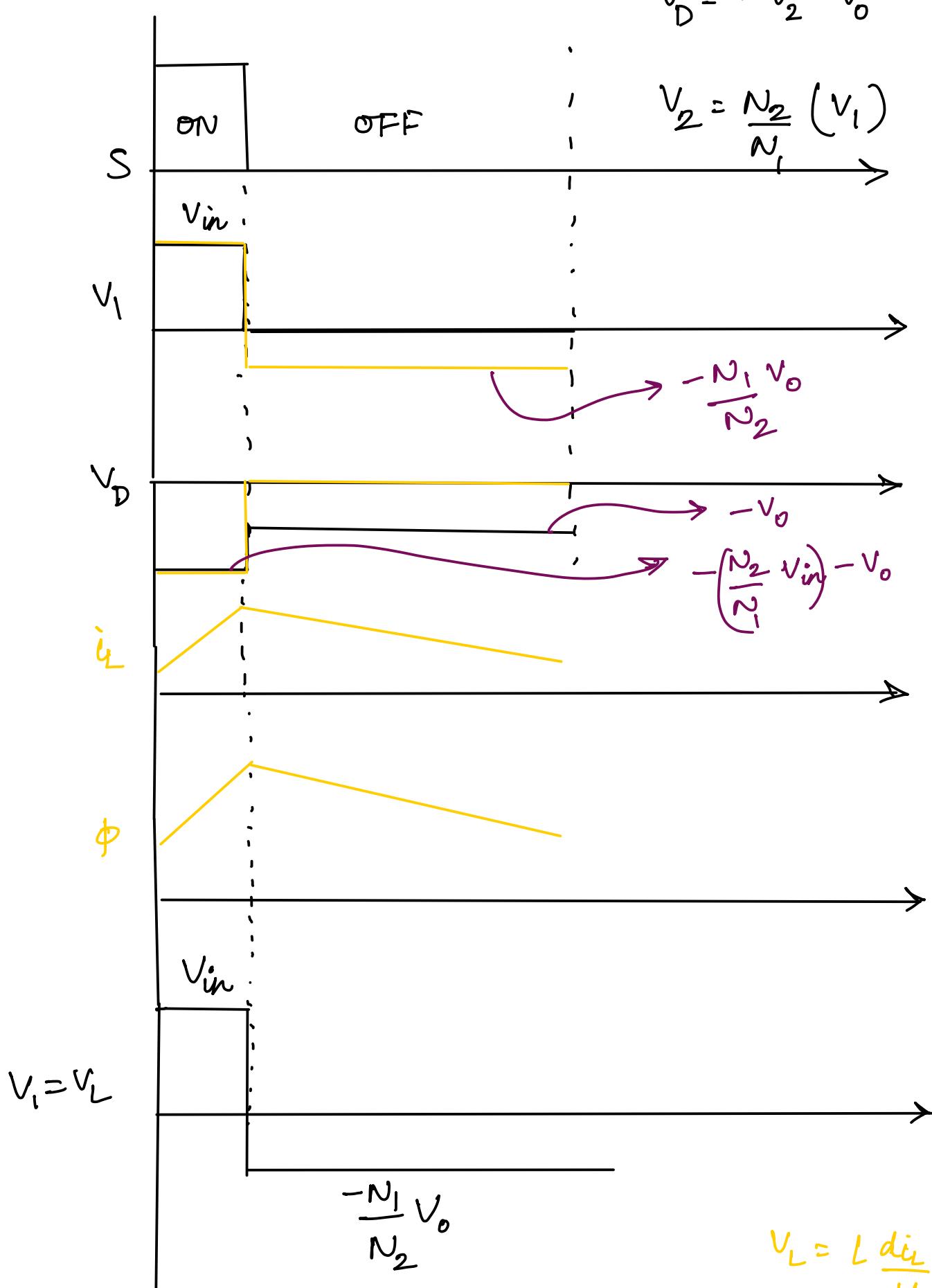

$$V_L = L \frac{di_L}{dt}$$

$$= N_1 \frac{d\phi}{dt}$$

$$\frac{Li_L}{N} = \phi$$

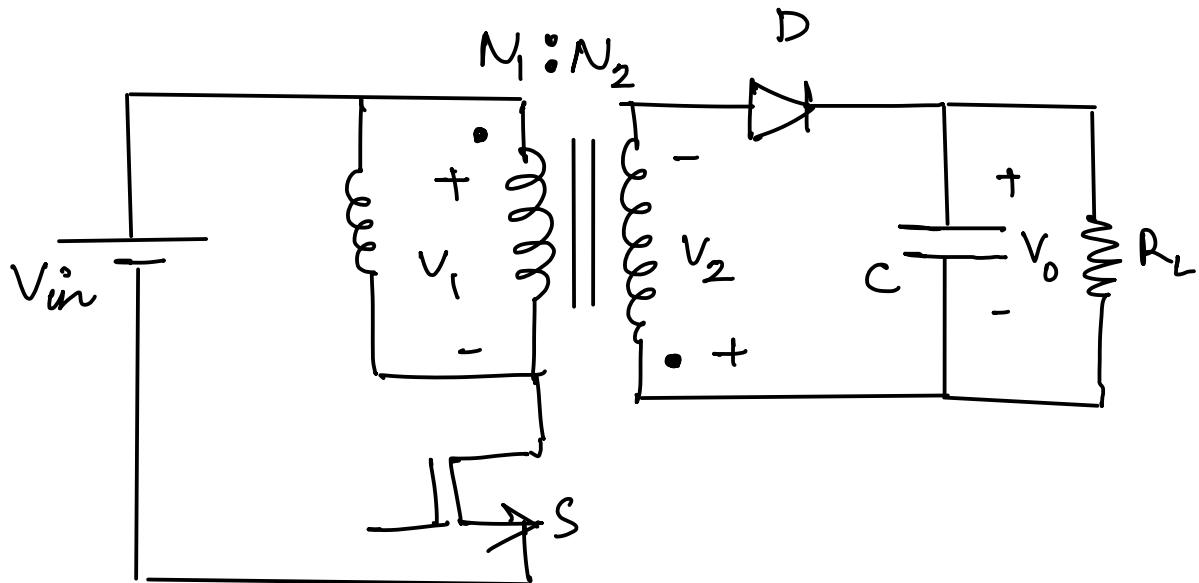



$$\text{Apply } \int_{0}^{T_s} v_L dt = 0 \quad (\text{voltage second balance})$$

$$\Rightarrow \int_{0}^{T_s} v_1 dt = 0$$

$$\Rightarrow V_{in} (D T_s) - \frac{N_1}{N_2} V_o (1-D) T_s = 0$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = \frac{N_2}{N_1} \frac{D}{(1-D)}}$$

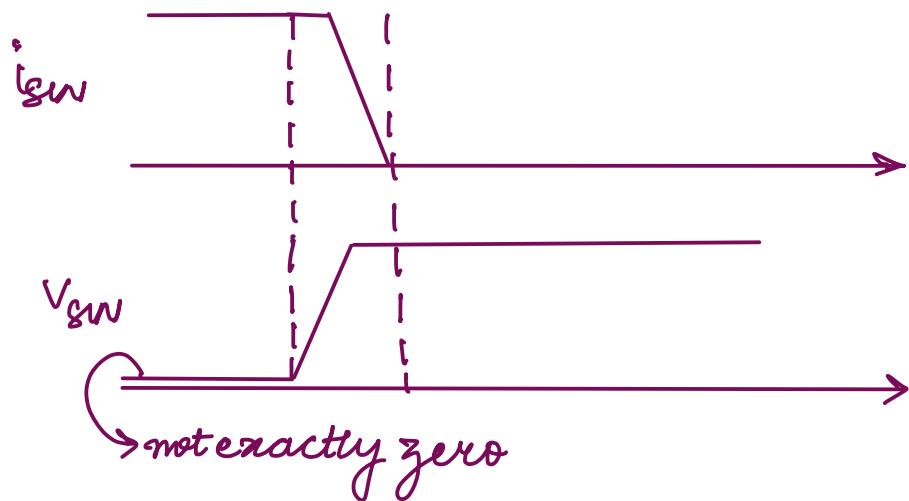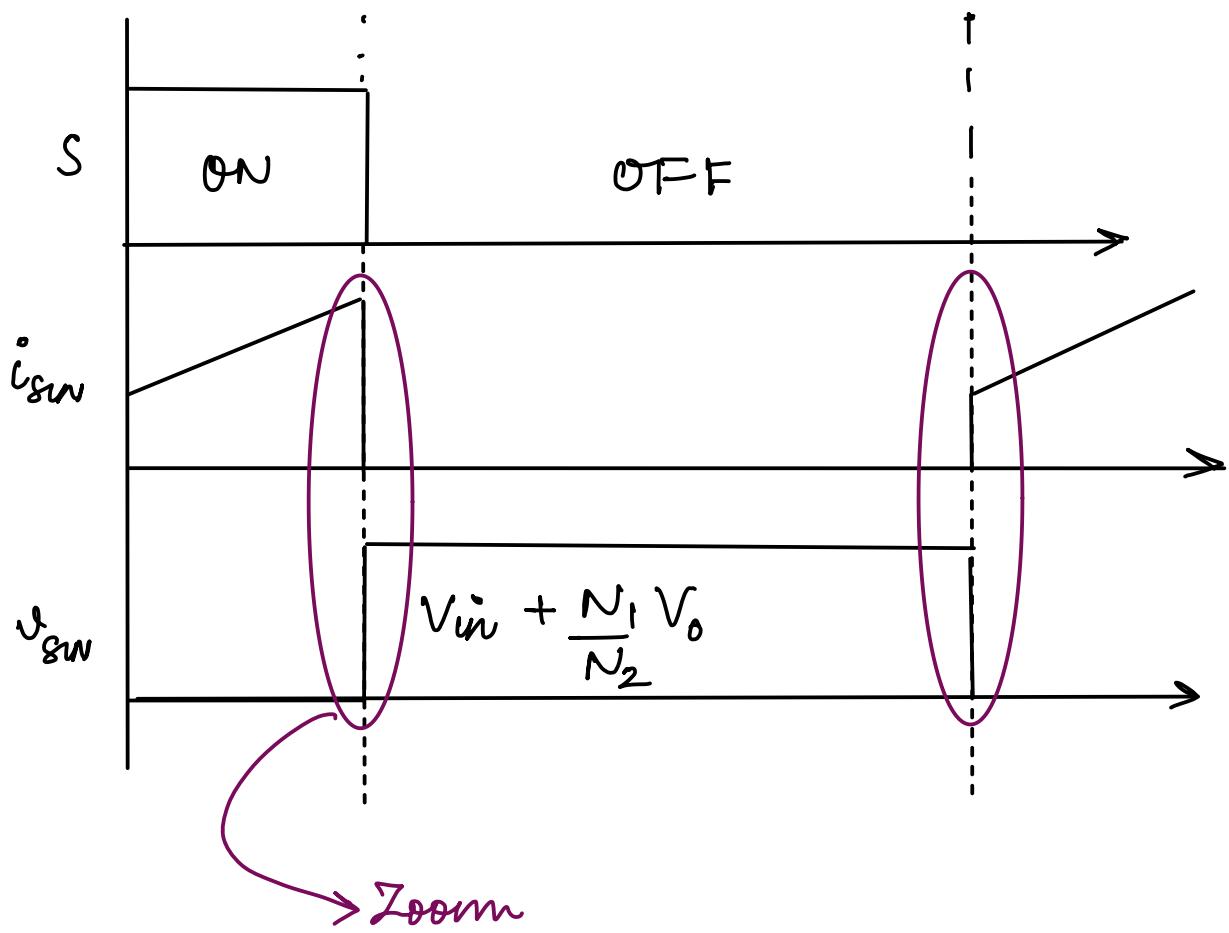In DCM, V_o has to $\uparrow\uparrow$ to keep $v_{avg} = 0$ since the second half will shrink.



Switch is on :

$$1) \text{ Conduction loss : } \frac{1}{T} \int v_{sw} i_{sw} dt$$

Switch is off :

2) Very small leakage current \Rightarrow Negligible loss

Switch in transition period :

- 3) Switching loss (larger than conduction loss)
↳ depends directly on switching frequency
(In diode → reverse recovery losses)

Inductore Loss / Transformer loss

→ Conduction loss

→ Core loss


These are the predominant losses

Basic details which define a MOSFET.

- Blocking Voltage (A buffer of 40-50% over max voltage is kept)
- Peak current
- Continuous Current (RMS current)
 - ↳ Maybe thermal constraints


Advantages of flyback

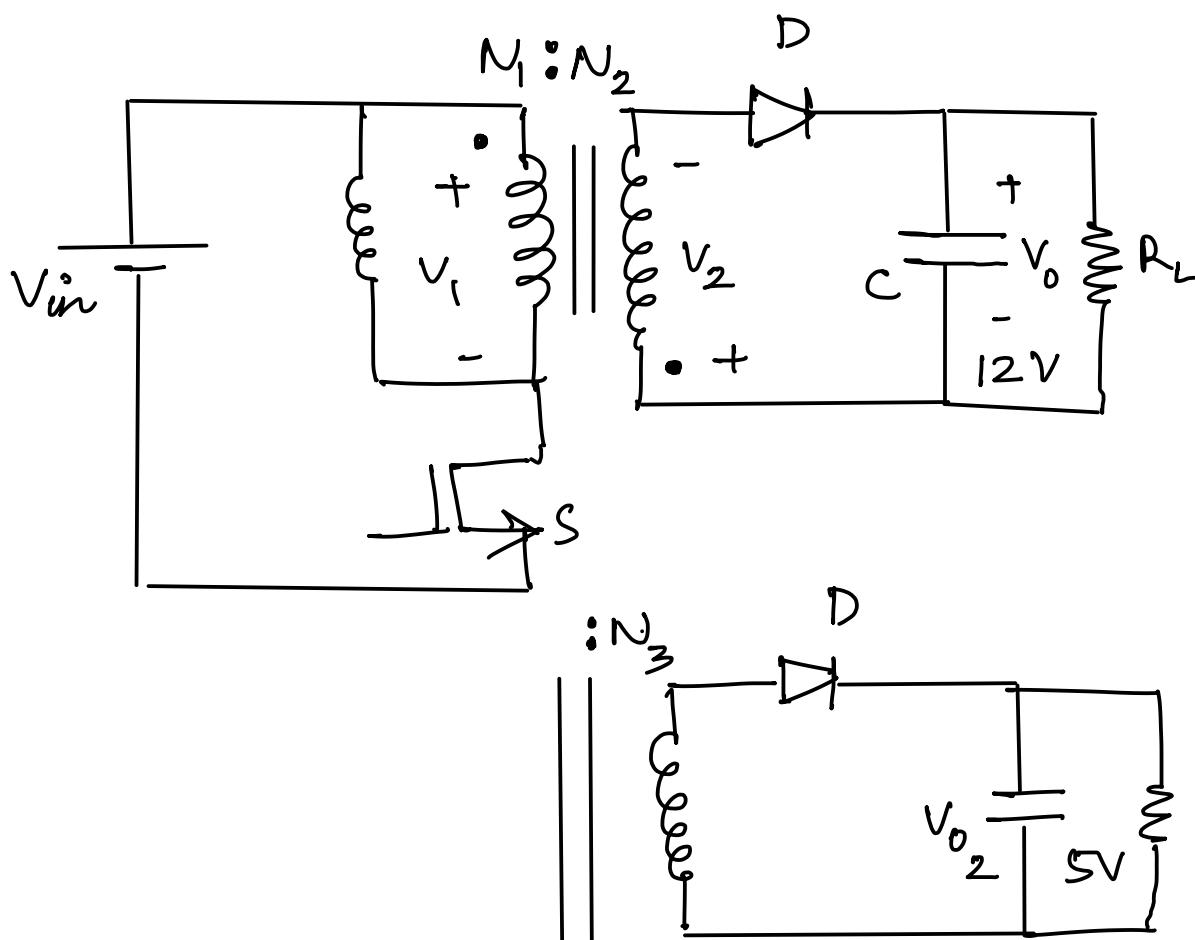- Can vary turns ratio for large attenuation.
- No stress on duty cycle.




$$\frac{12}{5} = \frac{N_2}{N_3}$$

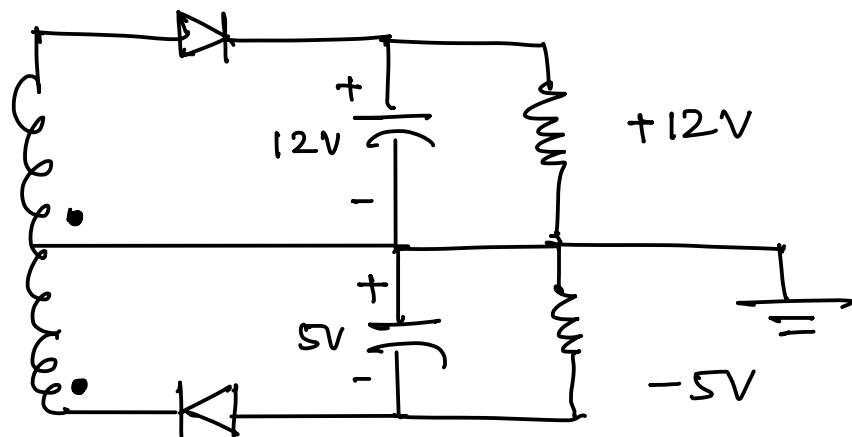Can use a tapped transformer here as well.




Limitations of flyback

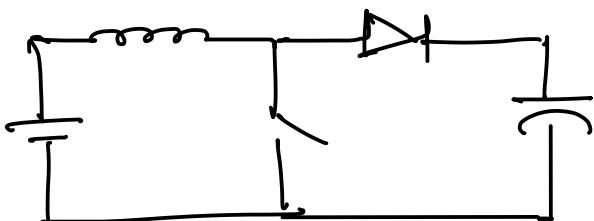
- 1) Output Ripple Voltage .
- 2) Large $L_m \Rightarrow$ Small Energy Transfer .
- 3)



Boost

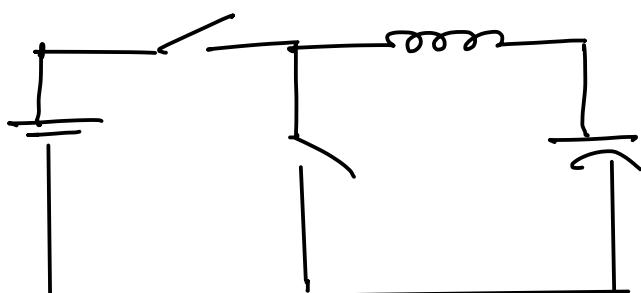


Buck

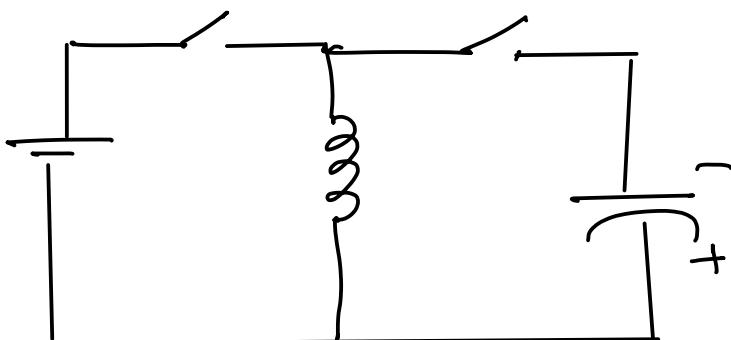

Buck - Boost
(Large ripple current at both i/p & o/p)

Forward Converter (Buck Derived)

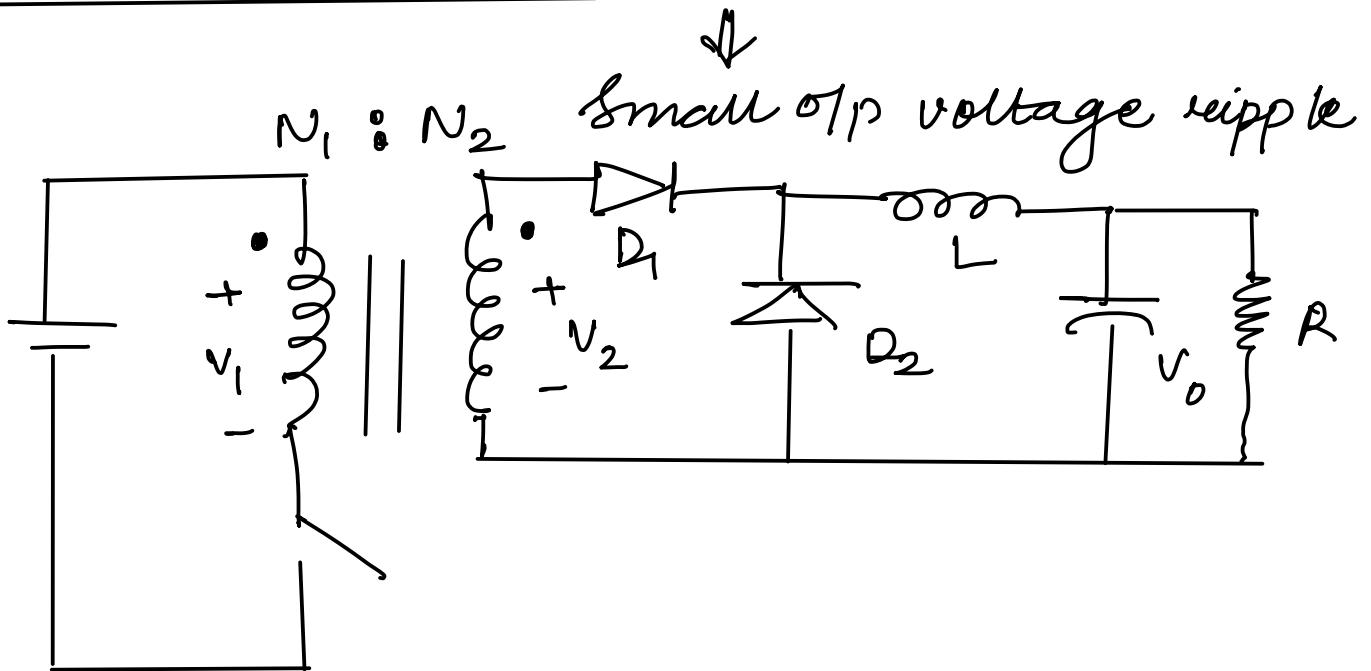


When S is on

$$V_1 = V_{in} \Rightarrow V_2 = \frac{V_{in} N_2}{N_1}$$

$V_2 > 0 \Rightarrow D_1$ conducts, D_2 remains reverse biased

⇒ Eq circuit on right side ⇒

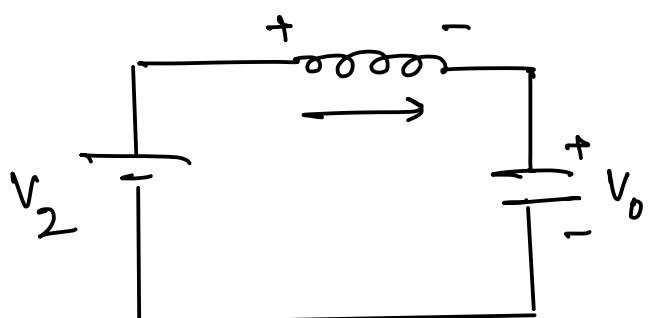

$$\frac{dV_2}{dt} = V_2 - V_0 = \frac{V_{in} N_2}{N_1} - V_0$$

S is off


Inductor current has two possibilities, then D₁ or D₂

Consider D₁

- ⇒ Current is leaving the dot on right side
- ⇒ Current will have to enter the dot on left side
- ⇒ Not possible

∴ D₂ conducts

$$V_L = \frac{L di_L}{dt} = -V_o$$

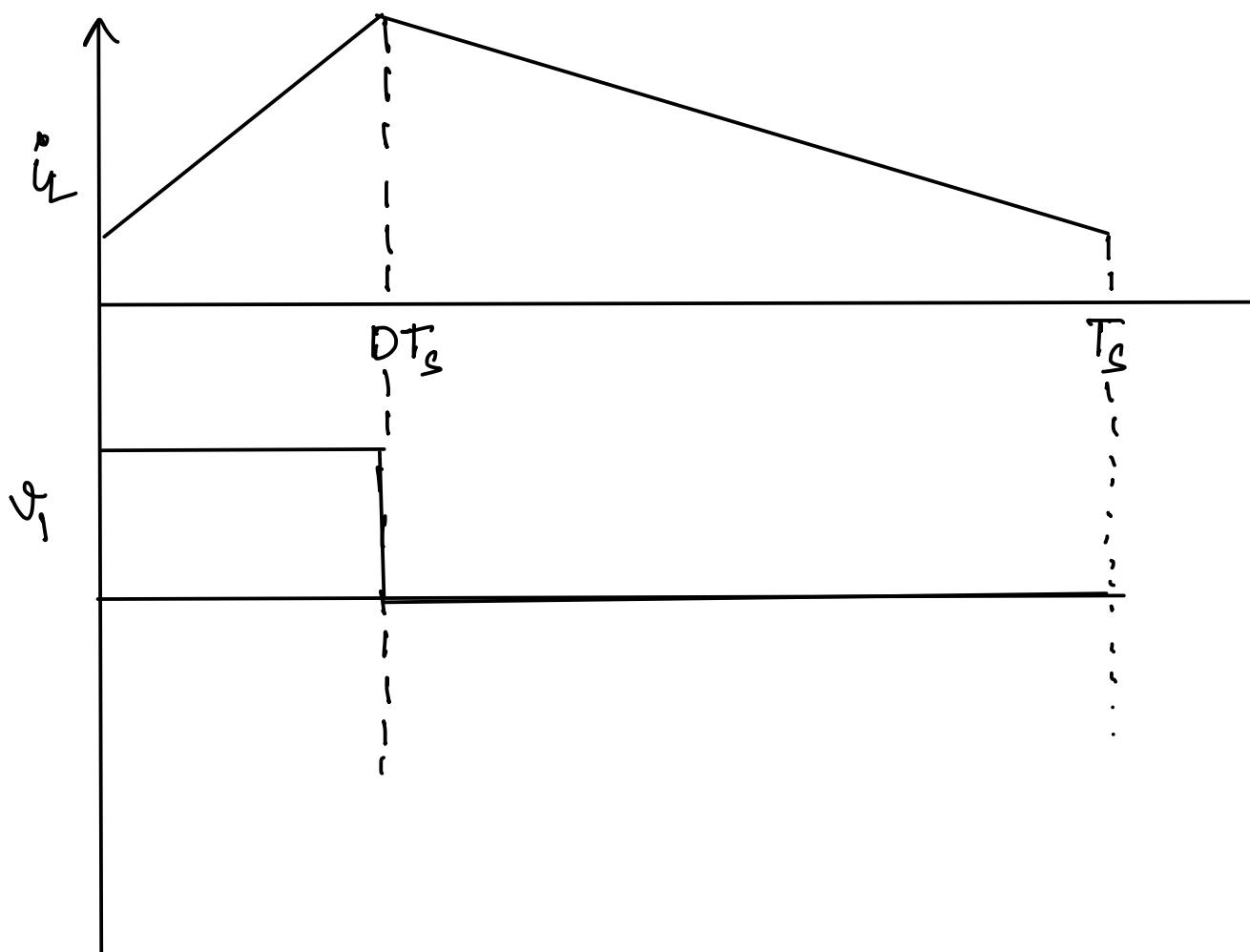



$$V_o = D V_{in} \frac{N_2}{N_1}$$

Although it is buck derived, we can still get a gain ($\frac{N_2}{N_1} \uparrow\uparrow$)

$$\Rightarrow V_o \gtrsim V_{in}$$

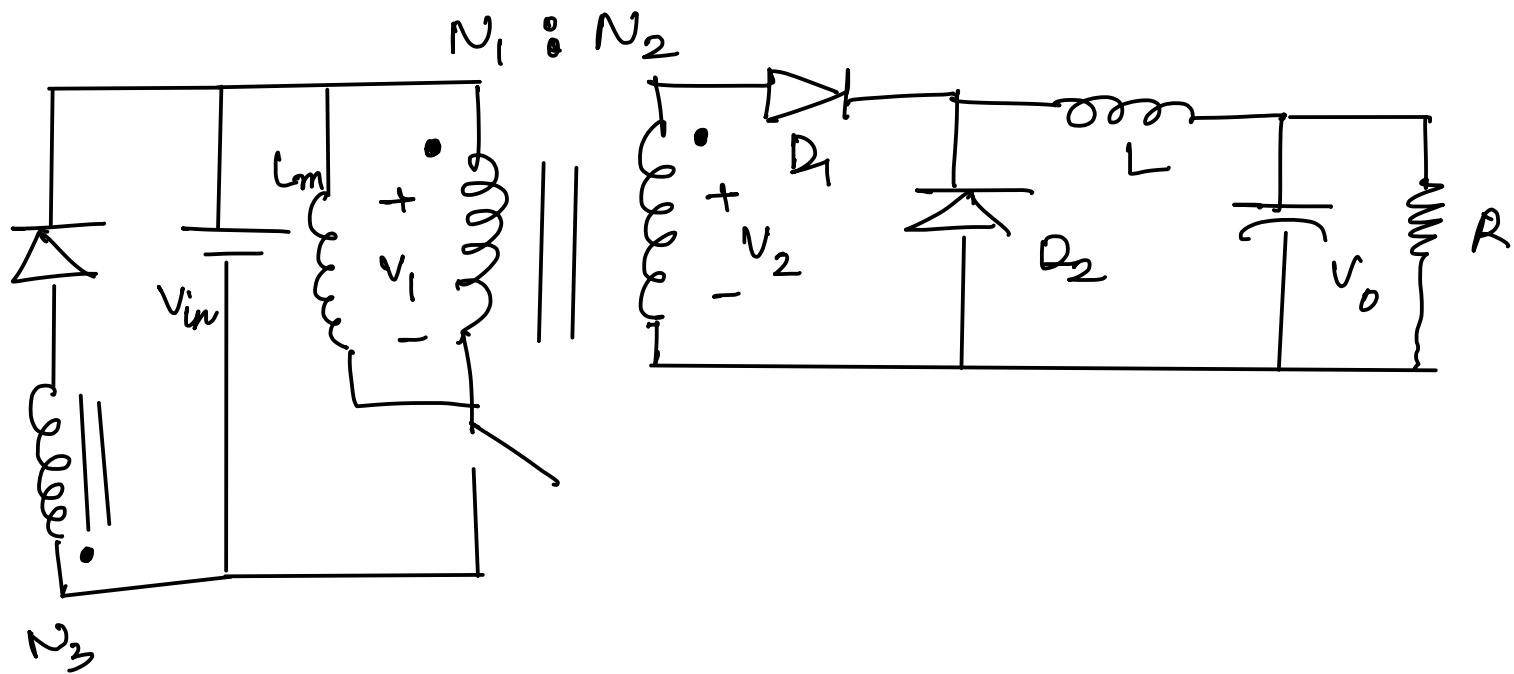Here V_i wrong value $> 0 \Rightarrow$ transformer flux will keep on rising \Rightarrow current rises exponentially.
 \therefore This circuit can't work in practical conditions



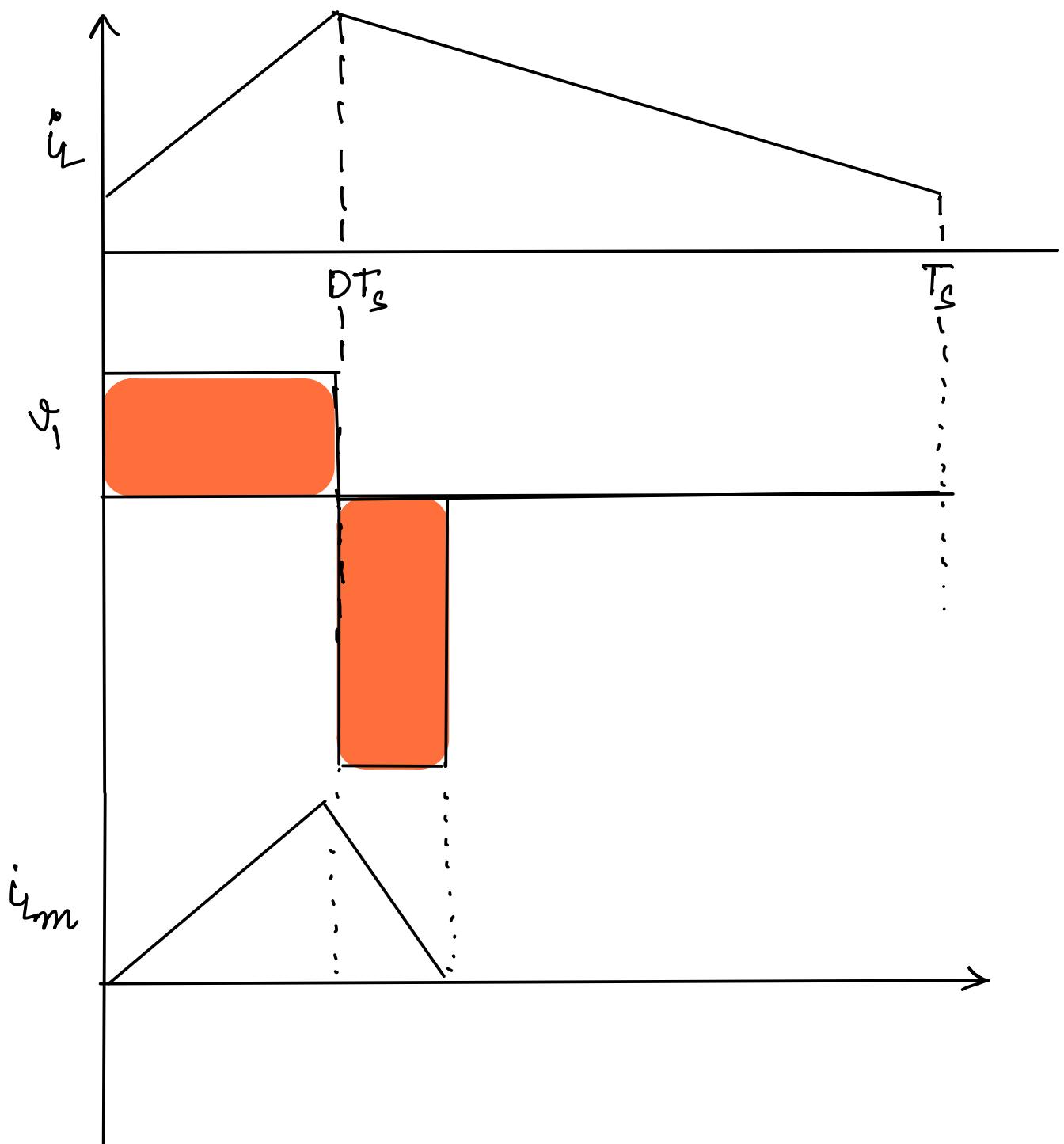

S_{off}

$$V_3 = V_1 \times \frac{N_3}{N_1}$$




$$V_3 + V_{in} = 0$$

$$V_3 = -V_{in}$$

$$V_1 = \frac{-N_1}{N_3} V_{in}$$


Fourier Series Revision

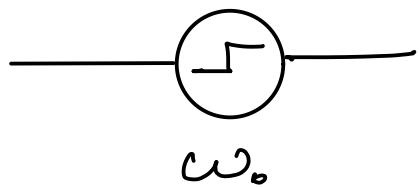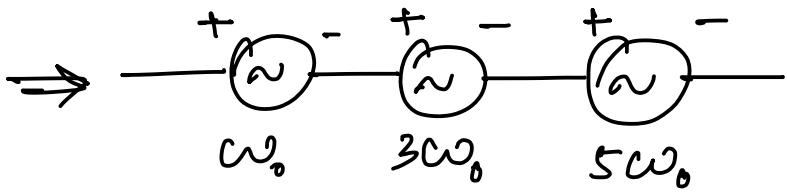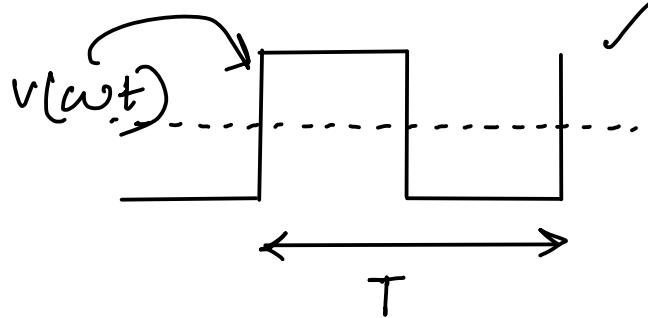half wave symmetric
 $f(\omega t) = -f(-\omega t)$



$$f(x) = -f(x + \frac{T}{2})$$

fundamental frequency

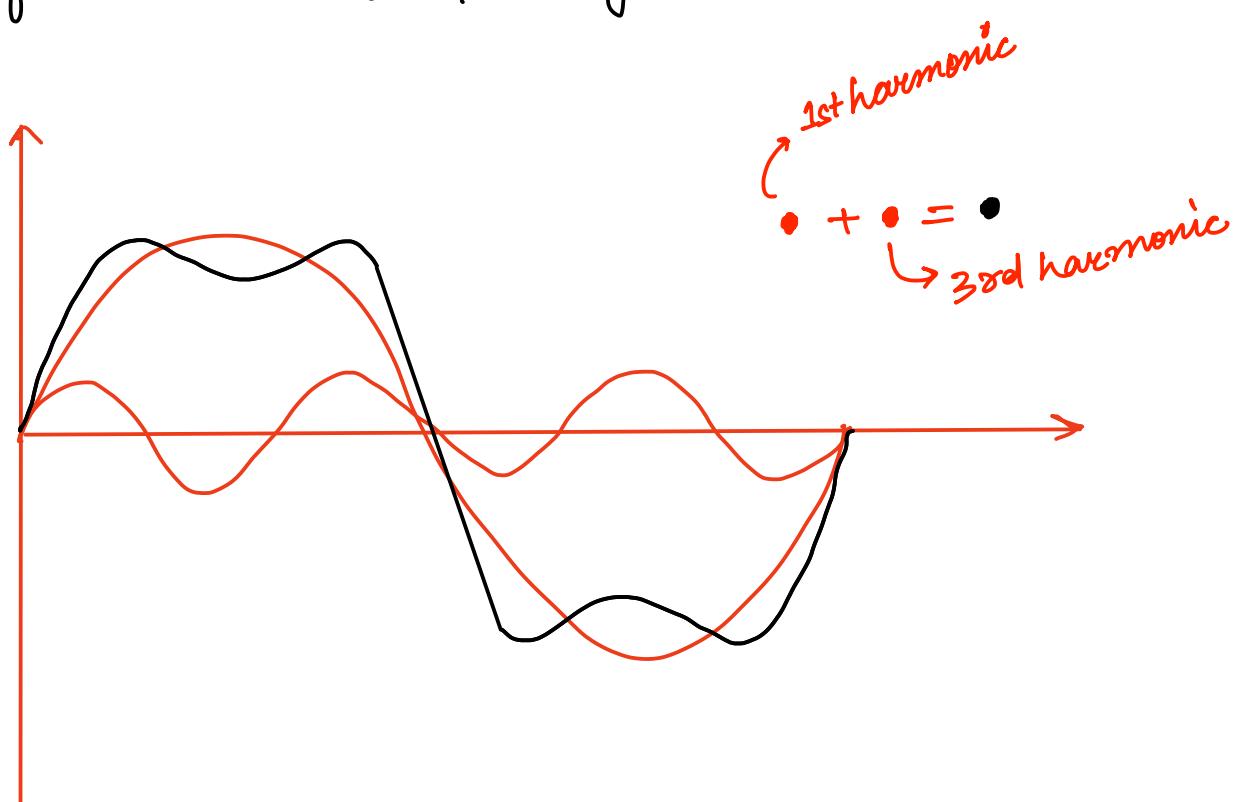

$$v(\omega t) = \left(\frac{1}{2}a_0\right) + \sum_{n=1}^{\infty} a_n \cos(\omega_0 n t) + \sum_{n=1}^{\infty} b_n \sin(\omega_0 n t)$$

$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} v(\omega t) \cos(n\theta) d\theta \stackrel{L}{=} 0$$

$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} v(\theta) \sin(n\theta) d\theta$$

$$a_0 = \frac{1}{\pi} \int_{-\pi}^{\pi} v(\theta) d\theta$$

$a_0 \rightarrow$ avg dc value.

There is no j anywhere here because the waveform is real.

$$V_{\text{rms}}^2 = V_1^{\text{rms}^2} + V_2^{\text{rms}^2} + V_3^{\text{rms}^2} + \dots + V_{dc}^{\text{rms}^2}$$


Total Harmonic Distortion (THD)

$$\text{THD} = \sqrt{V_2^{\text{rms}^2} + V_3^{\text{rms}^2} + \dots}$$


(can be greater than 1)

For a pure sine wave, THD = 0%
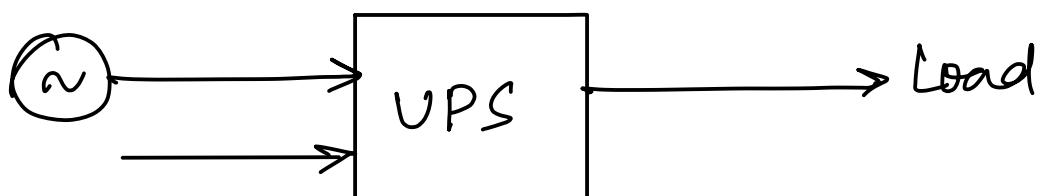
$$\begin{aligned} V_{\text{rms}}^2 &= V_1^{\text{rms}^2} \\ &\quad - V_{dc}^{\text{rms}^2} \end{aligned}$$


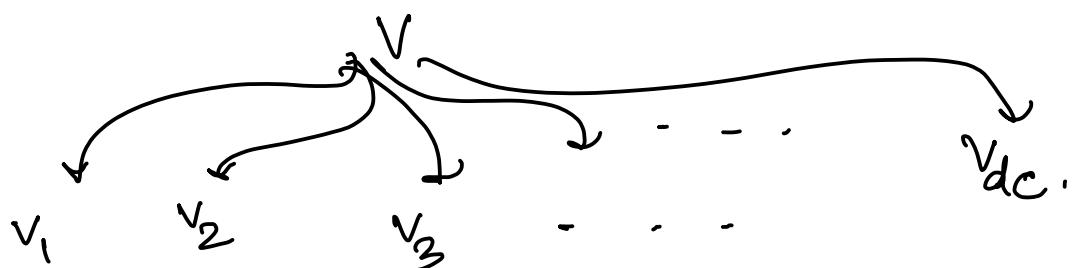
$$V_2^{\text{rms}} = \sqrt{\left(\frac{a_2}{\sqrt{2}}\right)^2 + \left(\frac{b_2}{\sqrt{2}}\right)^2}$$




$$V_{dc} = \frac{v_{cl0}}{2}$$

$$V_1 = a_1 \cos(\omega_0 t) + b_1 \sin(\omega_0 t)$$


$$V_2 = a_2 \cos(2\omega_0 t) + b_2 \sin(2\omega_0 t)$$
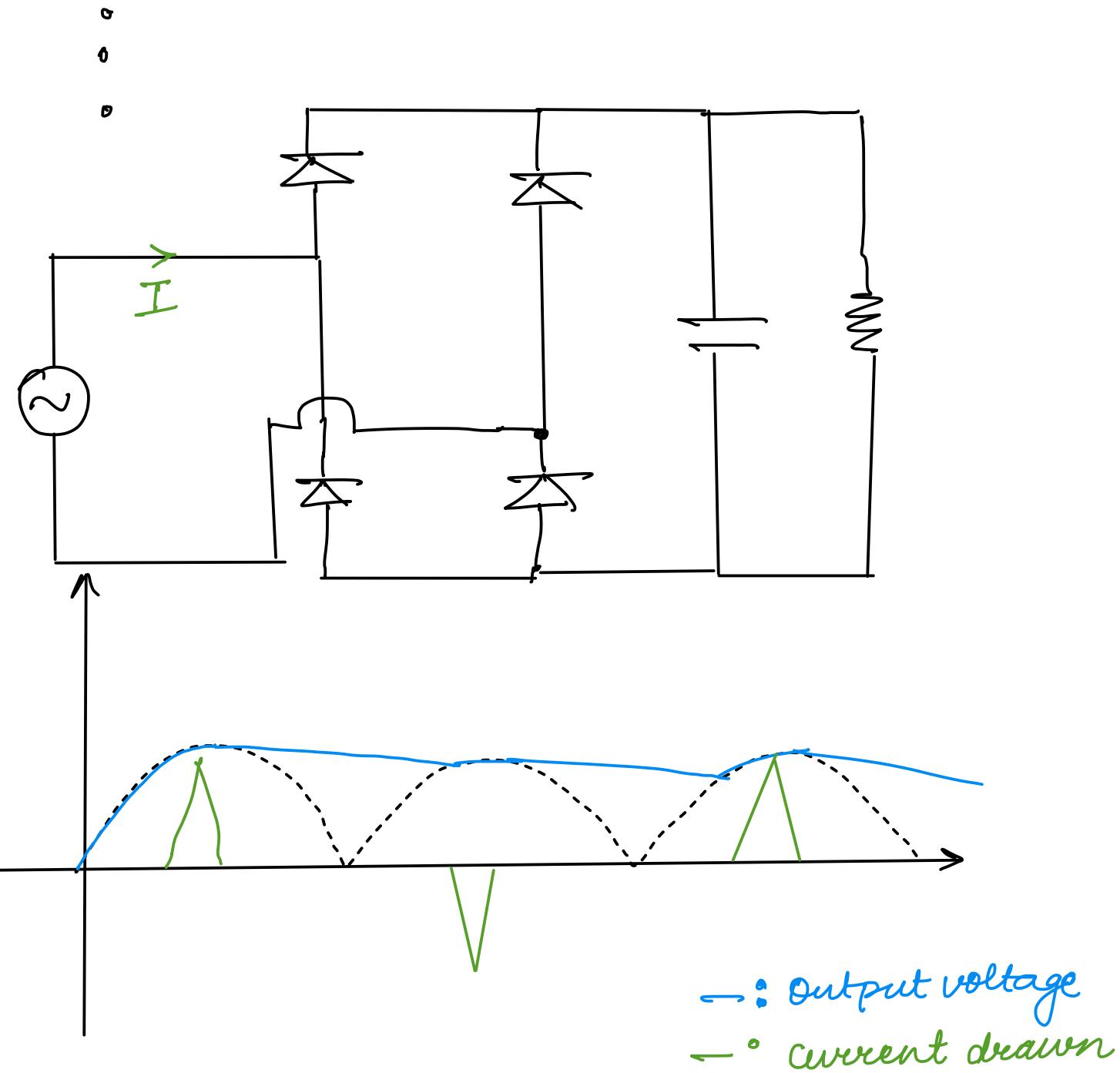
$$V_3 = a_3 \sin(3\omega_0 t) + b_3 \sin(3\omega_0 t)$$



I is half wave symmetric \therefore Grid rarely contains even harmonics.


Inverters (aka DC-AC)

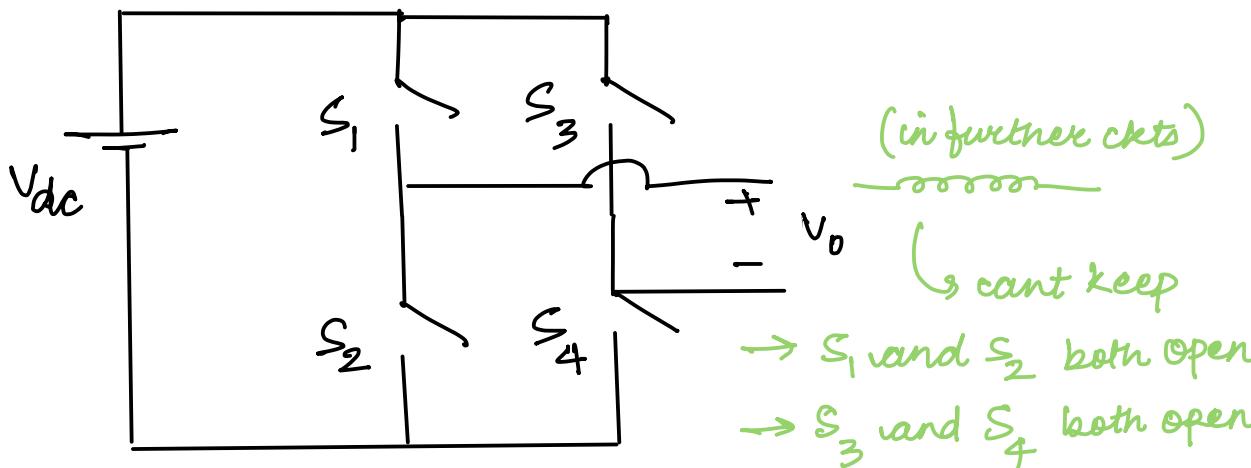

1 ϕ inverter
 H-bridge inverter or full bridge inverter

S_1	S_2	S_3	S_4	v_o	
1	0	1	0	0	←
1	0	0	1	V_{dc}	Zero states
0	1	1	0	$-V_{dc}$	
0	1	0	1	0	←

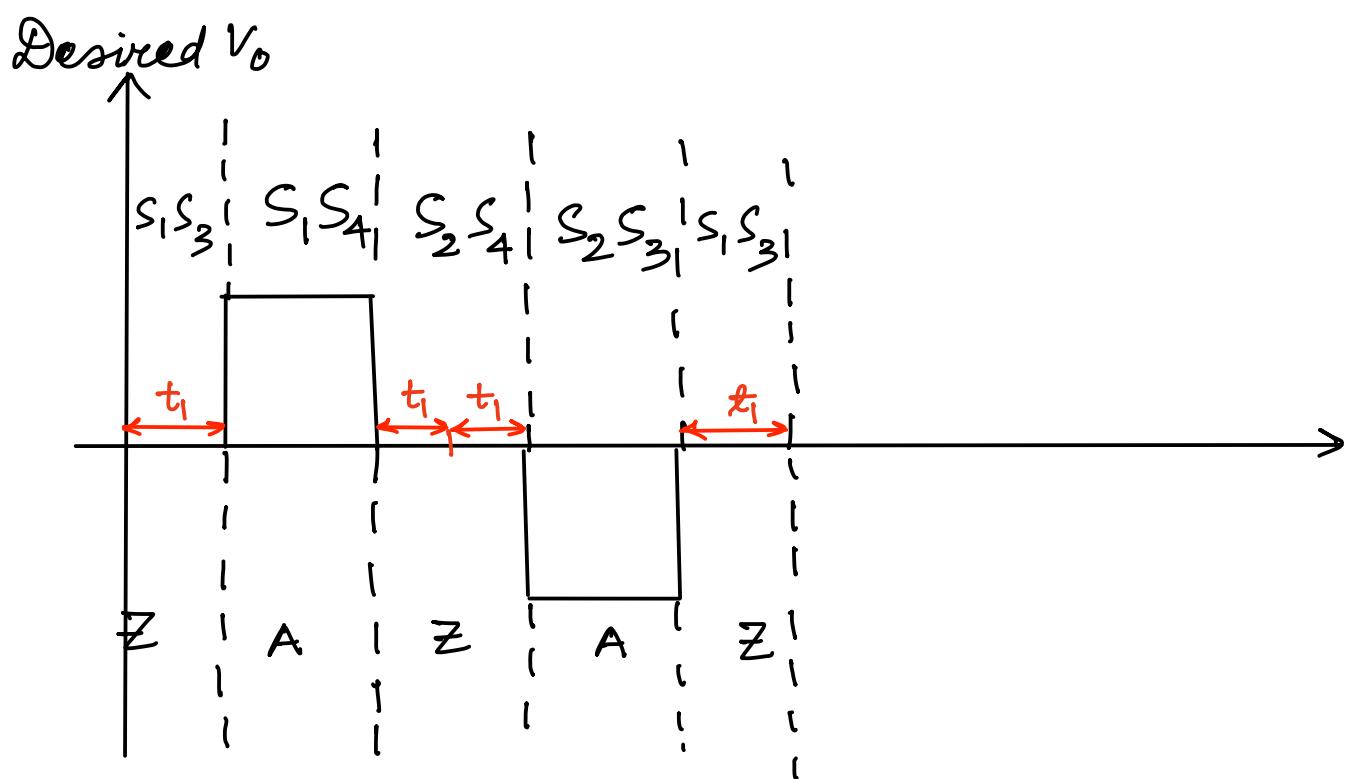S_1 S_2 S_3 S_4 combos \rightarrow popularly called states



If we use say only S_1, S_3 as zero state, RMS current ↑↑ and too much load on S_1, S_3
 (We try to divide the conduction losses)

To change the magnitude ($V_{o\text{rms}}$), change the width of states.

$$V_{o\text{rms max}} = V_{dc}$$

$V_{o\text{rms}} \leq V_{dc}$

Q Why is the waveform drawn to be so symmetric?

Ans: To keep half wave symmetry and eliminate the even frequencies.

(we want as less harmonics as possible)


Say we use this inverter to power an induction motor. It would draw some fundamental current and harmonic currents and the motor will not work as smoothly as we want.

Pure sinusoid would have created a rotating flux field perfectly, but now these harmonics mess up a bit with the rotating flux field.


So why not at least eliminate the even harmonics :)

Keeping the midway symmetry also reduces fundamental frequency r.m.s -

Half Bridge

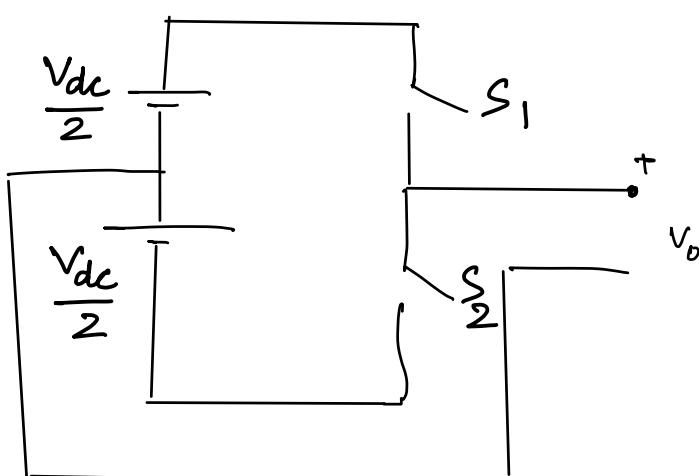


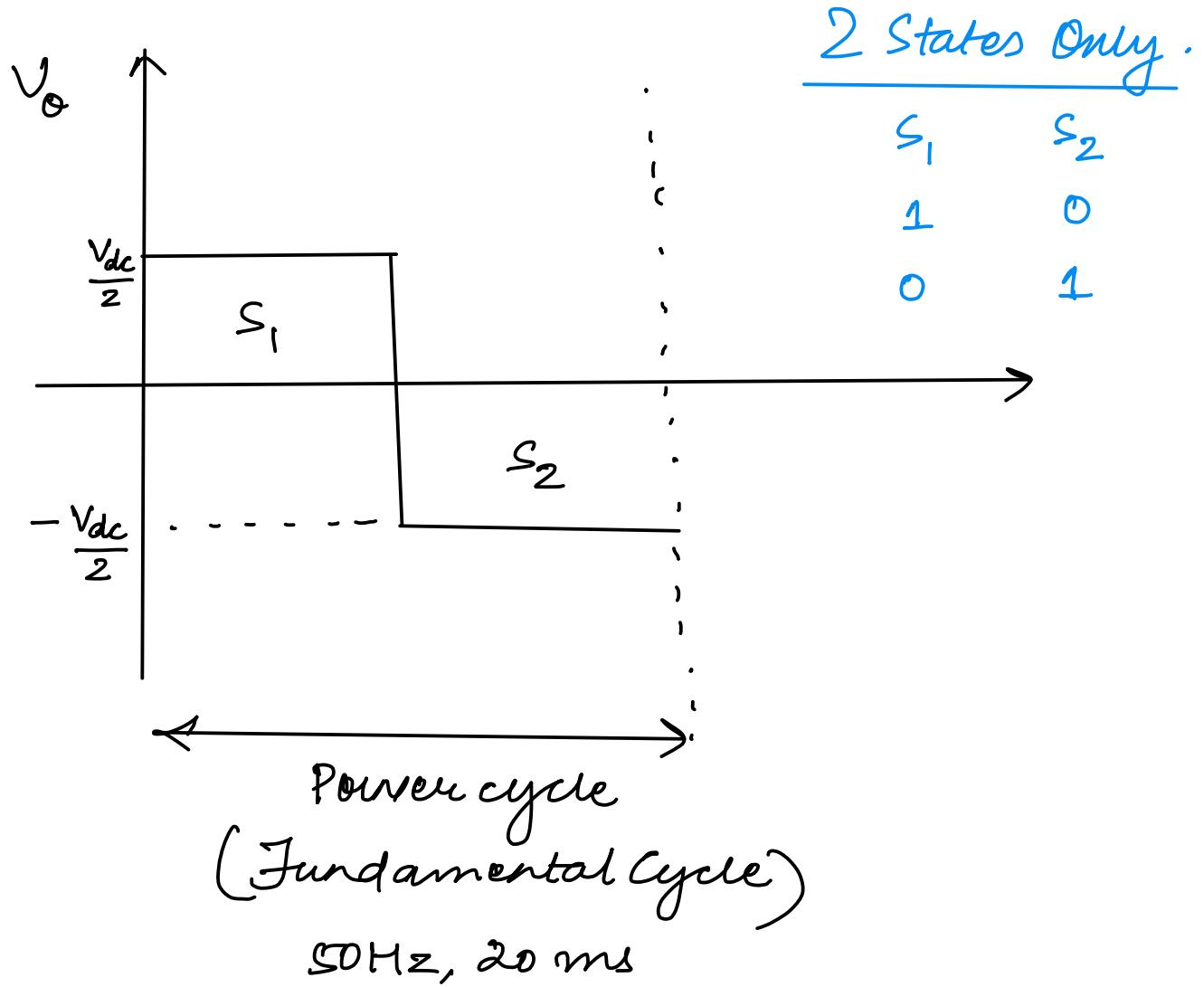Here $V_{\text{rms}} = \frac{V_{\text{dc}}}{2}$ (non-adjustable)




What we have looked at till now \Rightarrow fundamental modulation

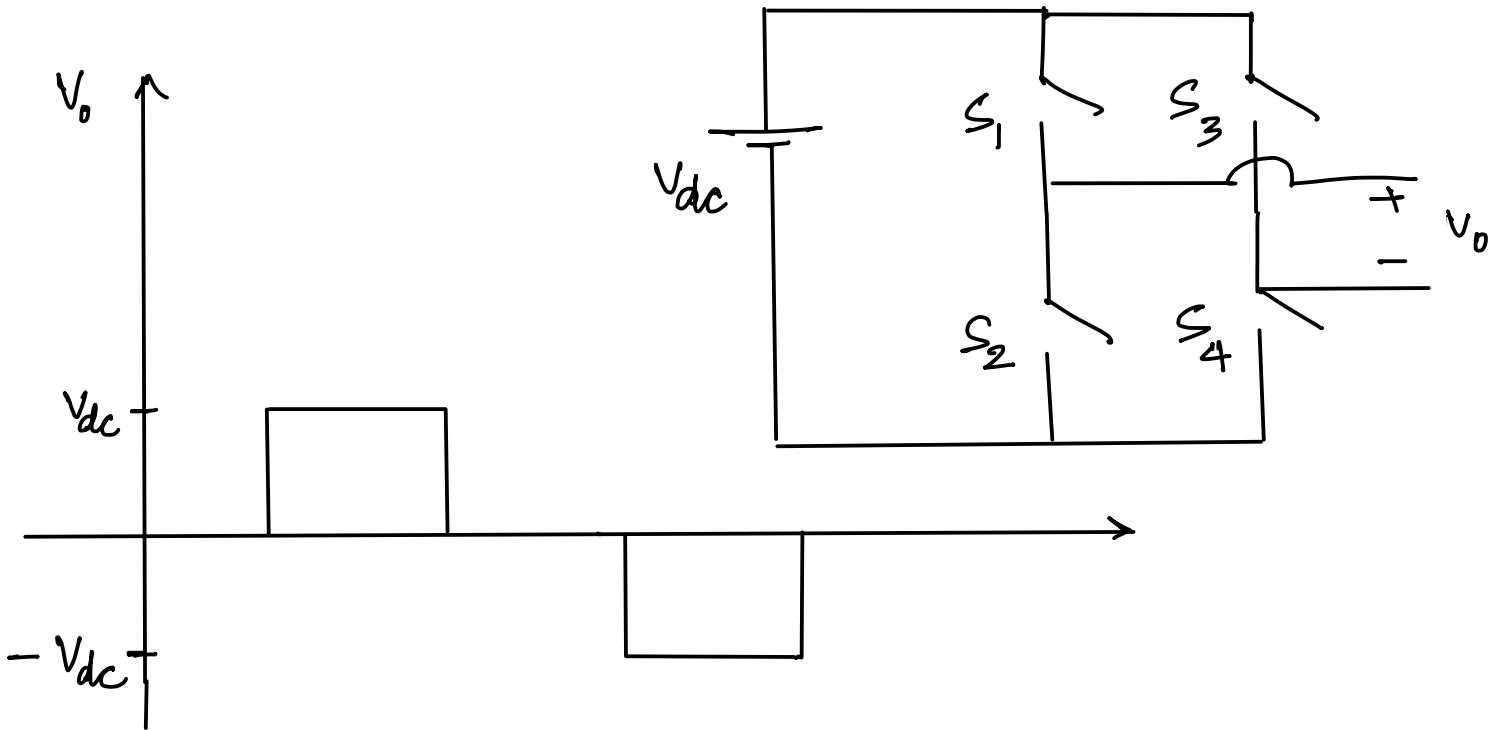Each switch is switched only once in power cycle -



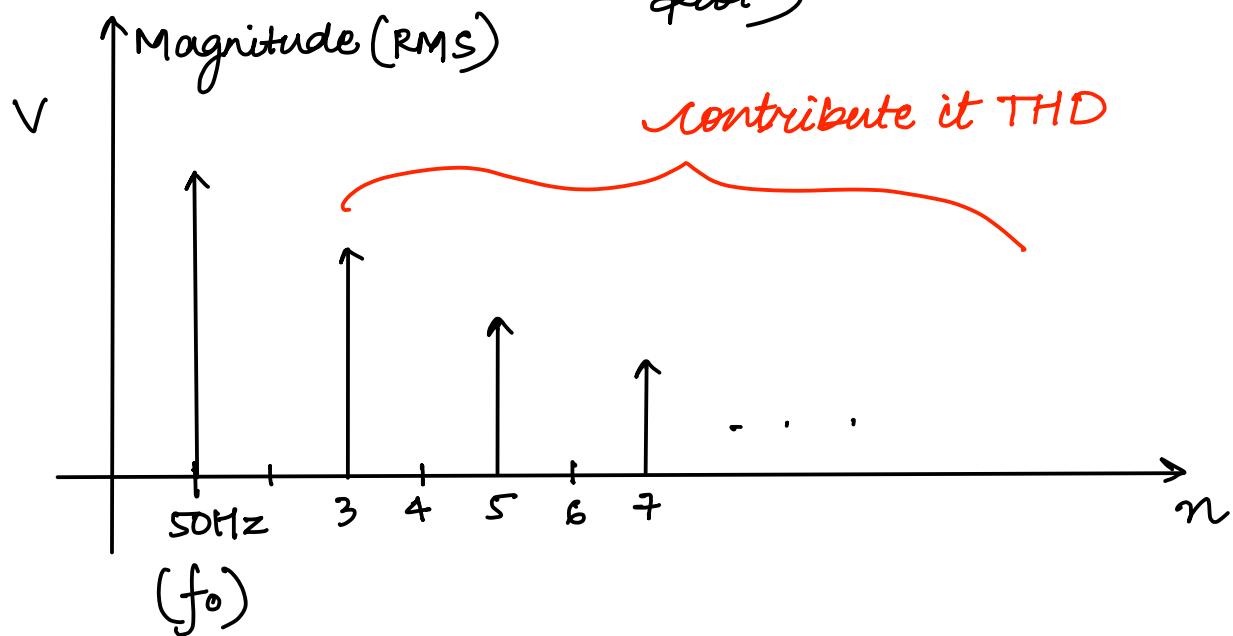Frequency Spectrum (Find fourier series and then plot)



$$\text{THD} = \frac{\sqrt{\sum_{i=2}^{\infty} V_i^2}}{V_1} = \frac{\sqrt{\sum_{i=2}^{50} V_i^2}}{V_1}$$

(standard)


Problems with THD:

- Oscillatory torque in motors
- Less utilisation of cables/wires

$$I^{RMS} = \sqrt{I_1^2 + I_2^2 + I_3^2 + \dots}$$


unnecessary.

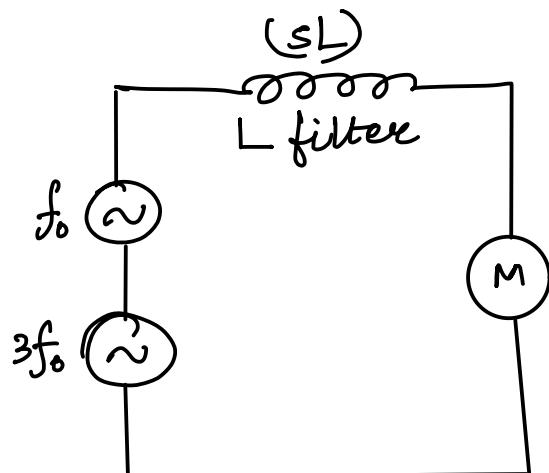- Losses (Harmonic currents causes additional losses) leading to heating of cables, motors, transformer
- Resonance (Some harmonic may excite LC component due to resonance)
- Interference (to other appliances)
 - Because wire is acting kinda like an antenna (due to high frequency components)




$$\bar{I} = \frac{\bar{V}}{sL}$$

$$H(s) = \frac{1}{sL}$$

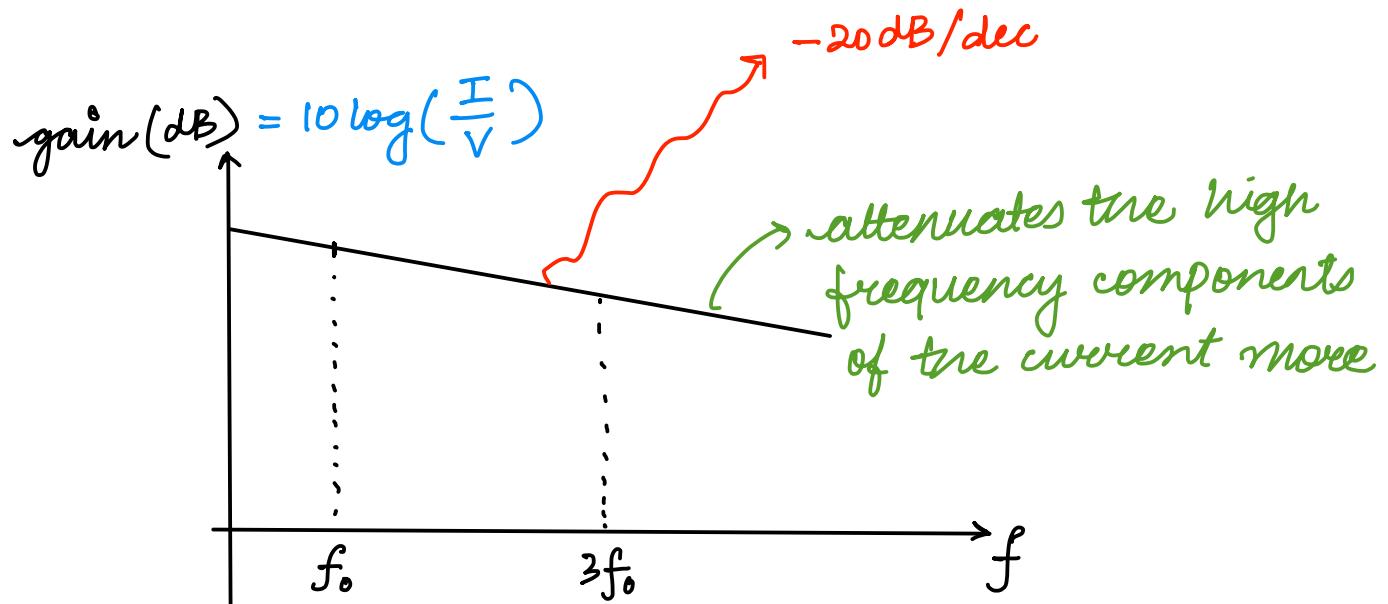


Using this inductor reduces THD in current as compared to THD in voltage.

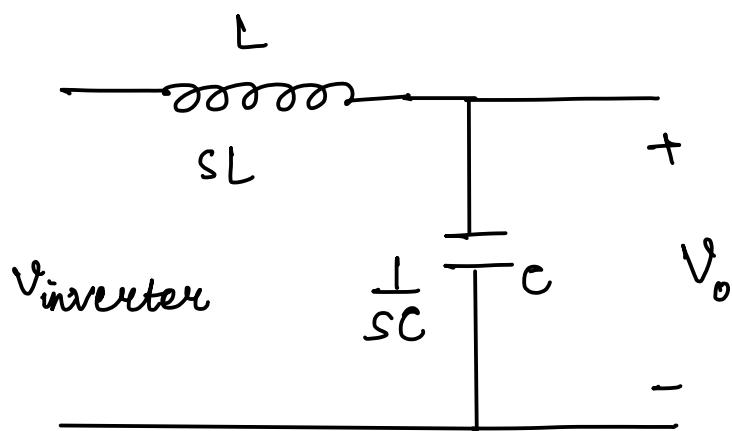(Say voltage has 50% distortion, this L filter would cause current distortion to be < 50%)




$$V_o = \frac{V_{\text{in}}}{sL + \frac{1}{sC}} \times \frac{1}{sC} = \frac{V_{\text{in}}}{s^2 LC + 1}$$
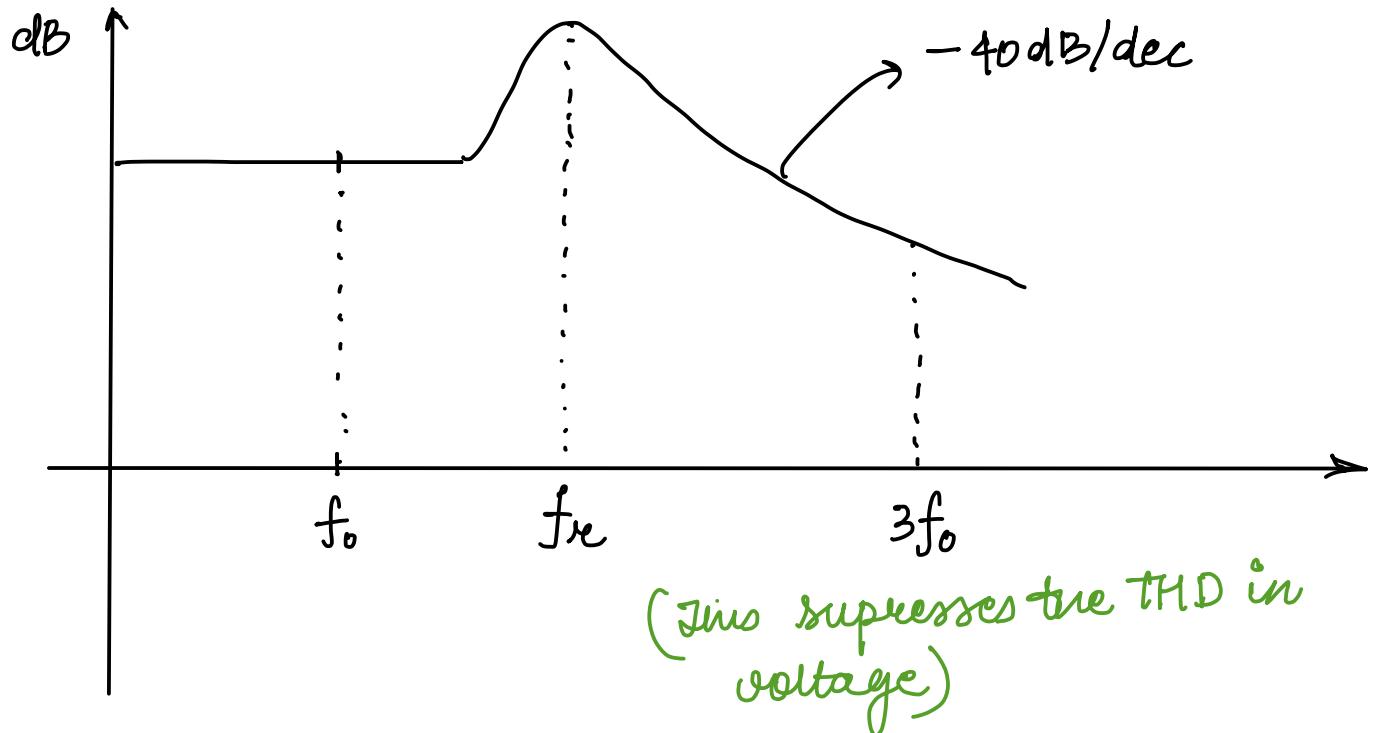
$$G_1(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s^2 LC + 1}$$



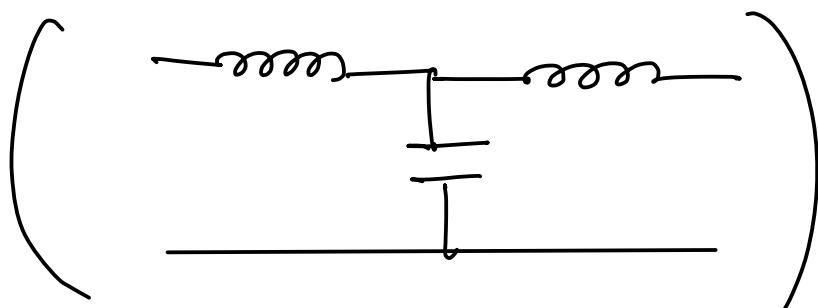We can have LCL filter, LCCL network filter. Keeps giving us better attenuation.




~~$$\text{Ass } f_{re} = \frac{1}{2\pi\sqrt{LC}} \approx 100 \text{ Hz. Two consequences:}$$~~

1) f_{re} is relatively low \Rightarrow Large L, C

2) Difference between f_3 and f_{re} is small \Rightarrow Less attenuation
 $(150 \text{ Hz}) \quad (100 \text{ Hz})$


Sine Triangle PWM


Harmonic Spectrum

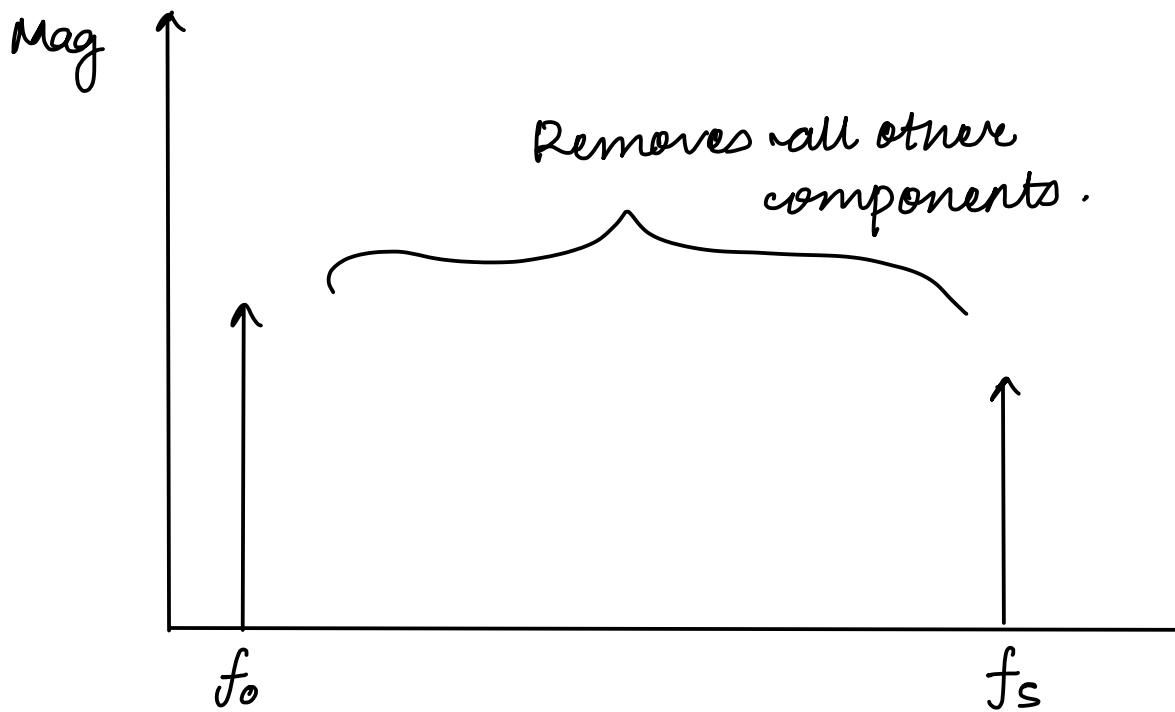

(eg. 10 kHz)

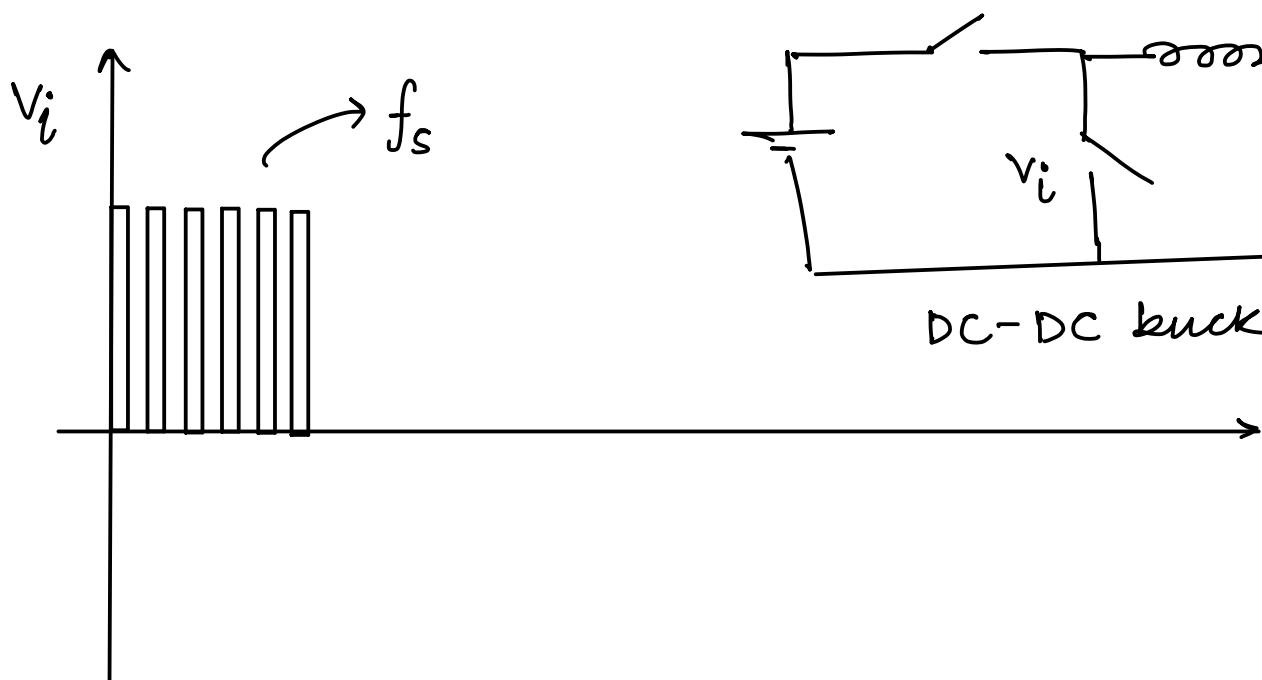∴ Now if I want to use a LC filter, f_c can be anywhere between f_0 and f_s . Thus smaller values of L and C. Also since f_s is crazy far away, we get crazy attenuation for f_s on using say a LC filter (-40 dB/dec)





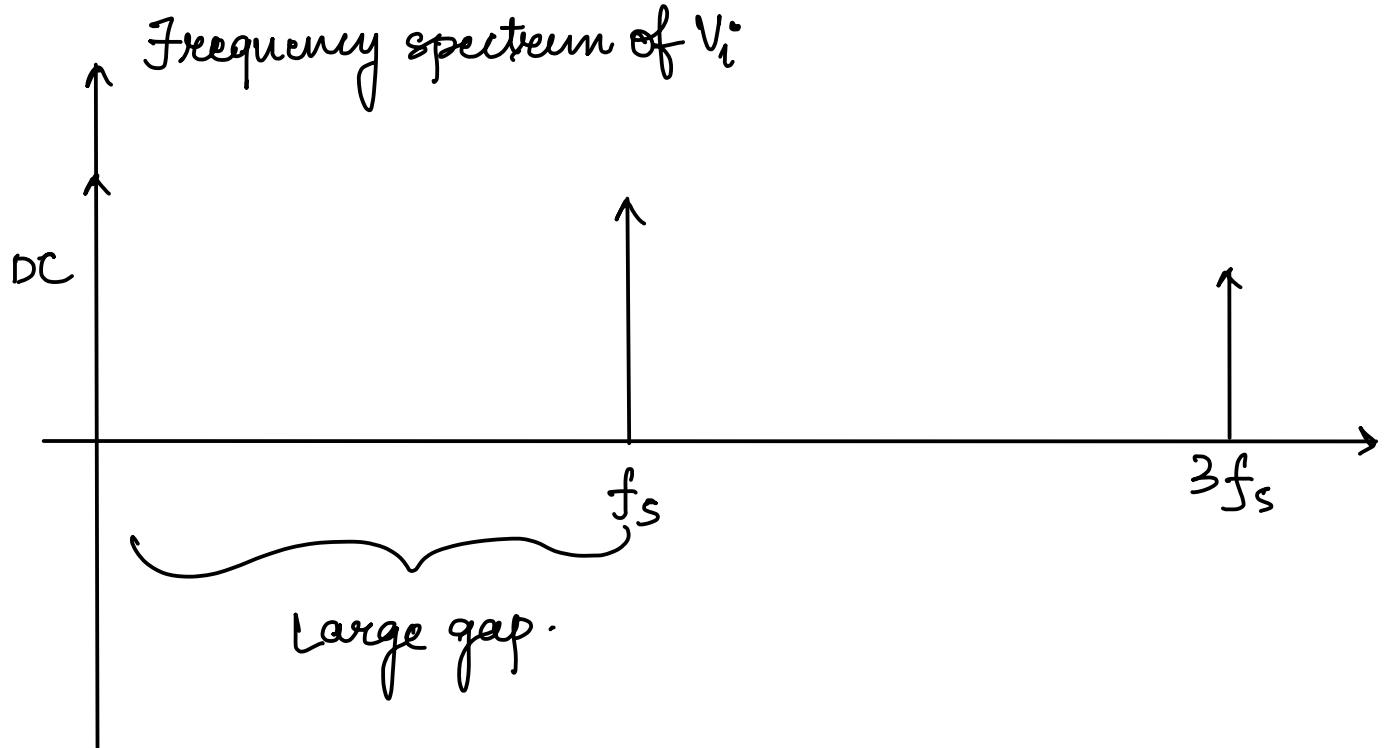



$$0 \leq M \leq 1$$


These are signals
(say written in Microcontroller)

$$\text{Ref} = M \sin(\omega_0 t)$$

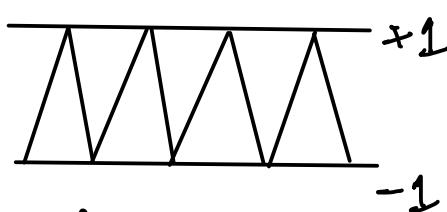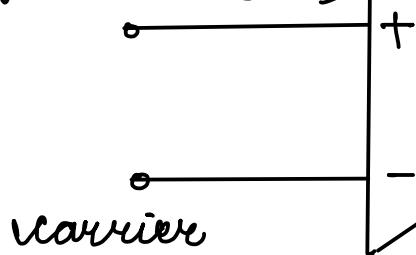


$$f_s = 10 \text{ KHz}$$

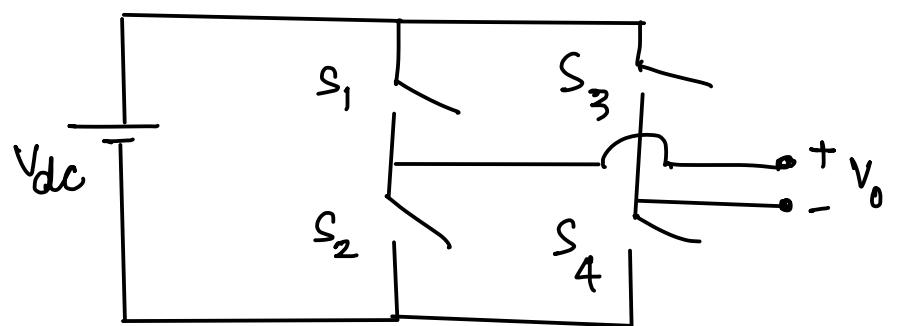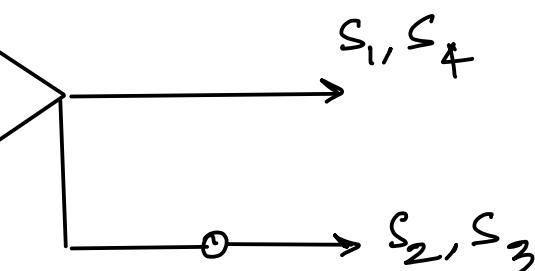


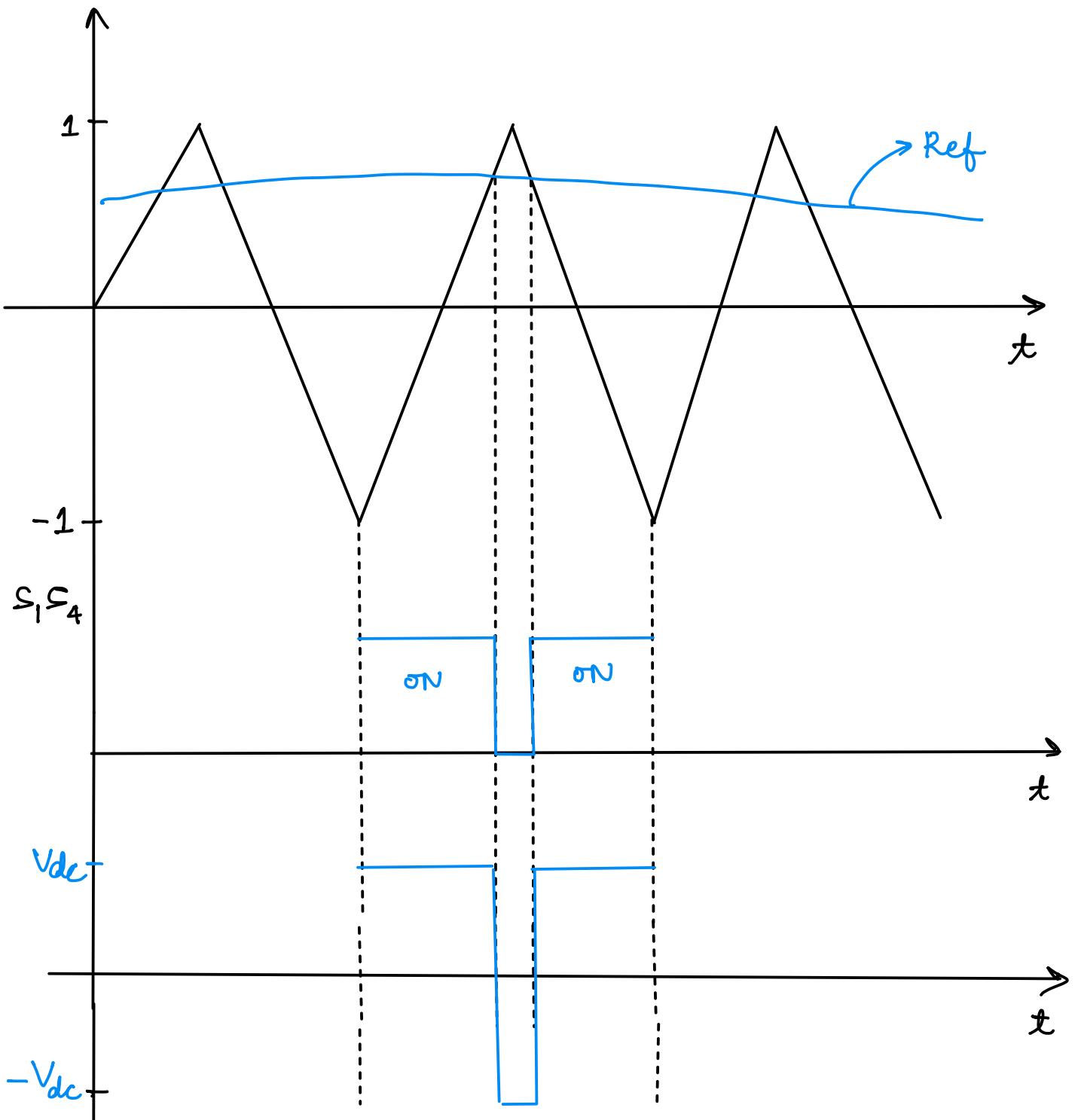

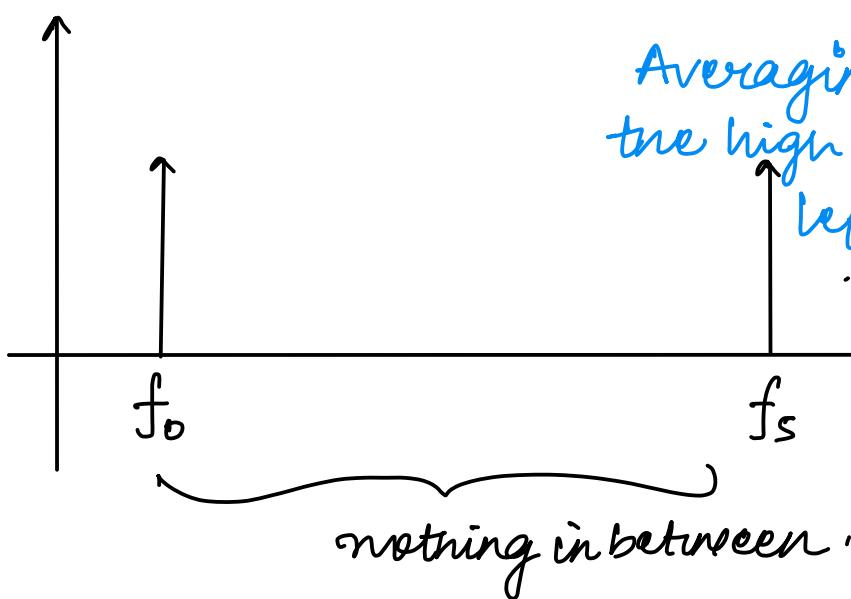Averaging over T_s removes the high frequency. We are left with fundamental freq. only.



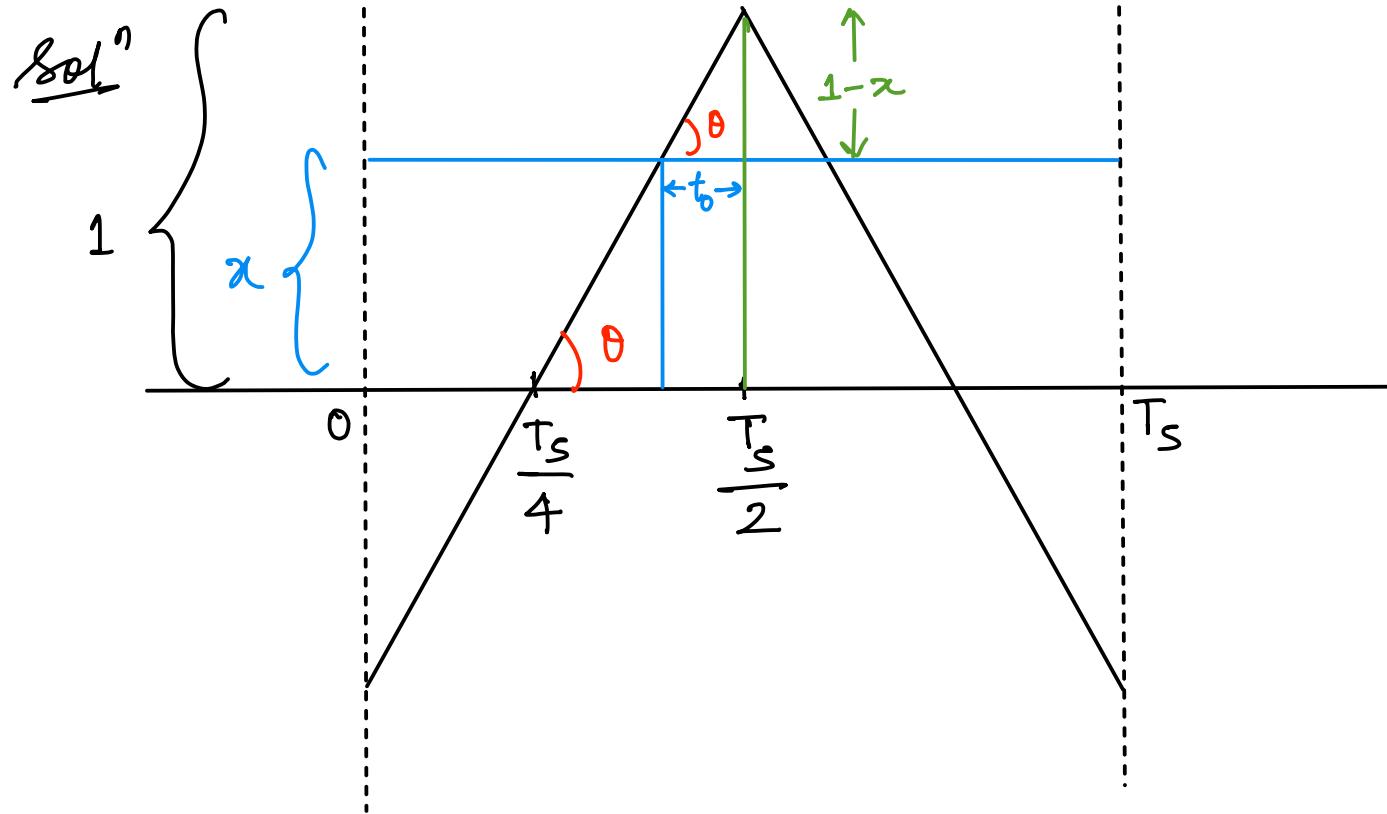Q Derive $\langle V_o \rangle_{T_s} = M V_{dc} \sin(\alpha_0 t)$



Reference signal is assumed to be constant over T_s

$$\tan \theta = \frac{1-x}{t_0} = \frac{1}{(T_s/4)}$$

$$\Rightarrow 2t_0 = (1-x)\left(\frac{T_s}{2}\right)$$

$$\therefore \langle V_o \rangle_{T_s} = \frac{2t_0 (-V_{dc}) + (T_s - 2t_0) V_{dc}}{T_s}$$

$$= \frac{T_S V_{DC} - 4t_0 V_{DC}}{T_S}$$

$$= \frac{V_{DC}}{T_S} \left(T_S - (1-\alpha) T_S \right)$$

$$= V_{DC} (1 - (1 + \alpha))$$

$$= \alpha V_{DC}$$

$$= M V_{DC} \sin(\omega_0 t)$$

Say our reference is a constant signal M .

Then on averaging over T_S , we would have got


$M V_{DC} \Rightarrow$ Buck converter.

Q How do we physically average over T_S ?


\Rightarrow Low pass filter.

Q Why are we getting $MV_{dc} \sin(\omega_0 t)$ instead of 0 after averaging?

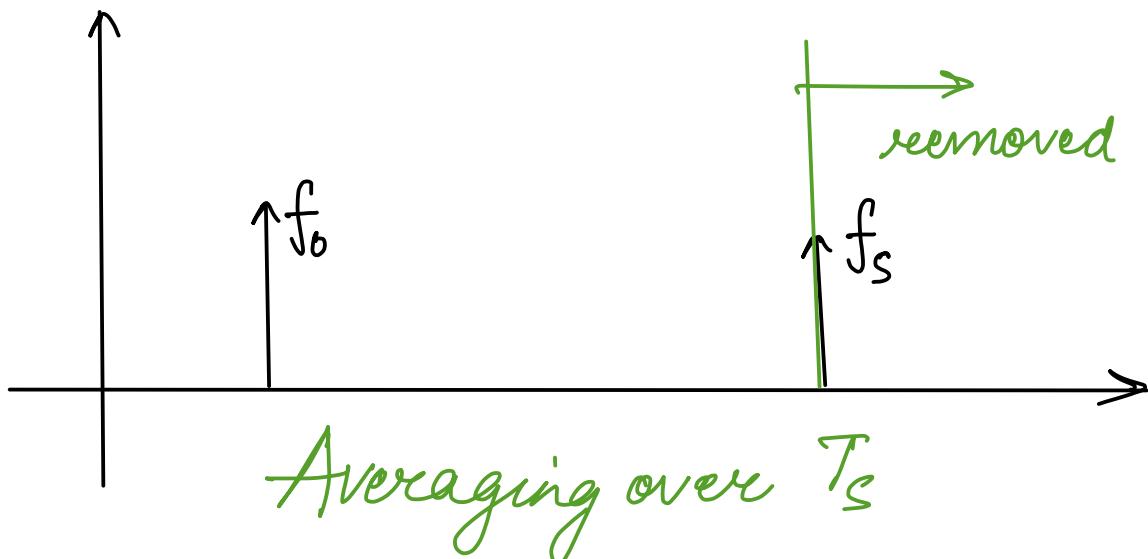Ans We are averaging over the switching period not the fundamental period



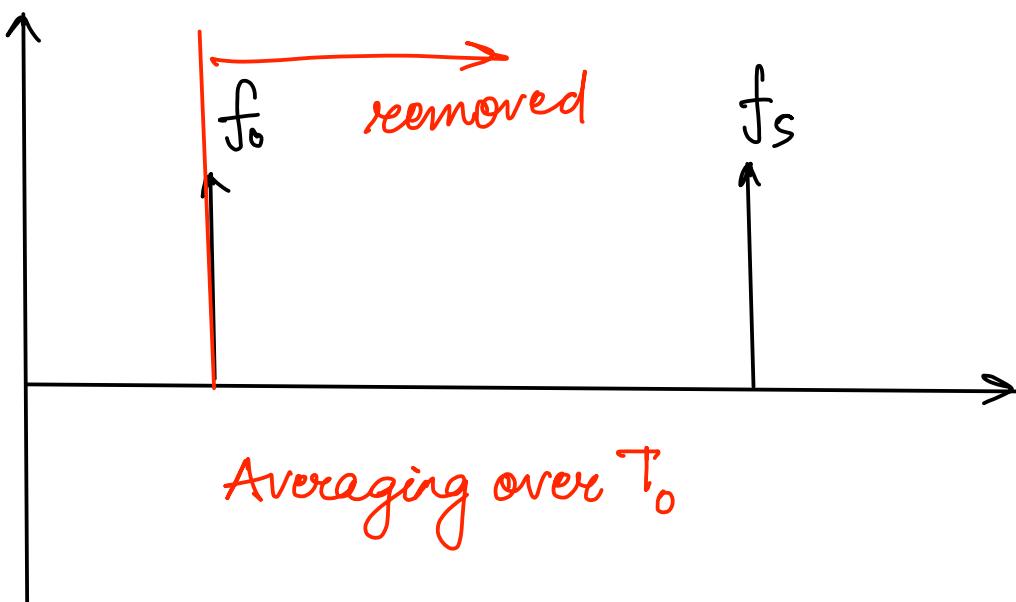
If we average over fundamental cycle, we get 0 because there is no DC component.



Inverter

Using 1- ϕ inverter for DC-DC

Application 1

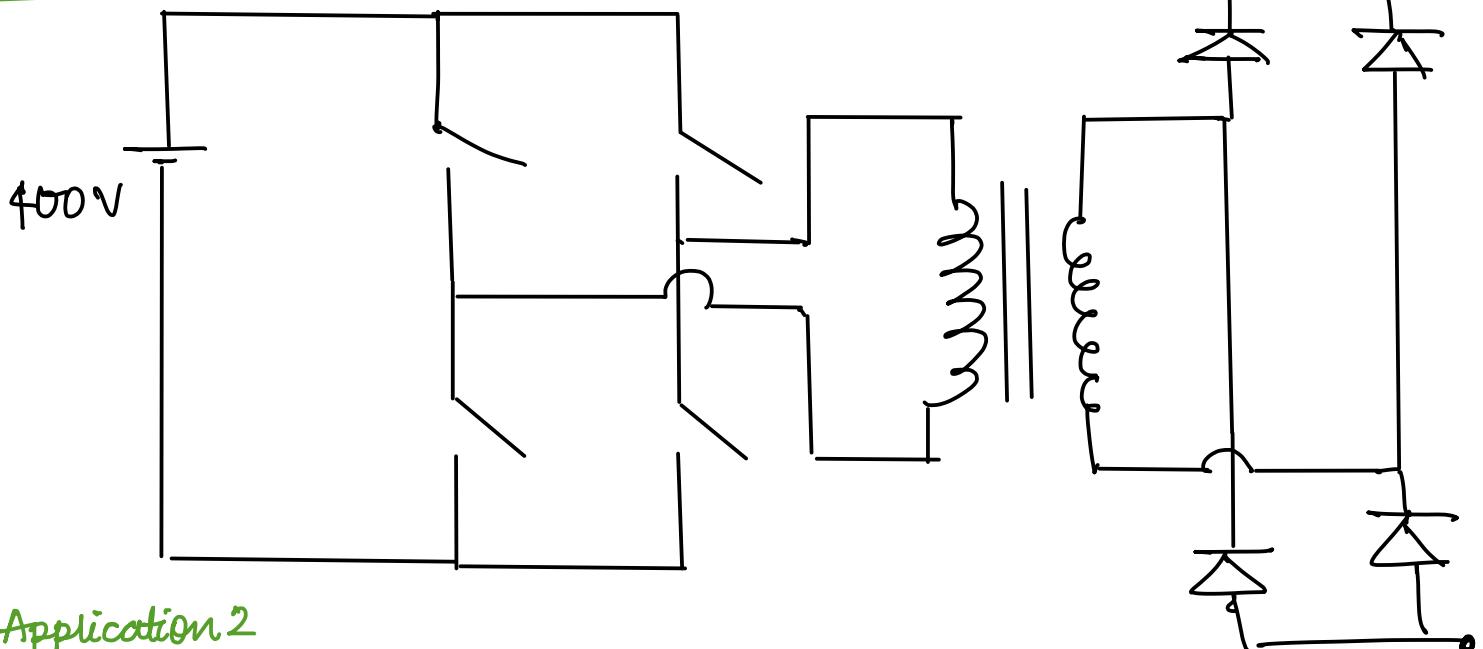

Application 2


In a house UPS system, because house would mostly have a single ϕ load

If we use SPWM \rightarrow no humming sound from fan
If we use fundamental modulation \rightarrow humming sound from fan due to other frequencies.




Only for IM fans -

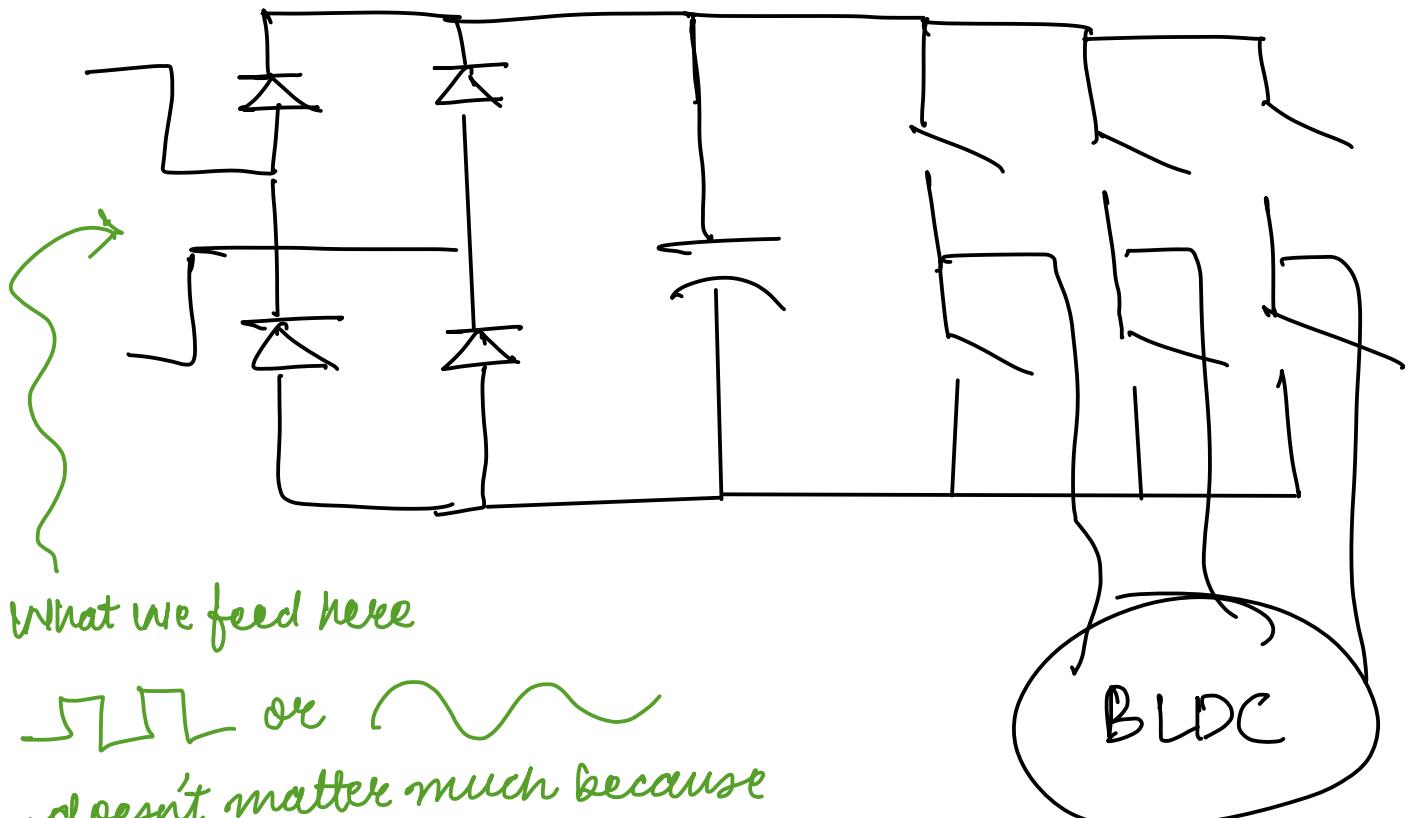BLDC fans → no difference whether it gets square or sine wave.




doesn't matter much because
it is anyways getting rectified. The torque production
happens on the right side not via the inverter in UPS .

(a)

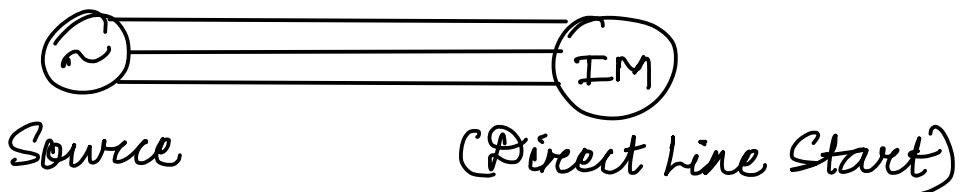

(b)

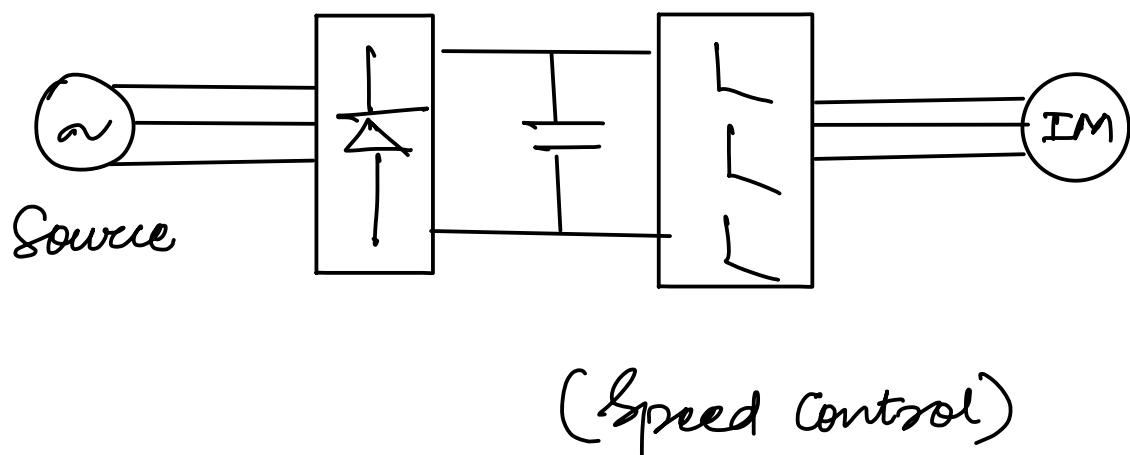


- (b) → Smooth Speed / Torque control
 → Field weakening ($\uparrow \omega$)
 → High T_{start}
 → Input current is always limited. \therefore low starting current.

Revise:

- τ -speed characteristics
- I_{max} formula
- Eq. ckt of IM.

3Φ Inverter

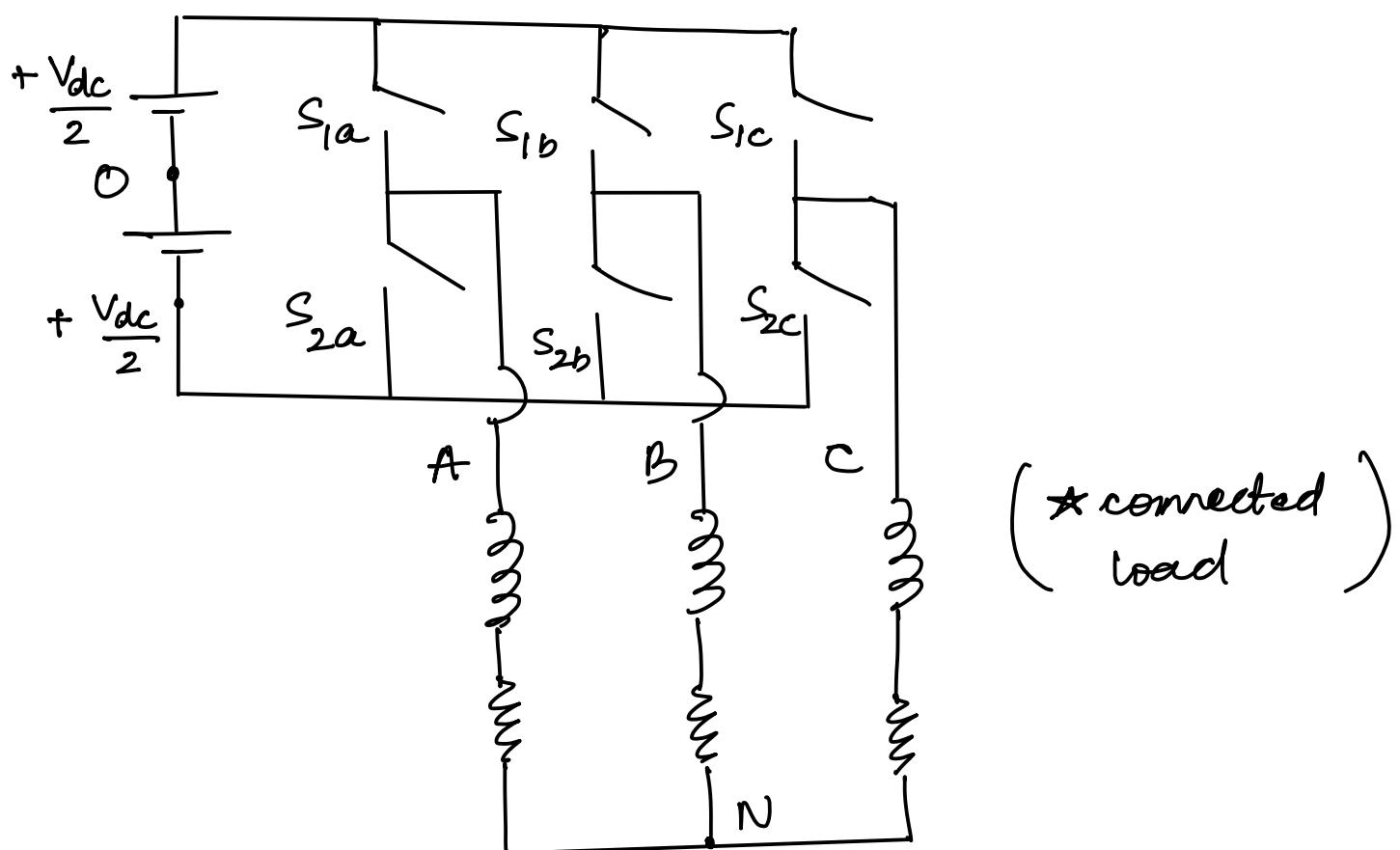


(*connected load)

(Balanced Load)

$$R_a = R_b = R_c (= R)$$

$$L_a = L_b = L_c (= L)$$

Fundamental Modulation

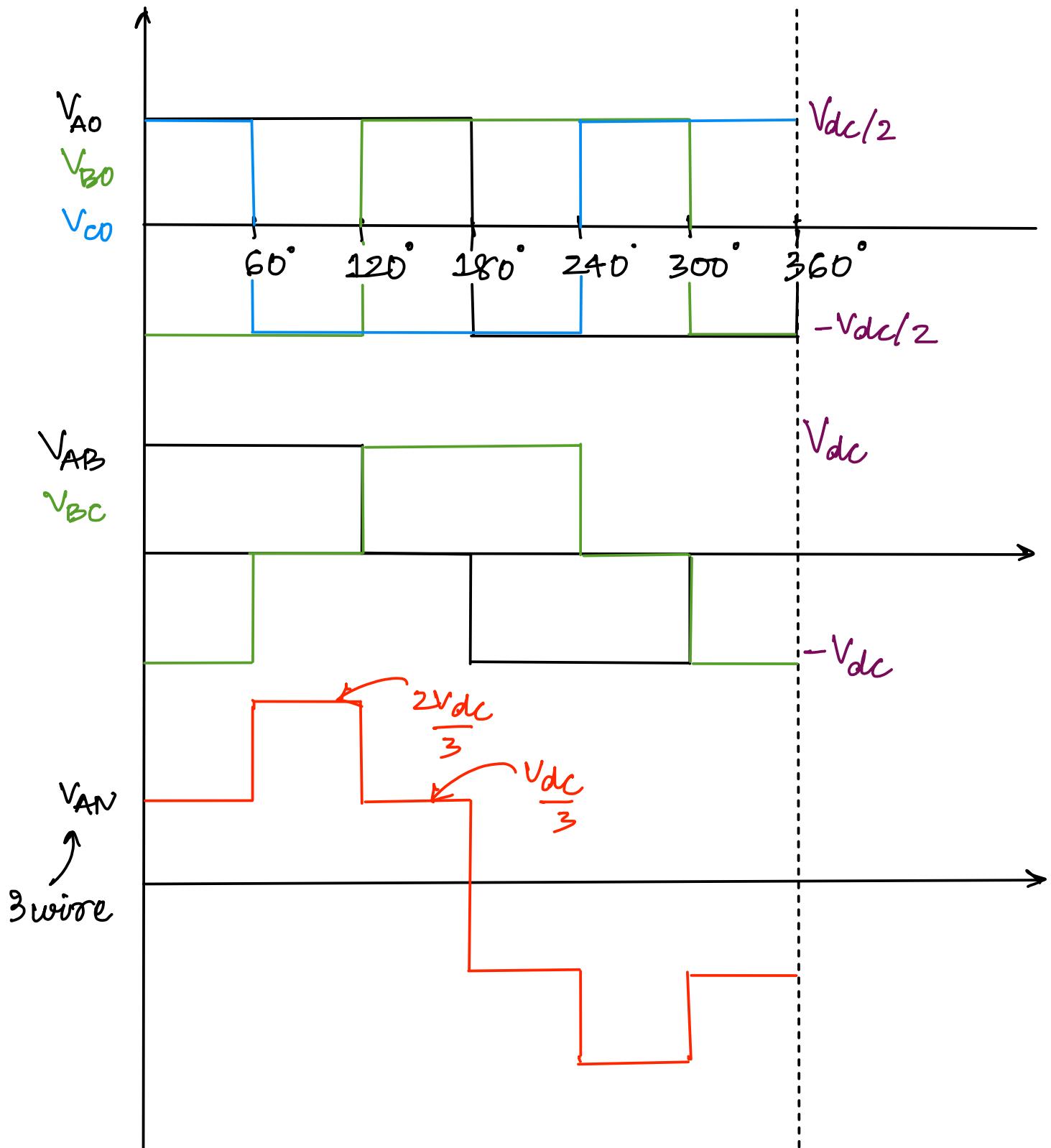

for 4 wire: Phase voltage = Pole voltage -

$$V_{AN} = V_{AO} - V_{NO}$$

V_{AO} : Pole Voltage for A -

V_{BO} : Pole Voltage for B

V_{CO} : Pole Voltage for C

V_{AB} , V_{BC} , V_{CA} : Line-to-line voltages

V_{AN} , V_{BN} , V_{CN} : Phase voltages

$$V_0 + V_{AO} - V_N = i_a R_a + L_a \frac{di_a}{dt}$$

$$V_0 + V_{BO} - V_N = i_b R_b + L_b \frac{di_b}{dt}$$


$$+ \quad V_0 + V_{CO} - V_N = i_c R_b + L_c \frac{di_c}{dt}$$

$$\Rightarrow 3V_0 + V_{AO} + V_{BO} + V_{CO} - R \cancel{\sum^0 i_a} - L \frac{d}{dt} (\cancel{\sum^0 i_a}) = 3V_N$$


$$\Rightarrow V_{NO} = \frac{1}{3} (V_{AO} + V_{BO} + V_{CO})$$

m: modulation index [m ∈ (0, 1)]

SPWM

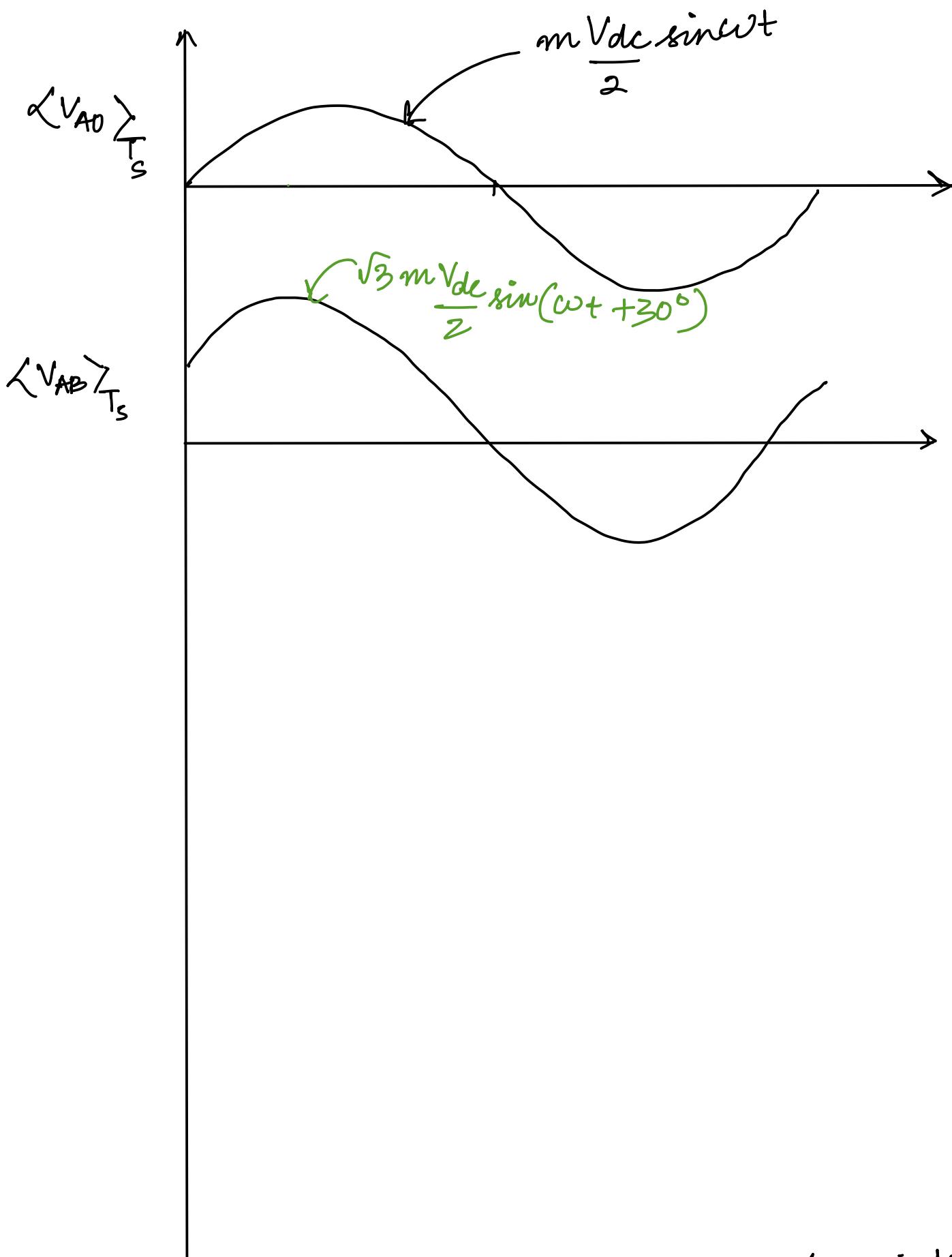

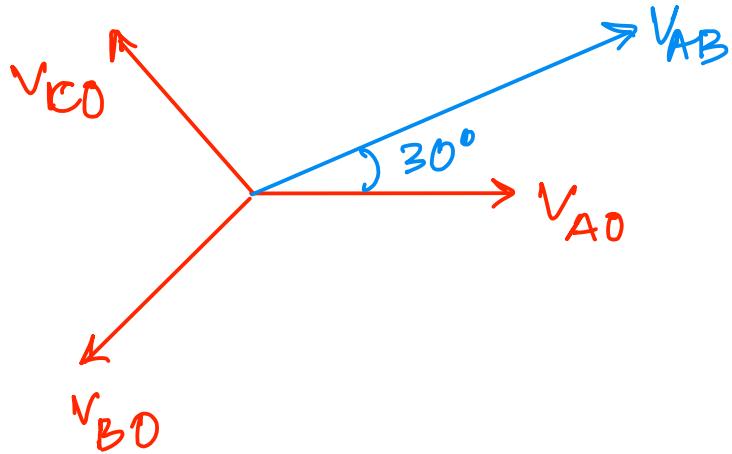The averaging of I will be done by the inductor in the load itself. Need not worry about it.



$$V_{AB} = \sqrt{3} \frac{mV_{dc}}{2} \sin(\omega t + 30^\circ)$$

Q What would be the phase and magnitude of fundamental component in phase voltage in 3-wire system?

Ans: $V_{AN} = V_{AO} - V_{NO}$

$$= V_{AO} - \frac{1}{3} (V_{AO} + V_{BO} + V_{CO})$$


$$= V_{AO}$$

\therefore Same as pole voltage.

In coming years, data centres as a load would become popular enormously.


Induction Motors

Equivalent ckt :-

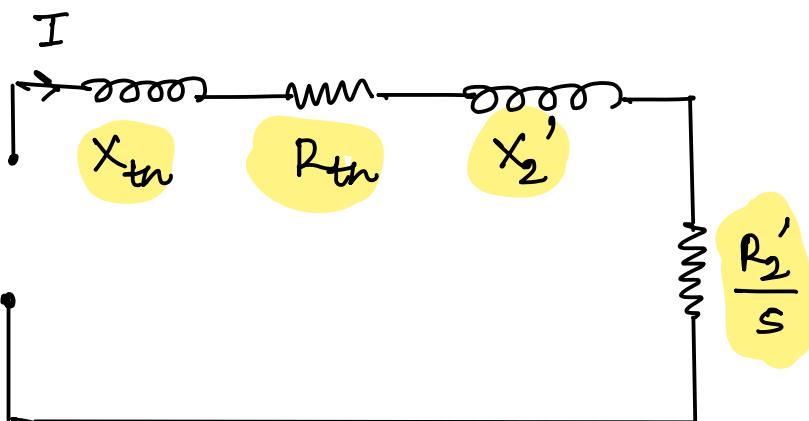

$$I = \frac{V_{th}}{\sqrt{(X_{th} + X_2')^2 + (R_{th} + \frac{R_2'}{s})^2}}$$

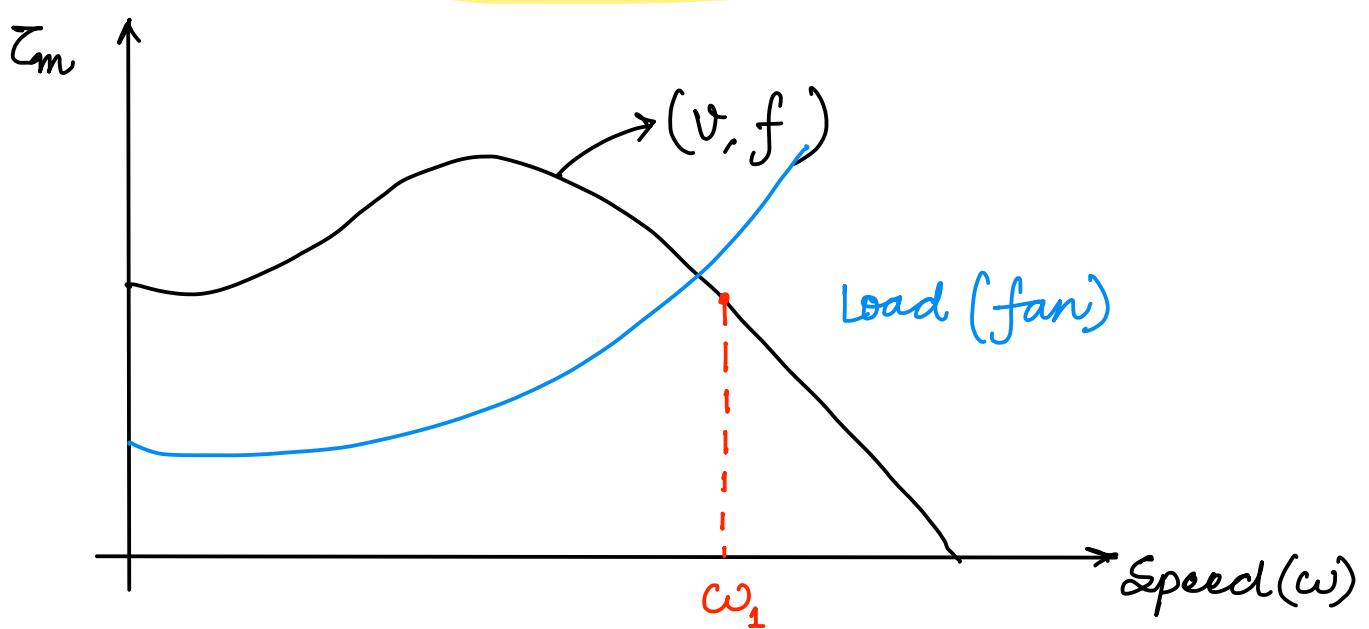
$$\tau_{max} = 3 \times \frac{V_{th}^2}{(X_{th} + X_2')^2 + (R_{th} + \frac{R_2'}{s})^2} \times \frac{R_2'}{C_{syn}} \times \frac{1}{s}$$




ω_1 : speed at which the fan will rotate.


Line start limitations

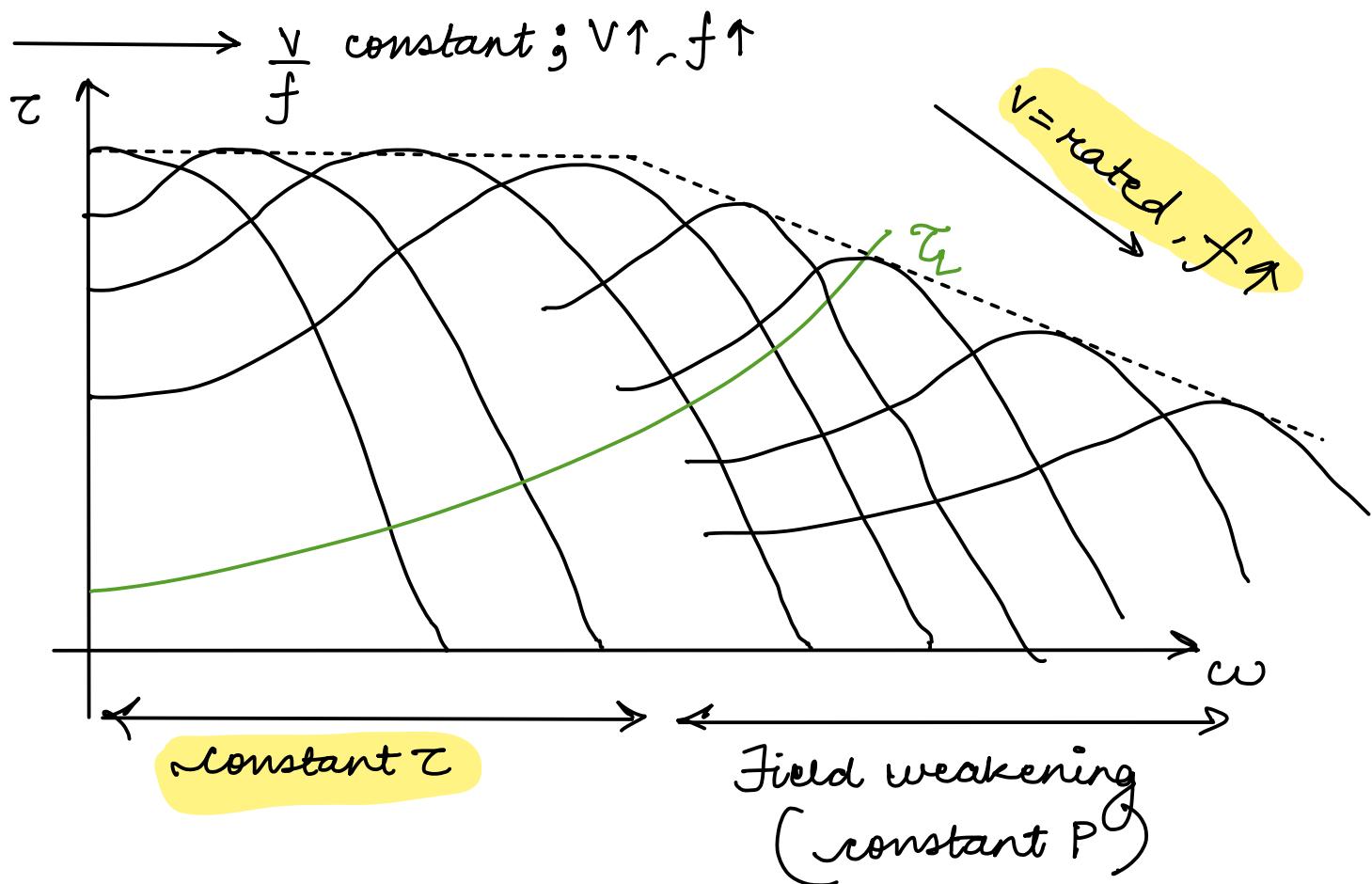
- Fixed speed
- $T_{start} < T_{max}$ (so it takes a long time to settle to desired speed)
- High starting current.



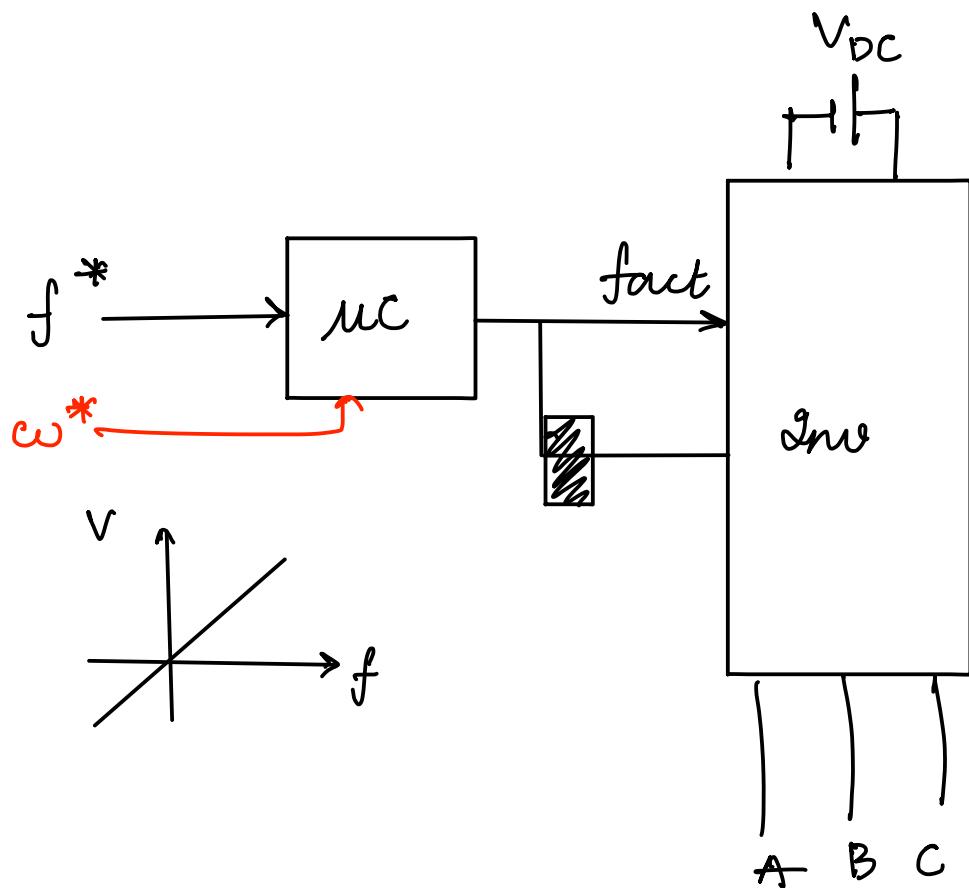

$$V_a^* = \sqrt{2} \cos(2\pi f t)$$

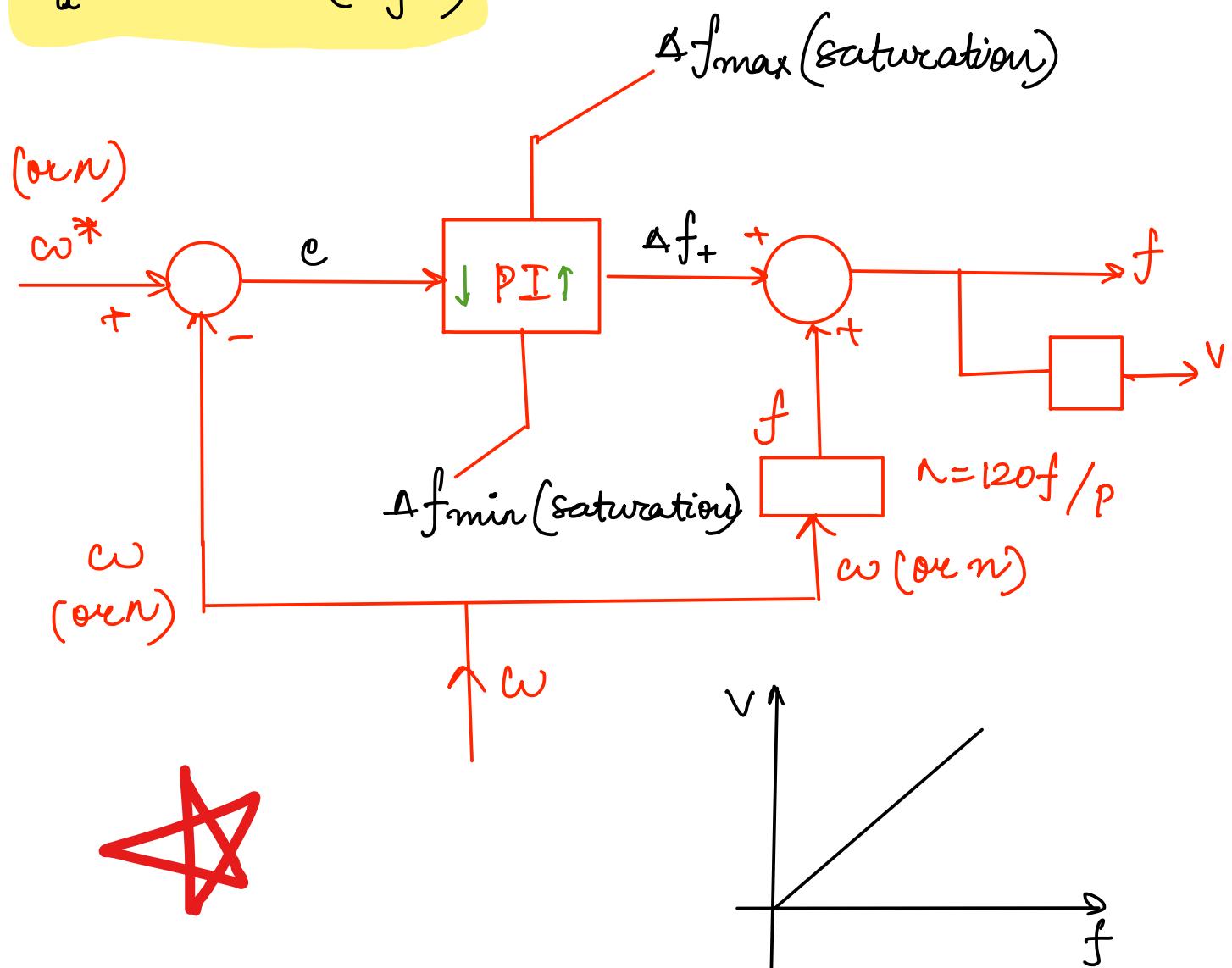


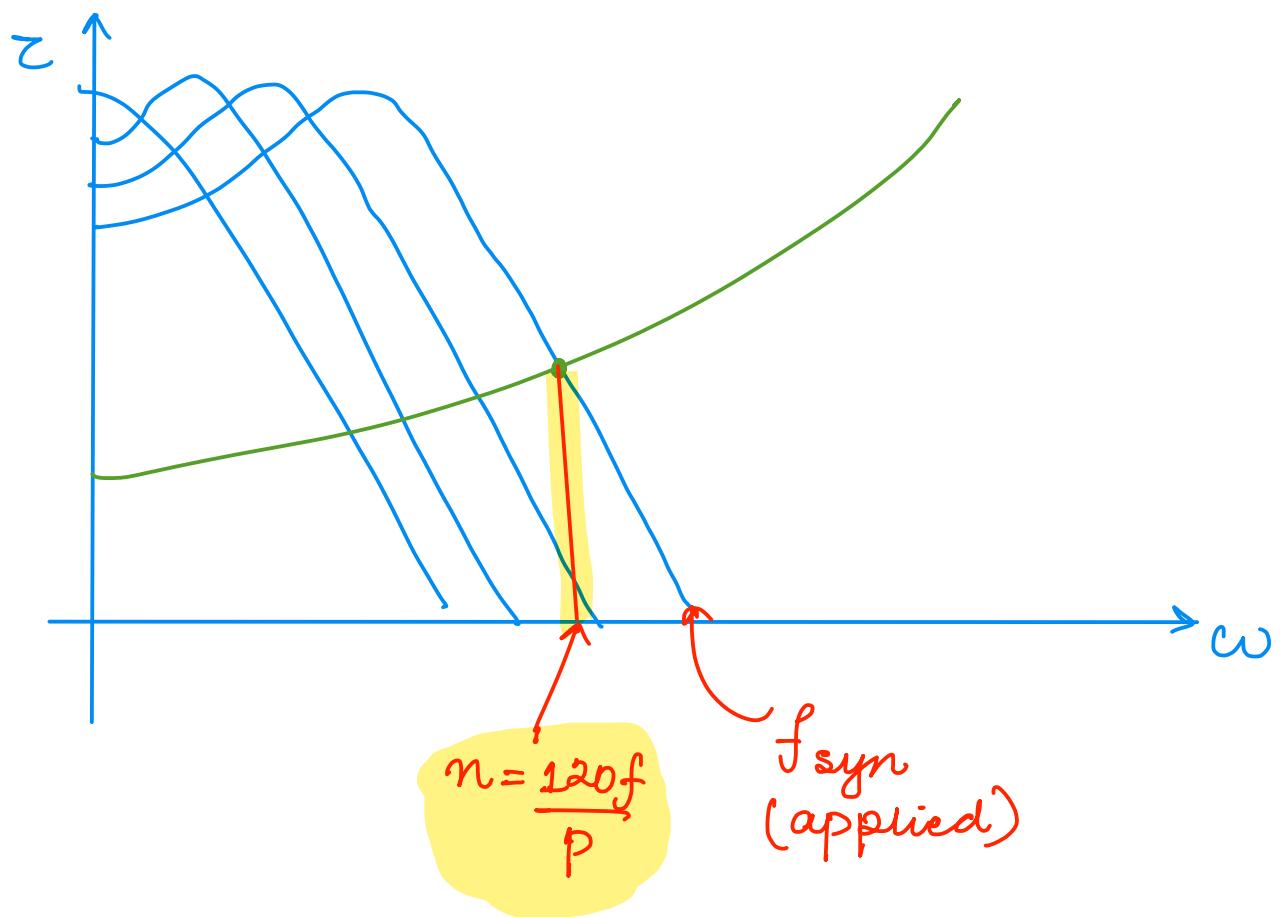



Power Systems

Limitations of 1 Generator

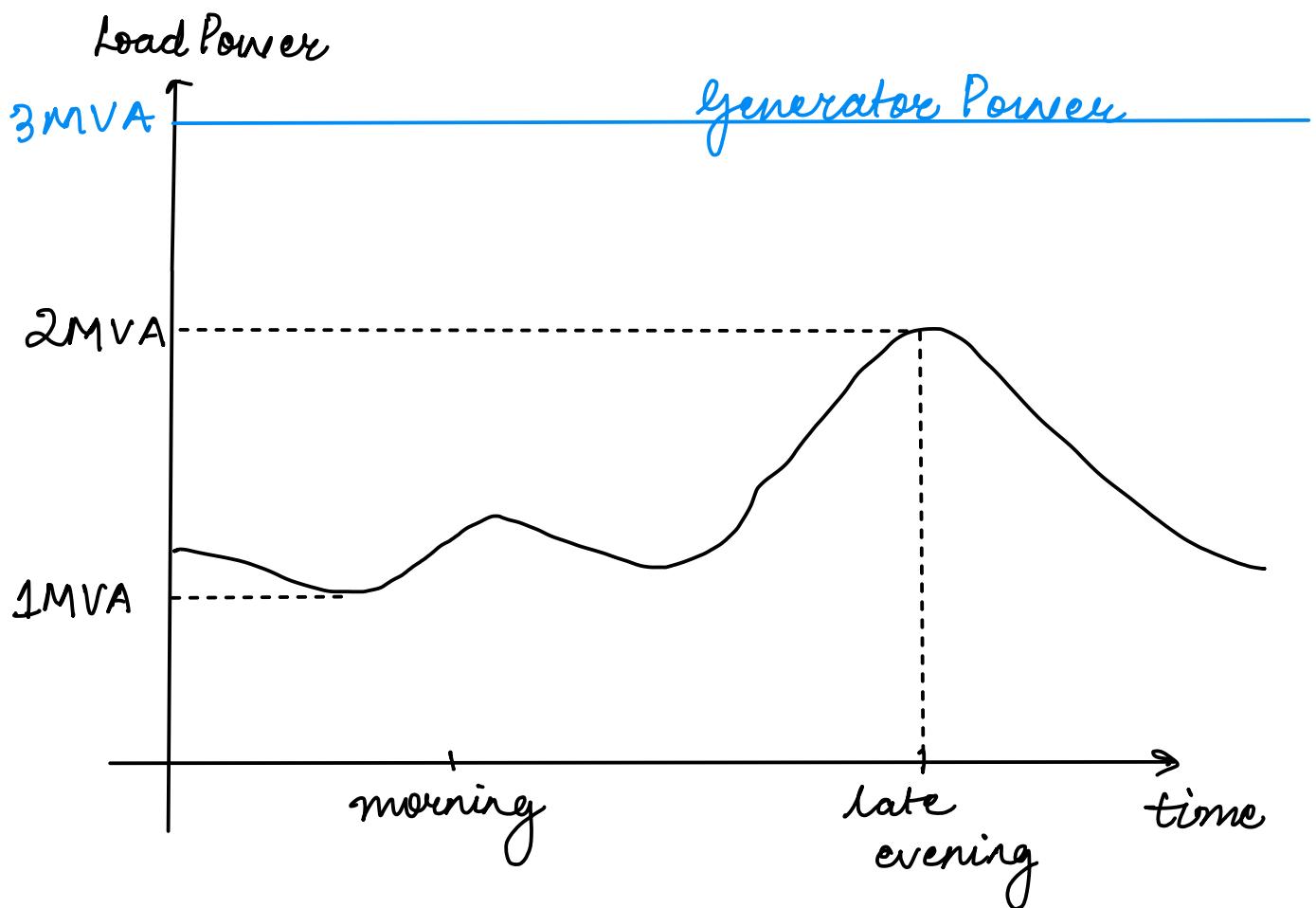- Reliability.
- Over sizing / capacity, generator
- Poor efficiency at light load.




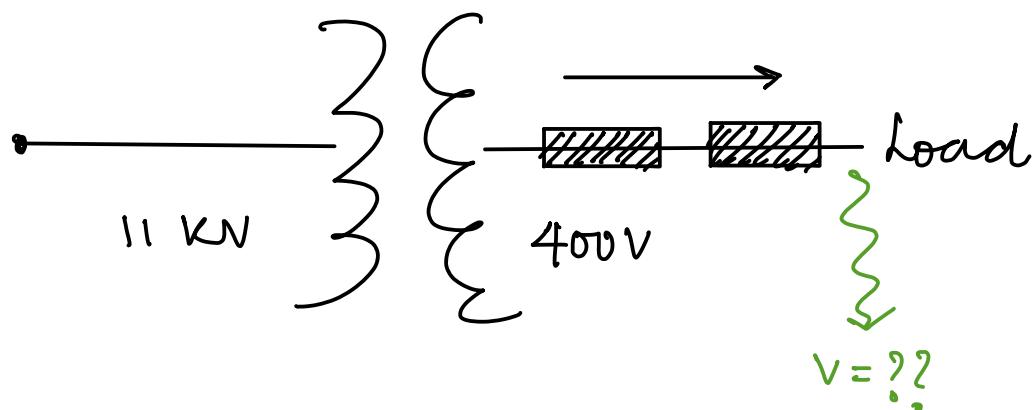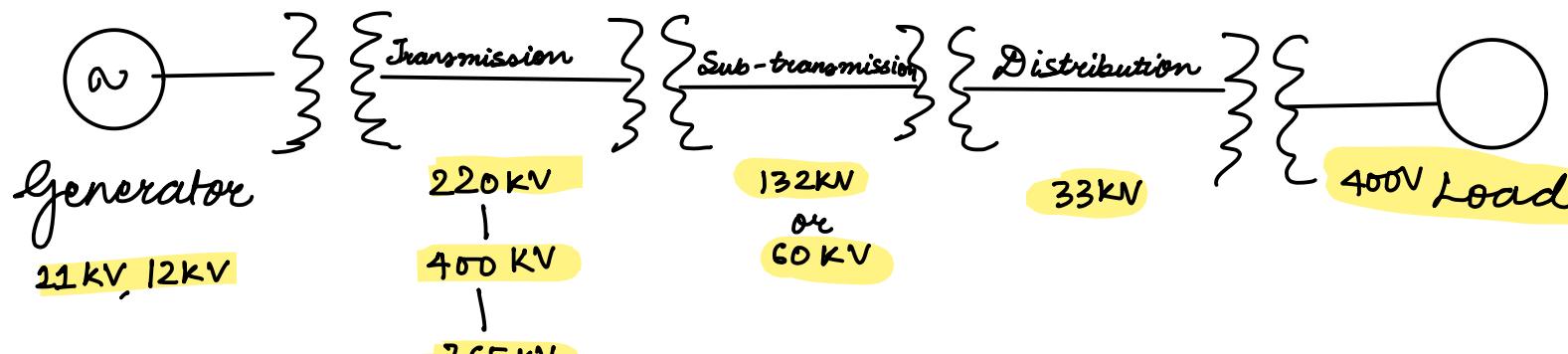These three problems can be solved by interconnecting multiple loads & generator systems together.





→ Auto transformer can be used, but in a small scale (such as a room), it is highly impractical


Thus we do this in a substation level

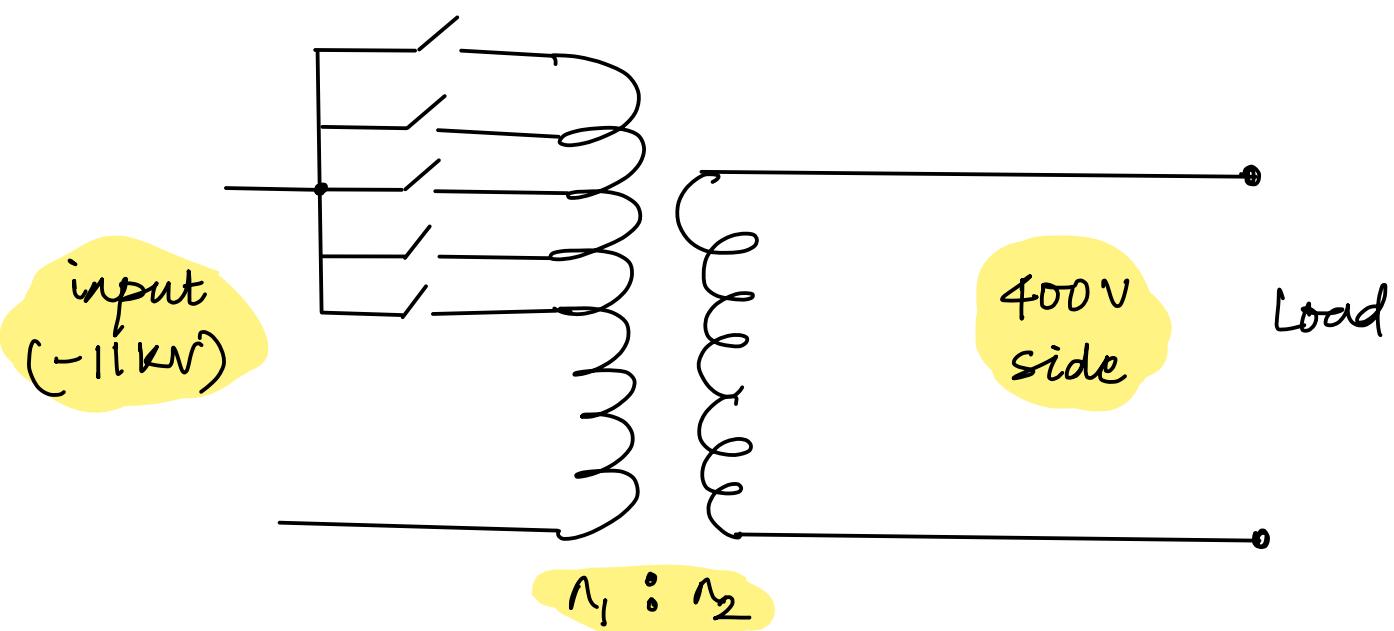

γ can be changed

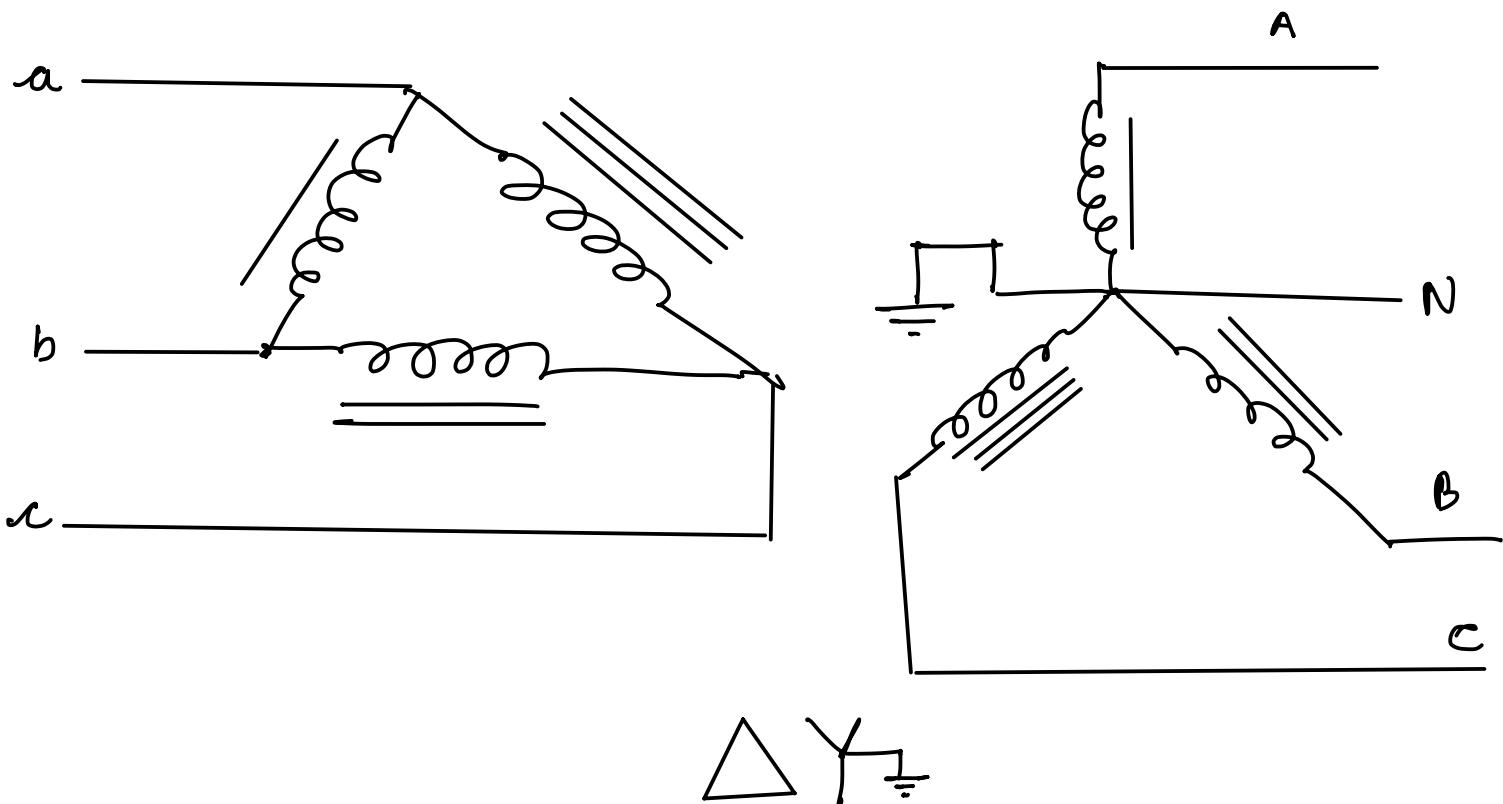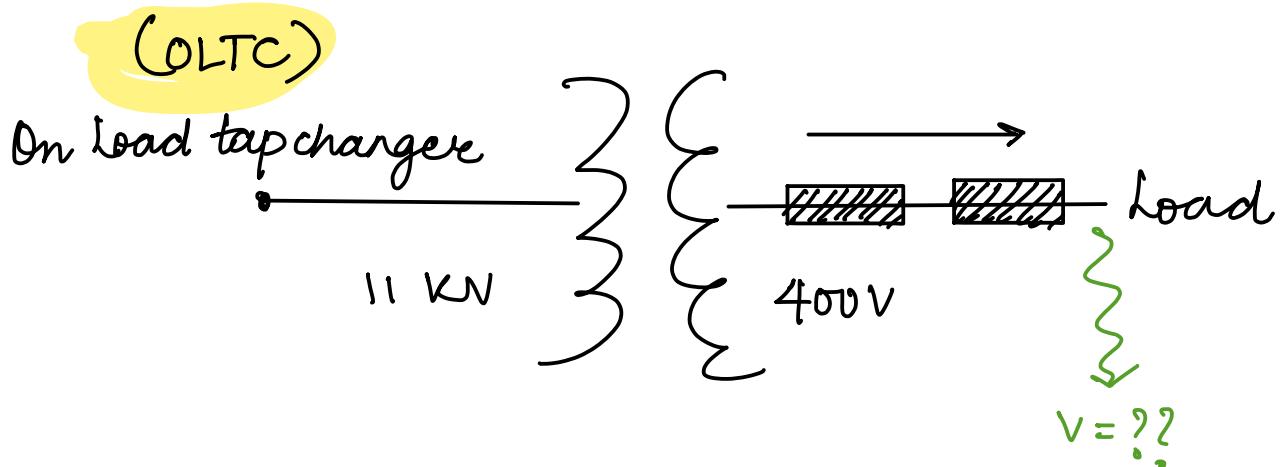Tappings typically on HV side, because less current on HV side, so easier to make and break circuit



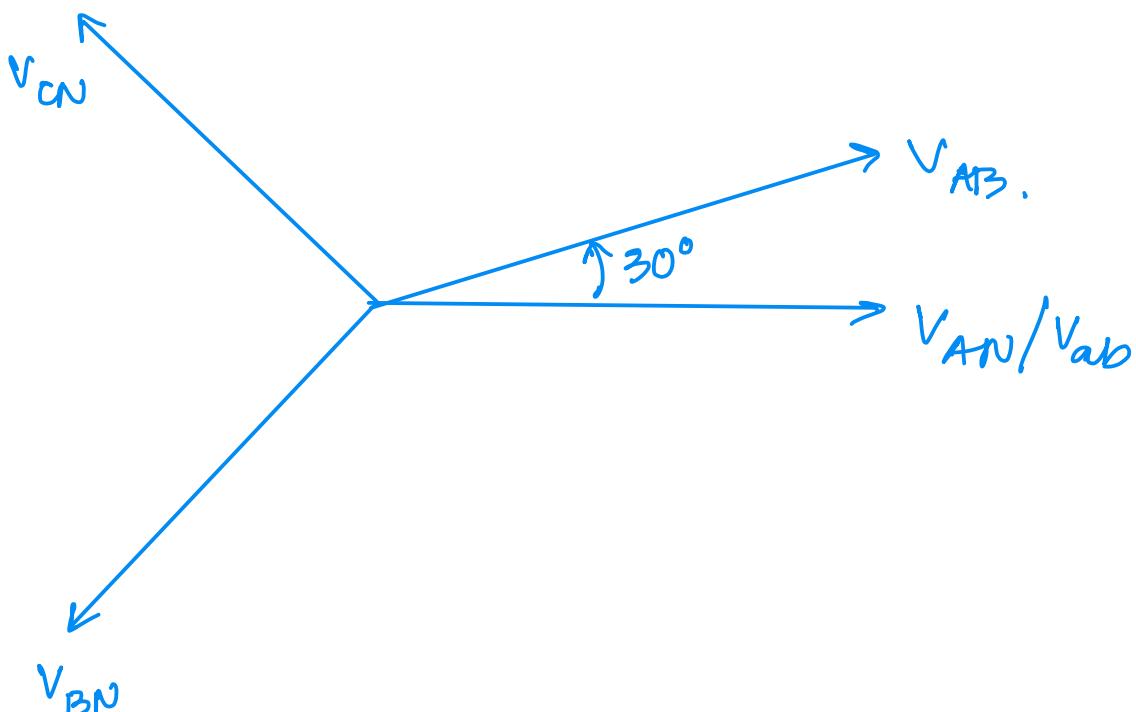

Line to Line of Y leads line to line of Δ


We have to do an earth at the Neutral on the load side, so that there is a well defined phase voltage that gets applied.

Δ on source? Because if we have a 3rd harmonic on source, we can chop it off or not send that 3rd harmonic to the load side.

Synchronous Generator

→ High speed (Less poles)
→ Low speed (More poles)

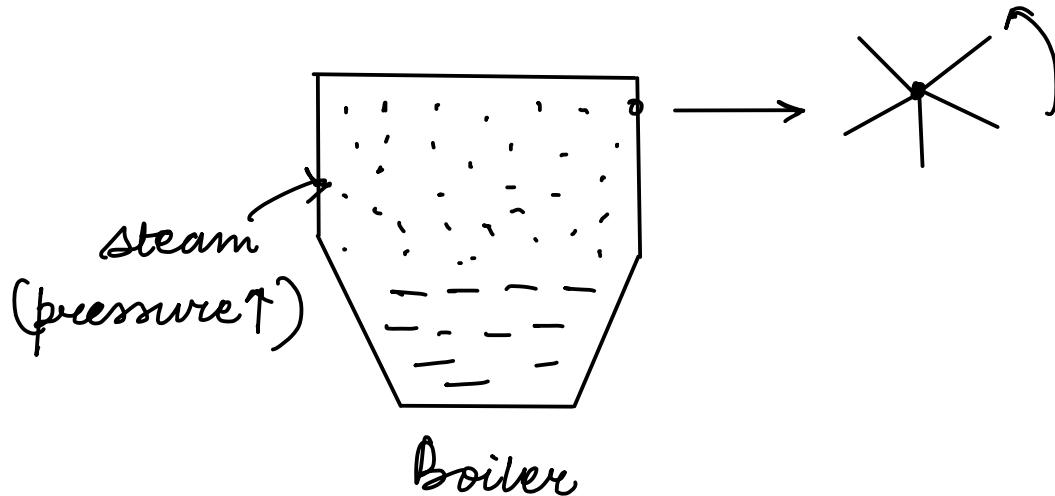ways of electricity production → Coal
→ Nuclear



→ Gas

→ Wind

→ Diesel

→ Hydro

→ Solar

→ Photo voltaics (PV)

→ Thermal (Based on sun's heat after concentration of sunlight using reflectors/concentrators)

All can rotate the sync. generator, but not all of them rotate with same speed -

$$n_s = \frac{120f}{P}$$

when n_s is low \rightarrow large number of poles
 n_s is high \rightarrow low number of poles

(We always want f to be 50 Hz in India)

We kept some systems running even if there are no loads \rightarrow Spinning Reserves.

(But we can't keep spinning reserves for all day)

$\Rightarrow \therefore$ we use a combo of spinning reserves and scheduling.

Photo Voltaics \rightarrow v. Fast but no control over power

Diesel \rightarrow fast but not connected to grid


Hydro \rightarrow fast

Wind \rightarrow fast but again no control over power

Gas \rightarrow fast

The substitute to spinning reserves is storage.


Synchronous Generator

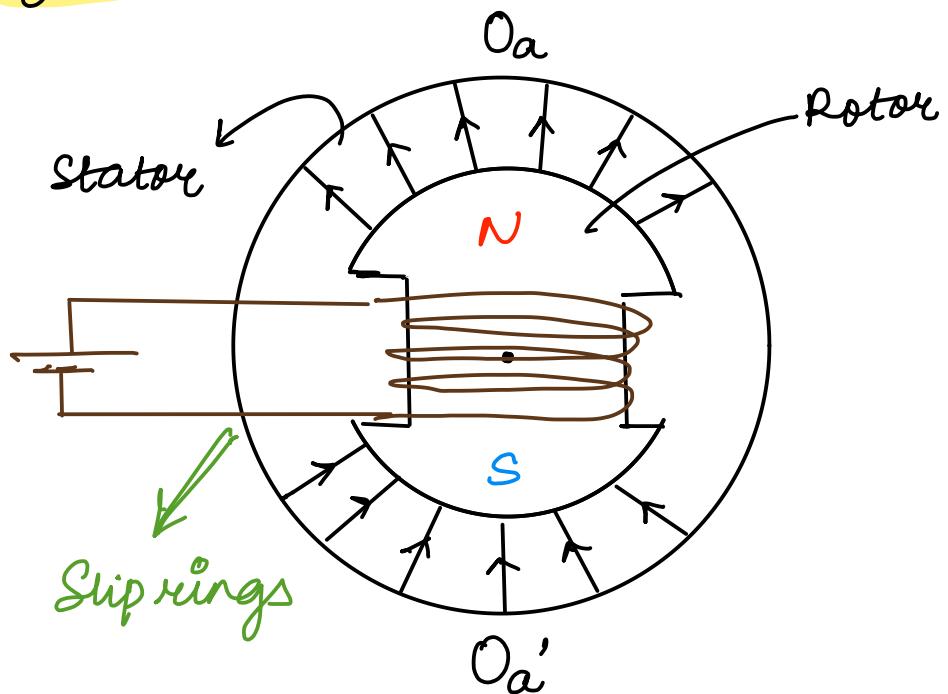


→ Wound rotor v/s Permanent magnet rotor

There is a net flux change in O_a O_a' coil when the rotor is rotating

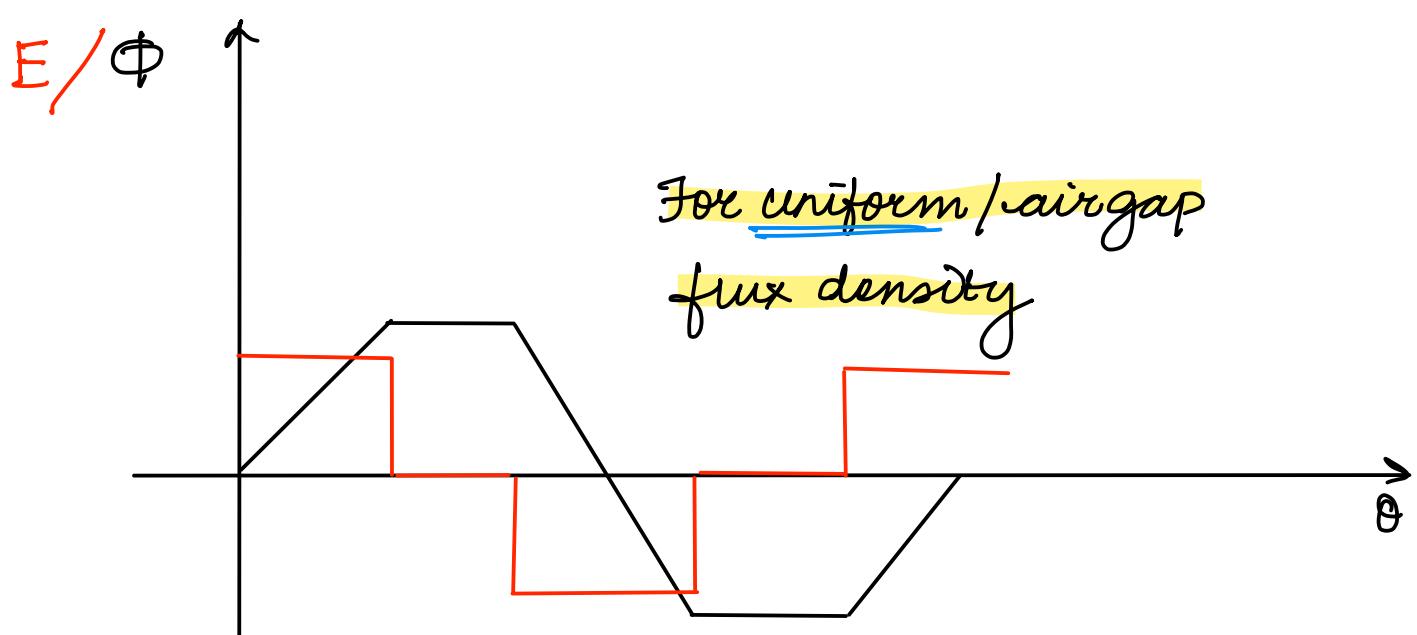(Don't confuse with brush commutator arrangement)




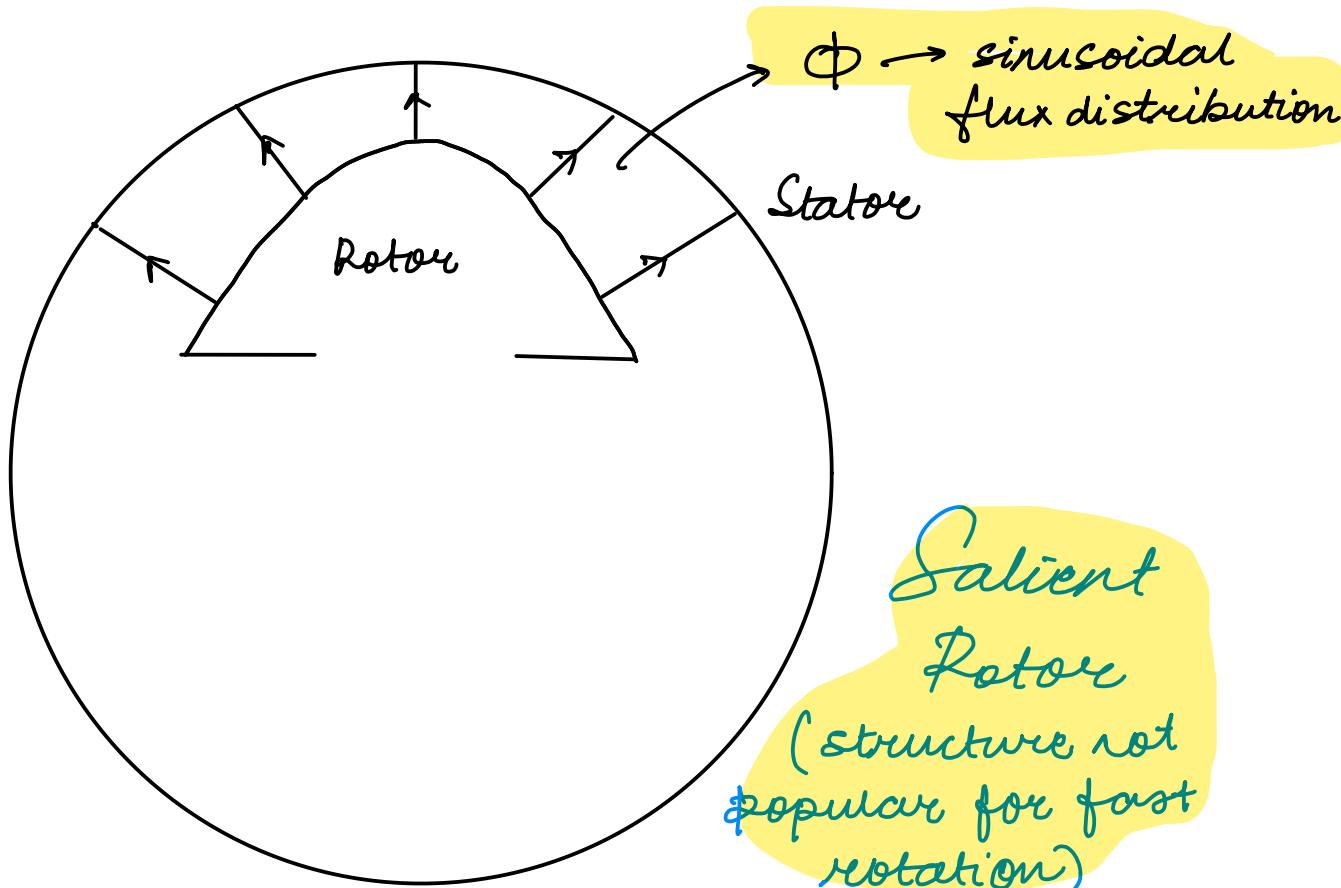

Salient Rotor
(structure not popular for fast rotation)


⇒ Shape of voltage induced = Sinusoidal

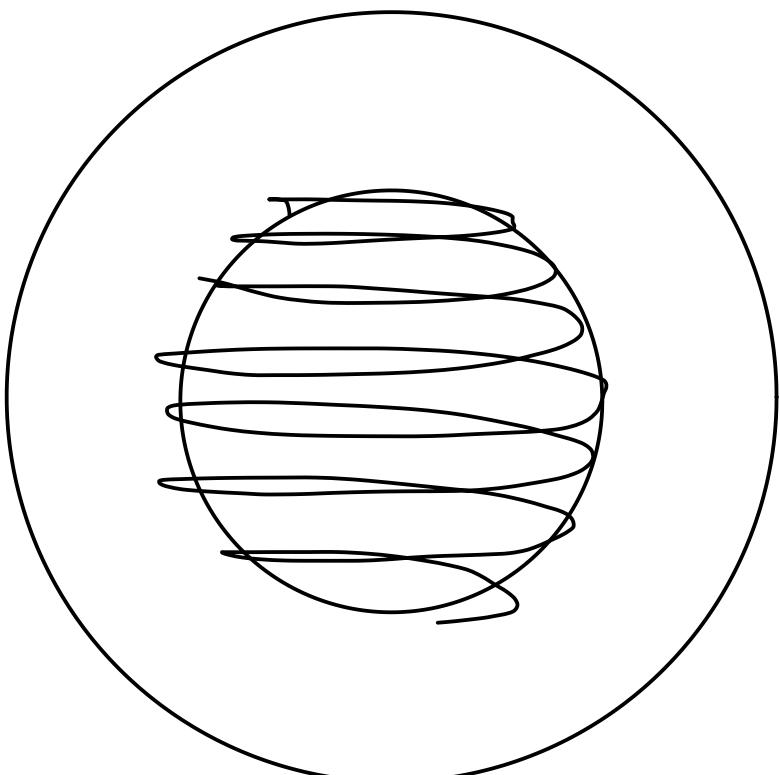Other way of getting a sinusoidal flux is ~



Cylindrical Rotor.

Sync Generator

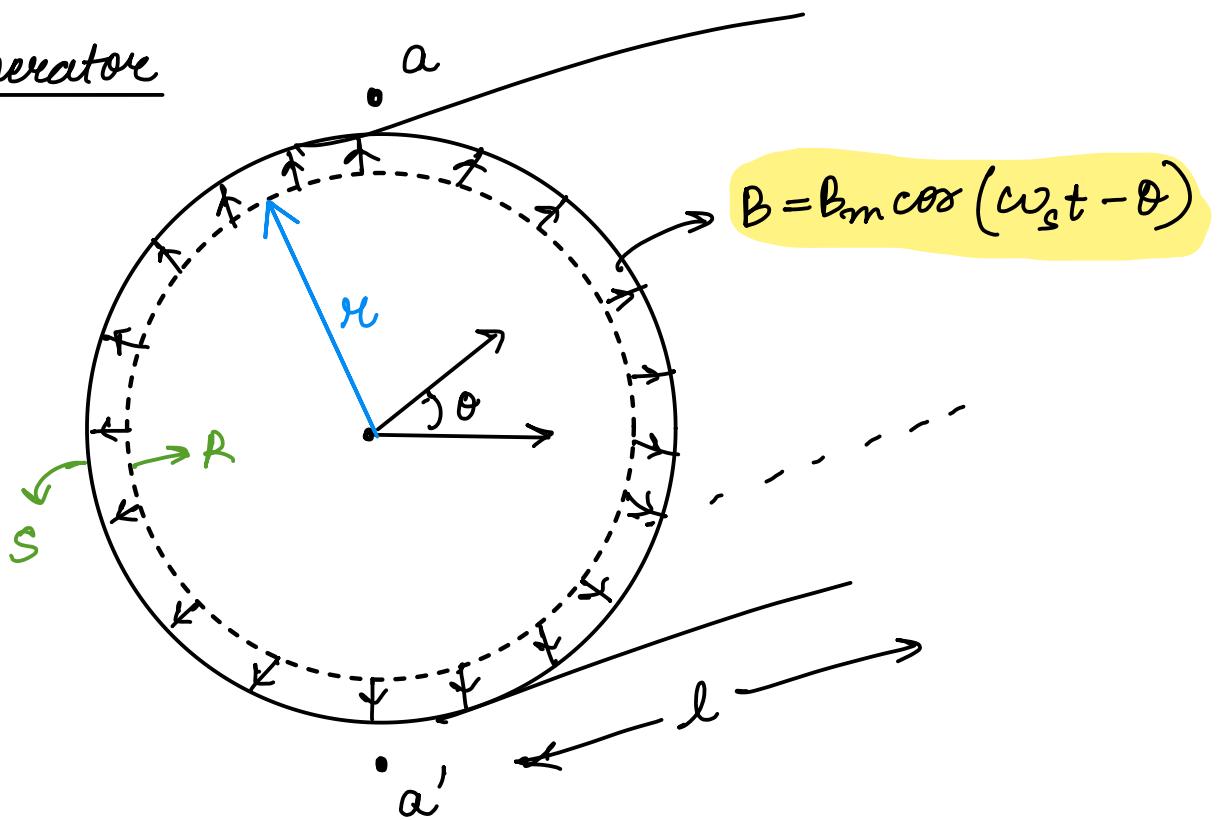

Rotor winding a.k.a. field winding
 Stator winding a.k.a. armature winding

(Used to be other way round
 in DC machine)

$$\Phi_{a-a'} = \int_{\pi/2}^{3\pi/2} B r d\theta$$

$$= \int_{\pi/2}^{3\pi/2} B_m l r \cos(\omega_s t - \theta) d\theta$$

$$= 2 B_m l r \cos(\omega_s t)$$


$$= \Phi_m \cos(\omega_s t)$$

$$e_a = -N \frac{d\phi}{dt} = N \Phi_m \omega_s \sin(\omega_s t)$$


In reality, we can't put N turns in a single slot -

$$\therefore e_a = k_w N \Phi_m \omega_s \sin(\omega_s t)$$

$$E = 4.44 N f \Phi_m k_w$$

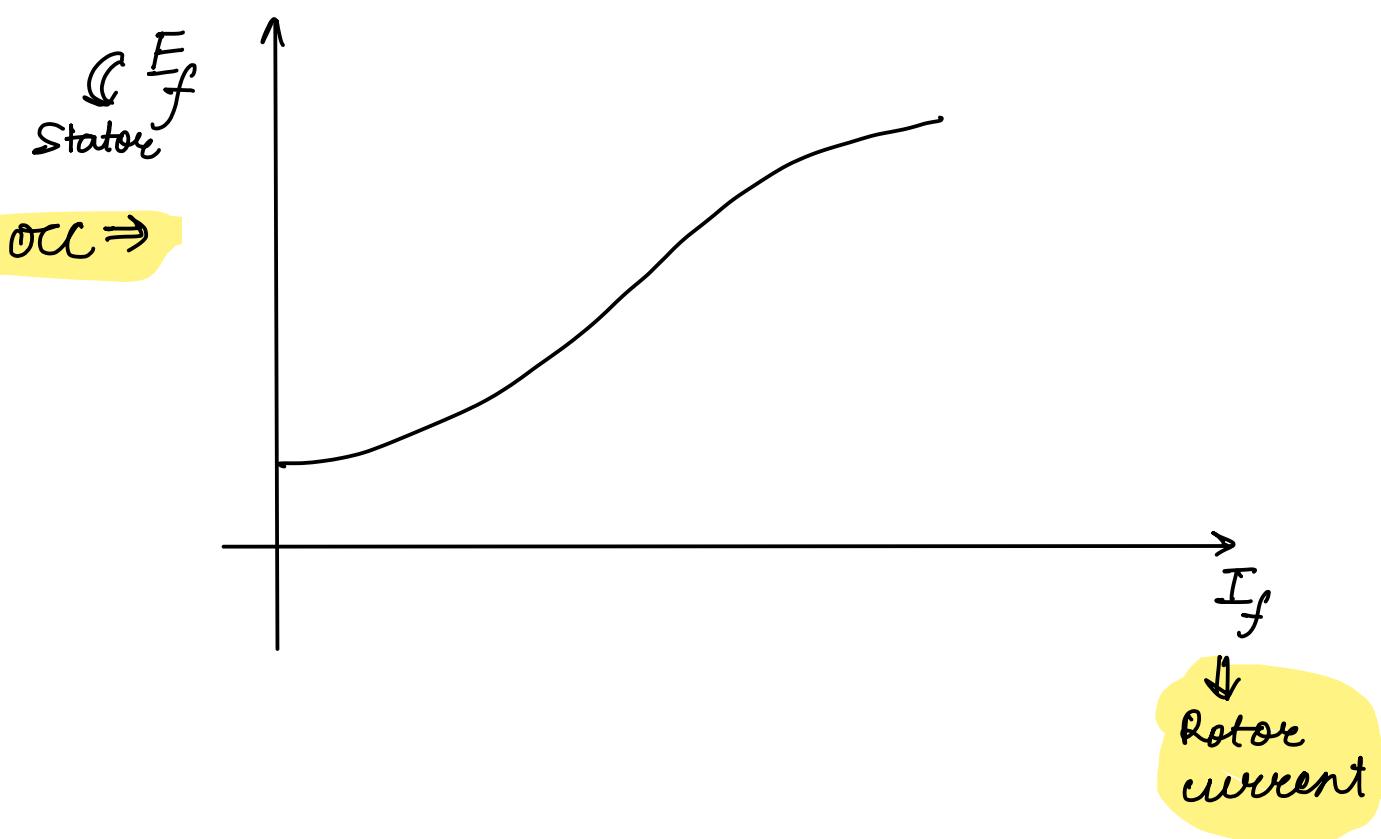



Eq. ckt:
(per phase)

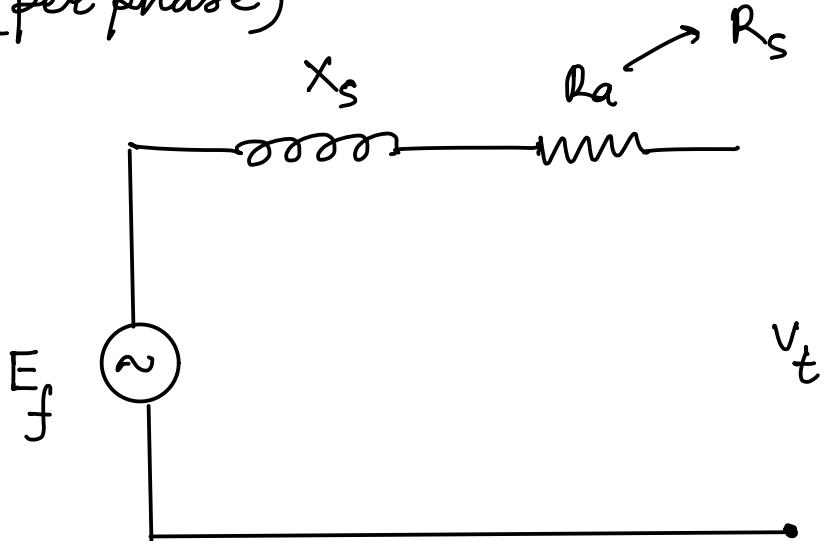

$$X_s = X_{arc} + X_L$$


(Synchronous Reactance)

1 Generator + 1 Load

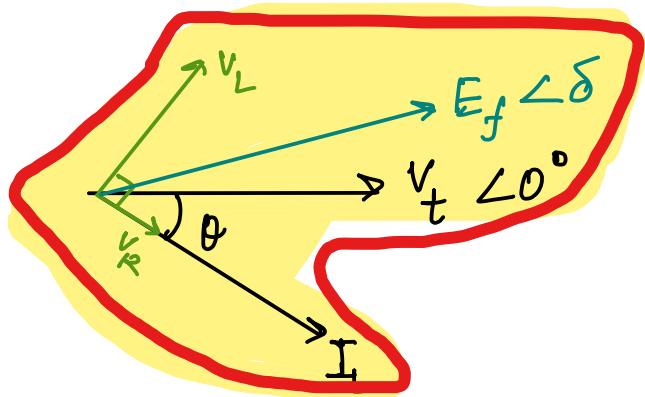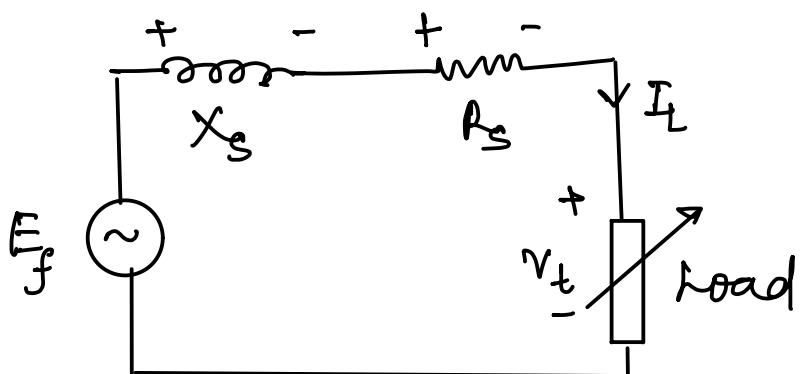

$$\vec{E}_f = \vec{V}_t + \vec{V}_R + \vec{V}_x$$

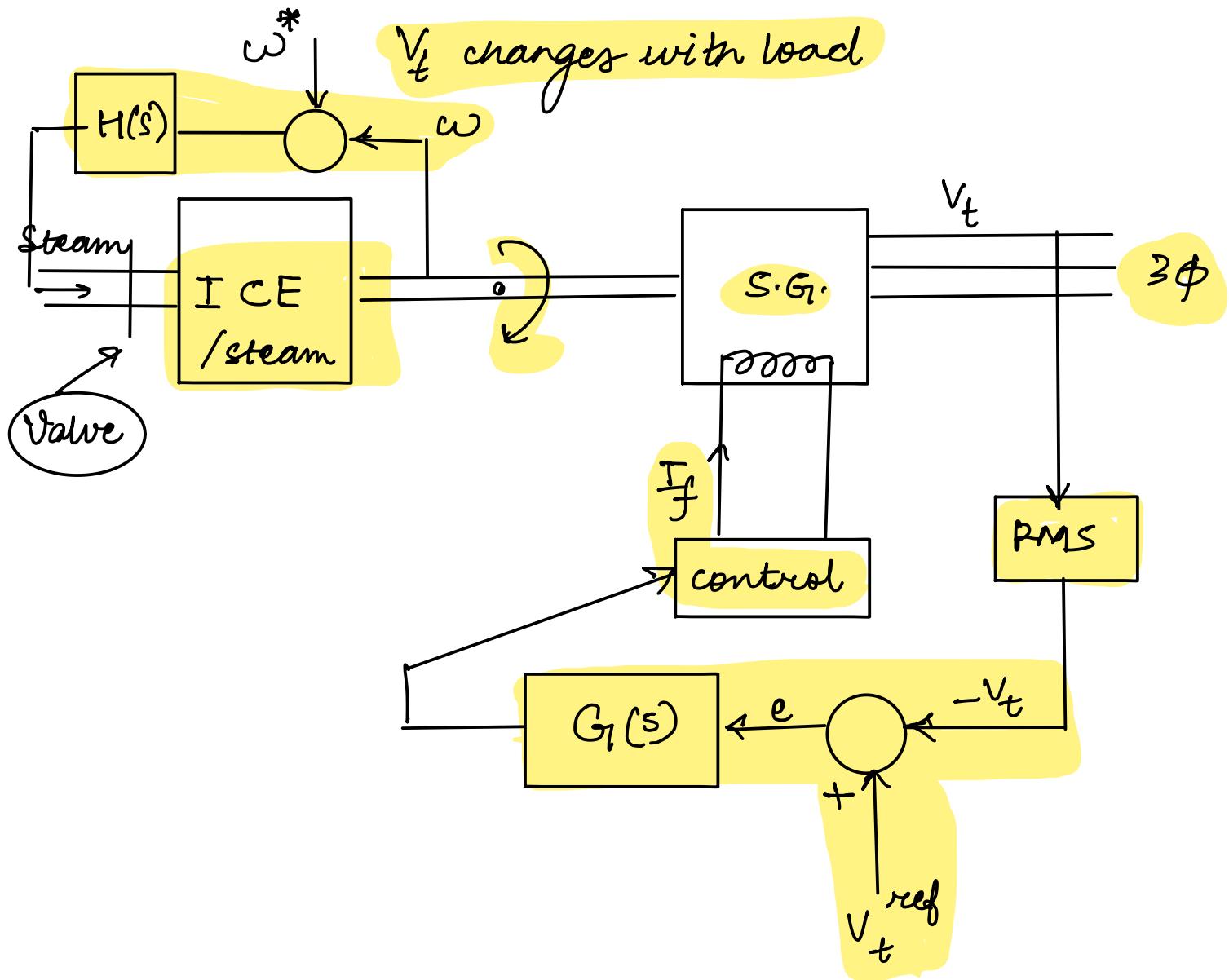
Assuming, rotation speed = constant
and current $I_f = \text{constant}$.




Objective
Fixed f
Fixed V


AVR
Automatic Voltage Regulator

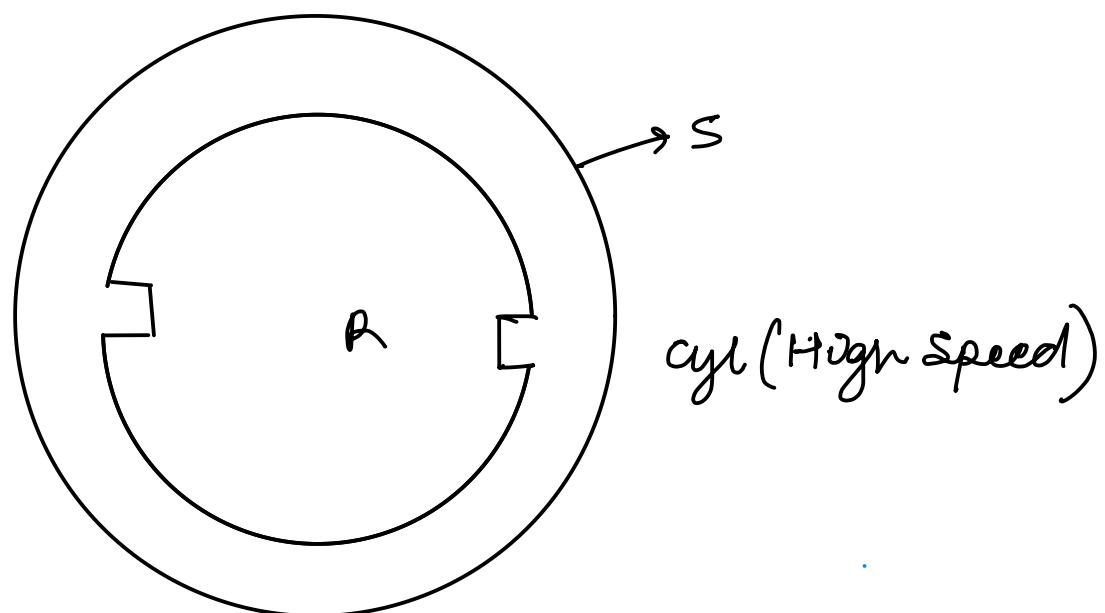★ We control If not valve (ω_s) because ω_s affects both f and V_t .



1 Generator - 1 Load

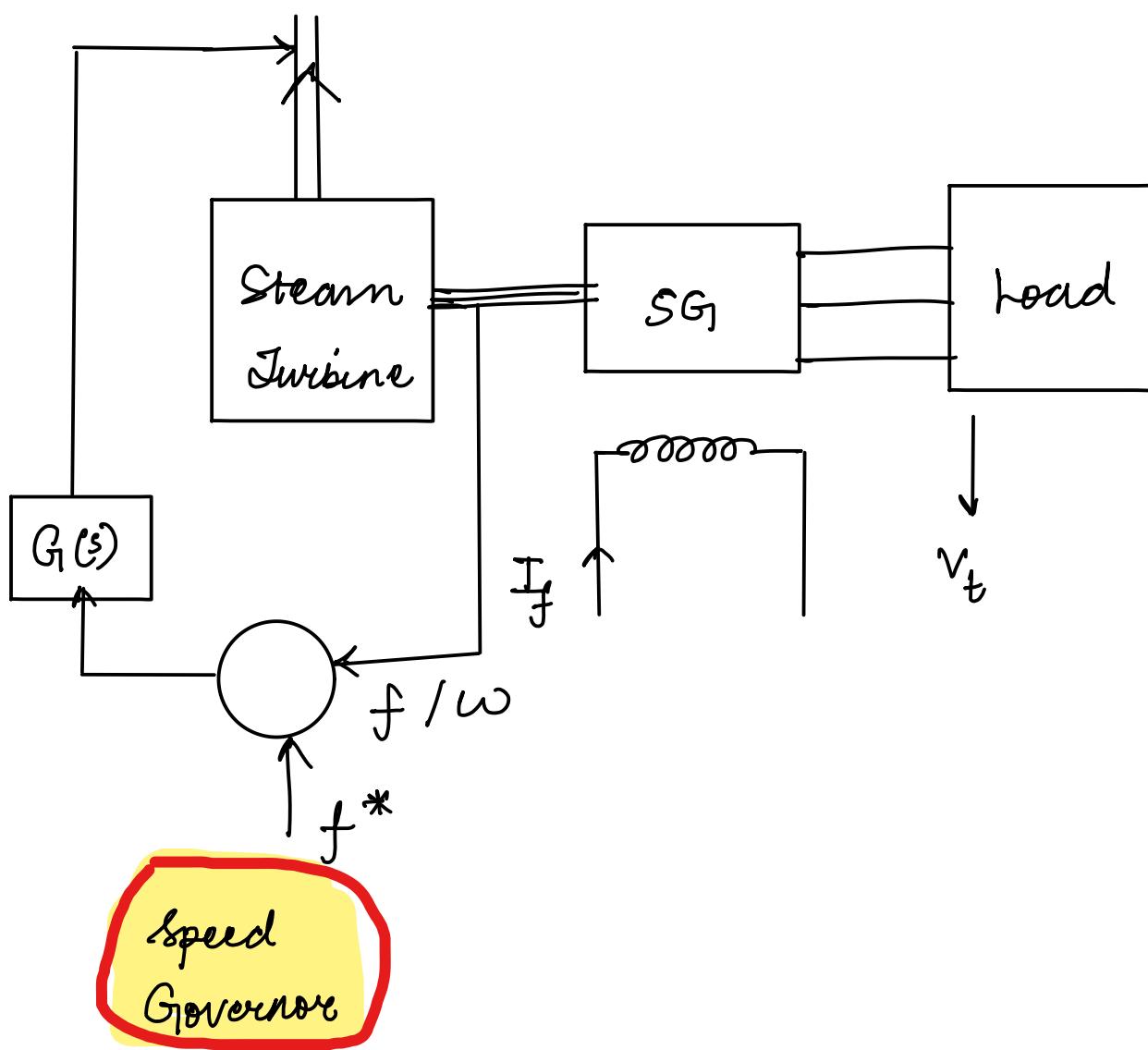

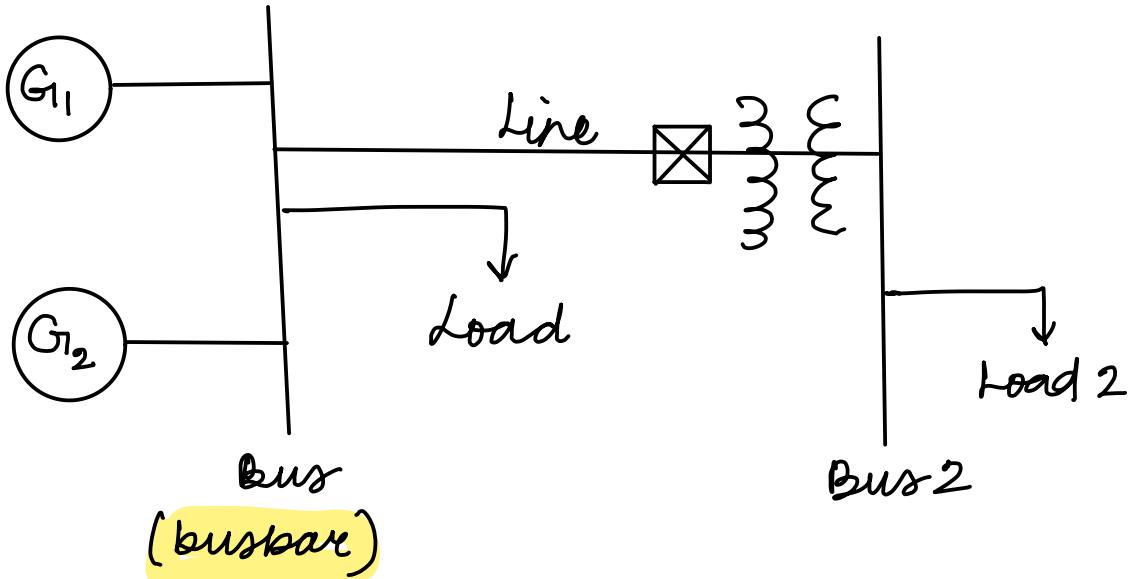


single line Diagram . (SLD)

Busbar \rightarrow no impedance

Line \rightarrow some finite impedance -

2 Generators Feeding 1 Load.

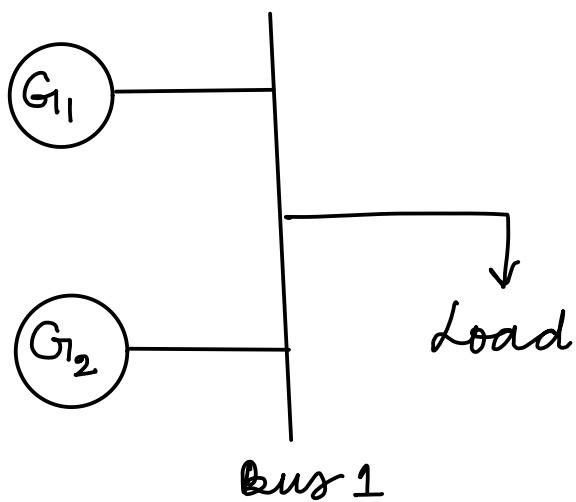


For equal work distribution in G_1, G_2 , we use only P instead of PI control.

"Droop Control"

$$P = P^* - m(f - f^*)$$

↑
Rated power.
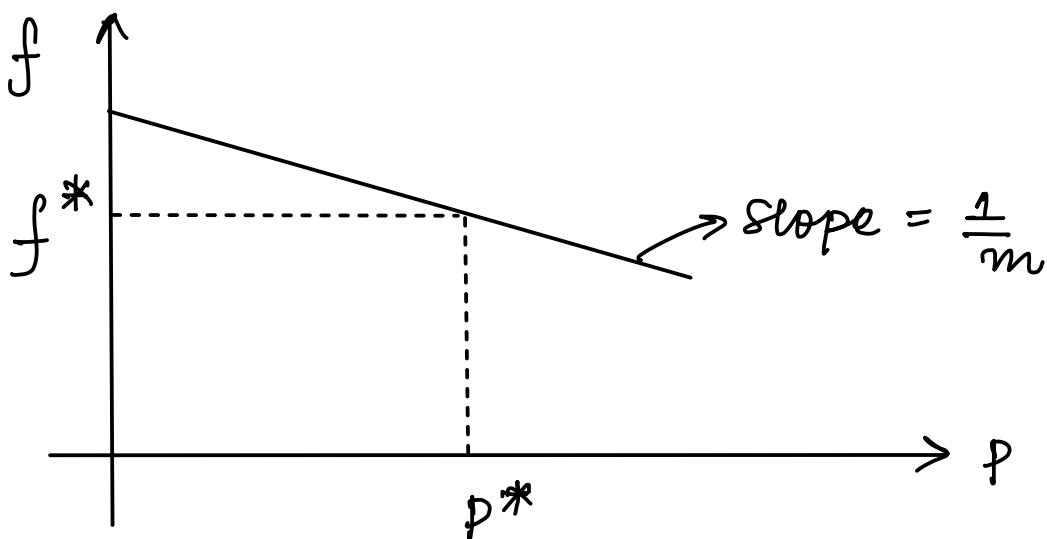
$$\rightarrow f \neq f^* \quad (f - f^* \rightarrow \text{small but not zero})$$



If m is large $\rightarrow f - f^* \rightarrow$ small

$$P_j = P_j^* - m_j(f_j - f^*)$$

$$\frac{P_j}{P_j^*} = 1 - \left(\frac{m_j}{P_j^*} \right) (f_j - f^*) \quad \text{--- } 1$$

$$\frac{P_2}{P_2^*} = 1 - \left(\frac{m_2}{P_2^*} \right) (f_2 - f^*) \quad \text{--- (2)}$$

$f^* = 50 \text{ Hz}$


$f_1 = f_2 = f$ (Because connected in a grid)

$$\text{If } \frac{m_1}{P_1^*} = \frac{m_2}{P_2^*} \Rightarrow \frac{P_1}{P_2} = \frac{P_1^*}{P_2^*}$$


Eg: 100 MW generator, 200 MW generator

If load is 30 MW \rightarrow 10, 20
 150 MW \rightarrow 50, 100.

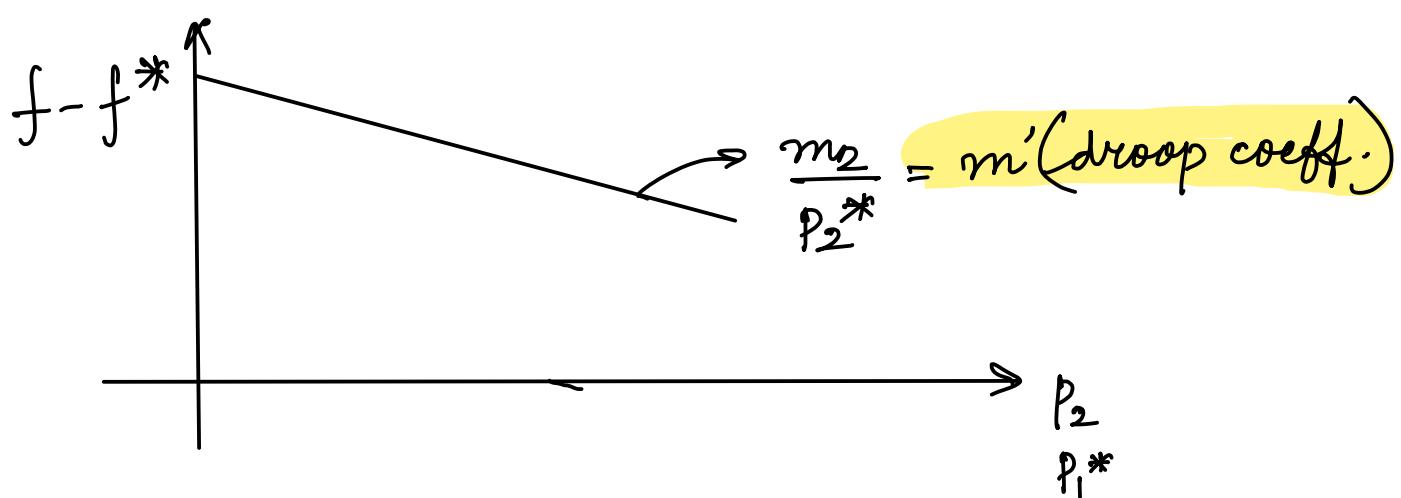
Eg: If G_1, G_2 are far away, we wouldn't want to divide power proportionally if there is heavy power loss in the line. Set m_1, m_2 accordingly.




Multiple Generators -

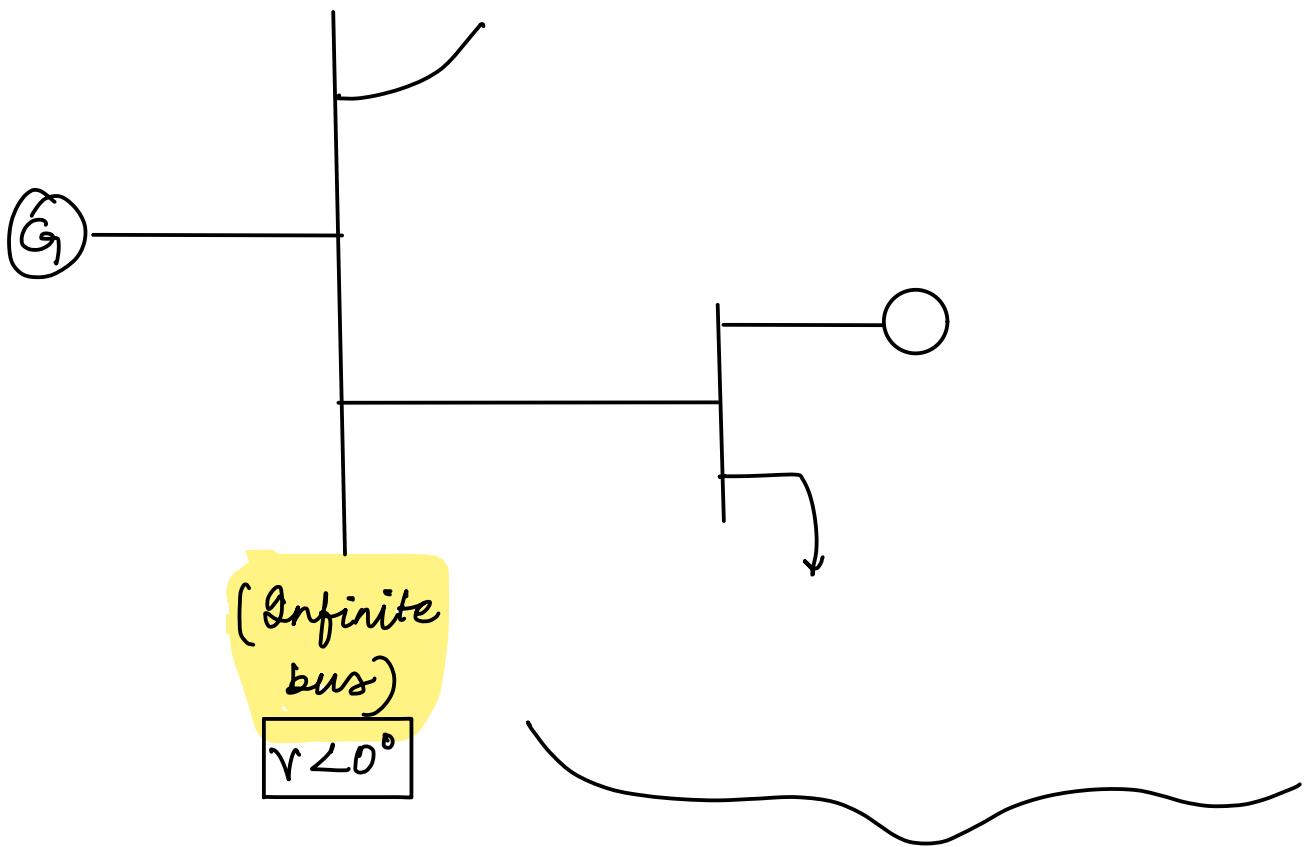

Complex network.

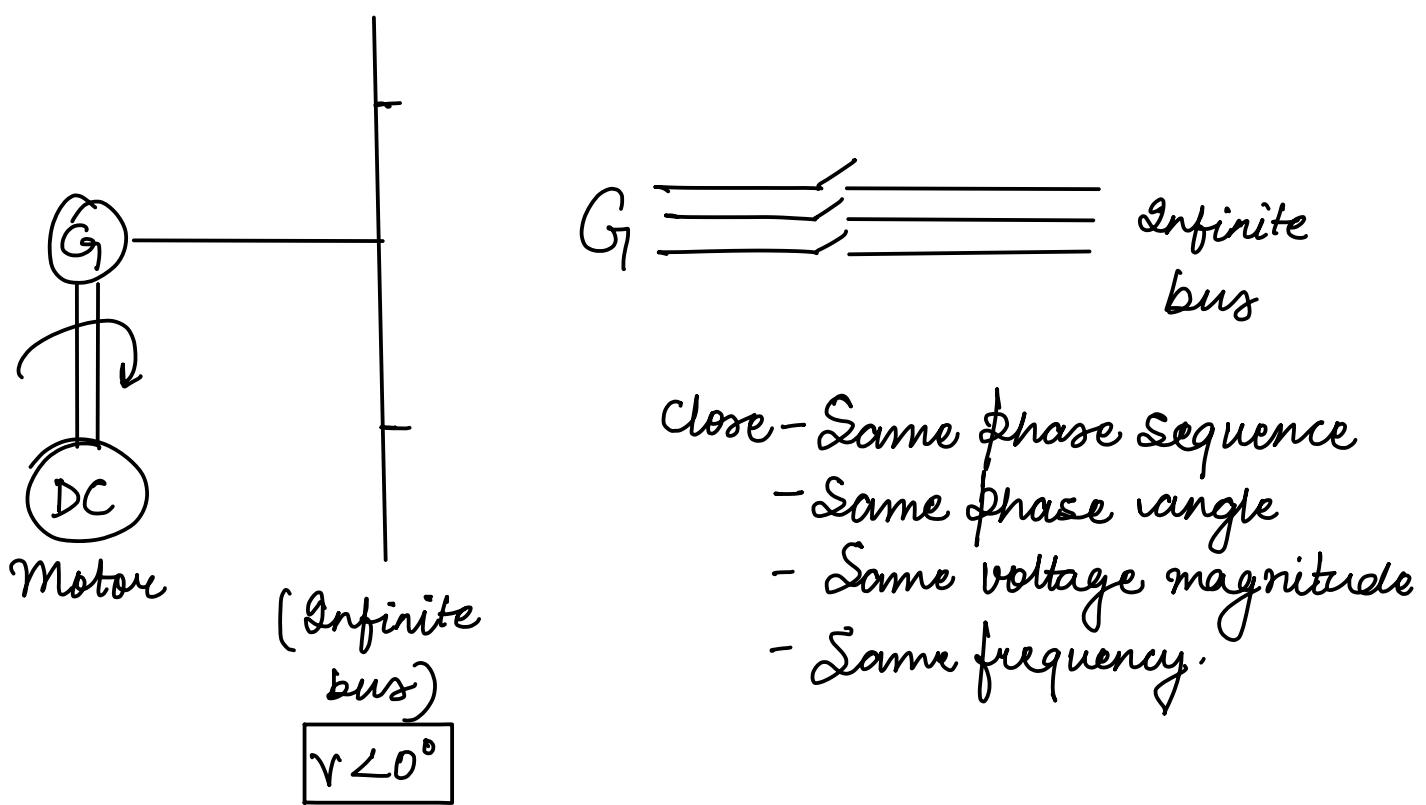

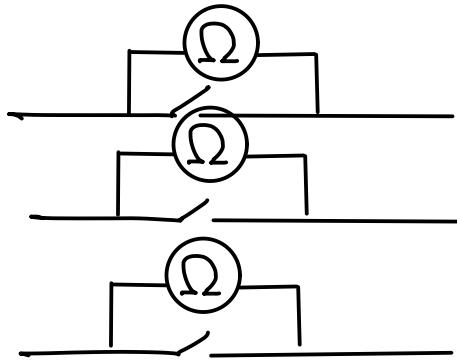

When all conditions are met \rightarrow bulbs become dark.


$$V_1^A = V_{m-1} \sin(\omega_1 t - \delta_1)$$

$$V_1^C = V_{m-1} \sin(\omega_1 t - \delta_2)$$

.



:
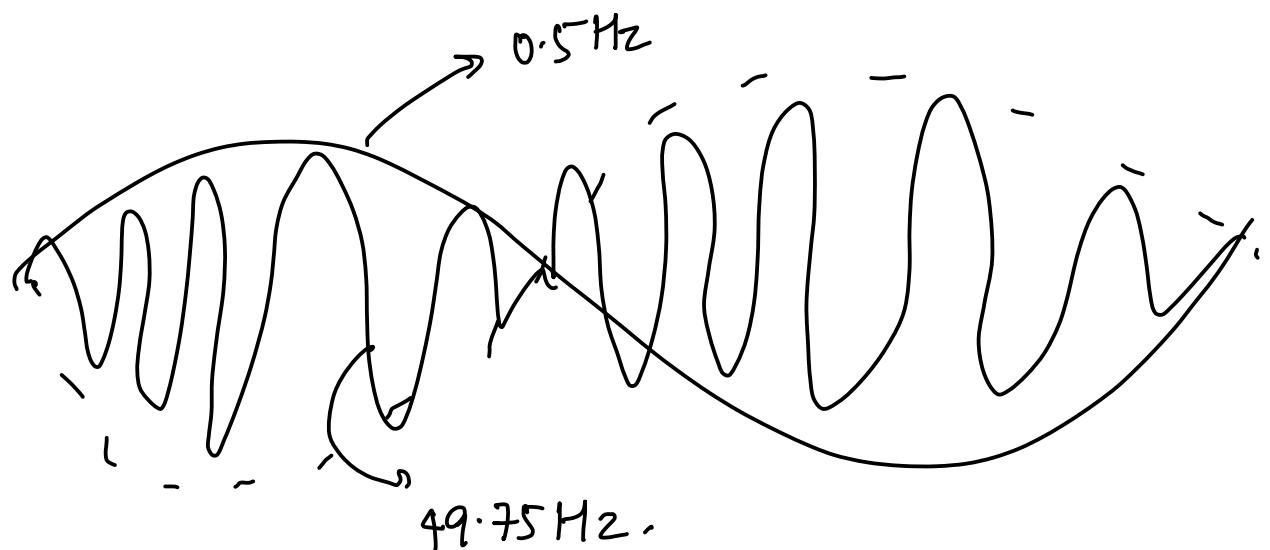
$$V_2^A = V_{m-2} \sin(\omega_2 t - \delta_2)$$



\Rightarrow Eyes cannot perceive 50Hz, it appears as if we are only seeing the 0.5Hz component.

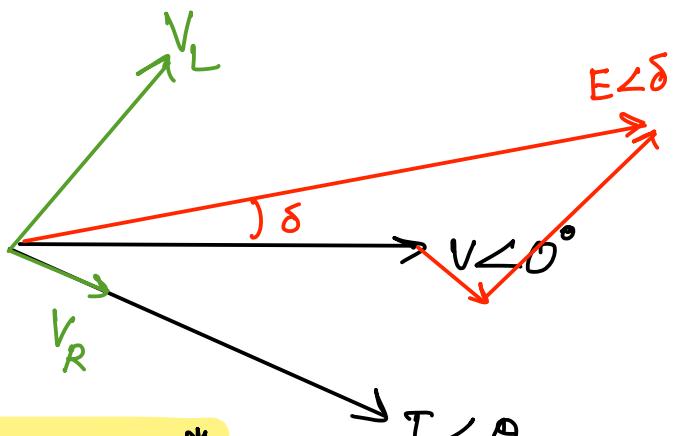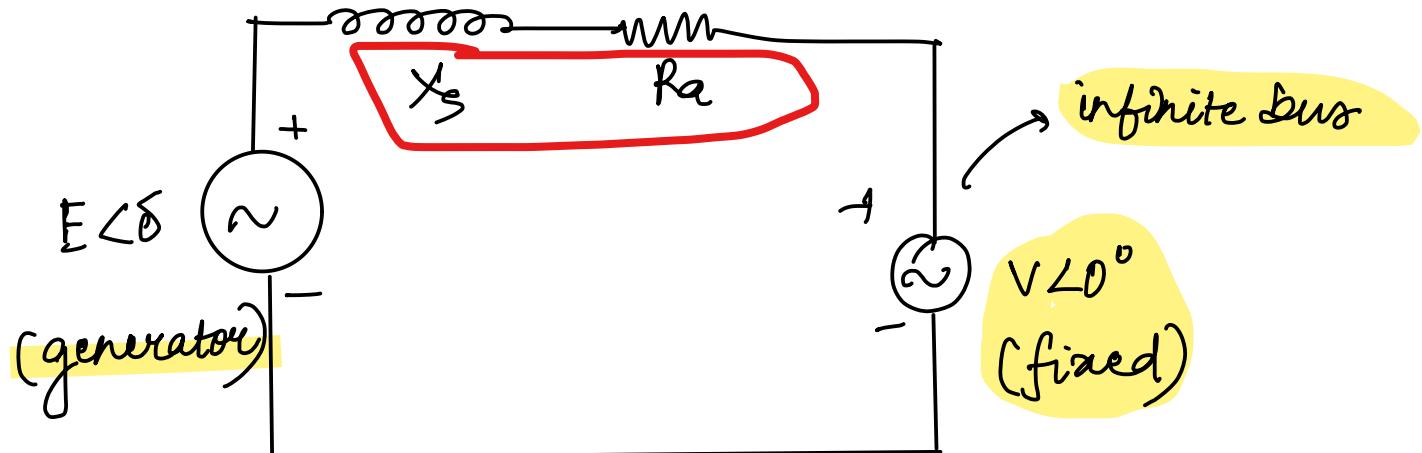Once generator is connected to infinite bus



$$S = 3 \times (V \angle 0^\circ) \times (I \angle \theta)^*$$

$$S_{1\phi} = V I^*$$

$$= V \angle 0^\circ \left(\frac{E \angle \delta - V \angle 0^\circ}{X_s \angle 90^\circ + R_a \angle 0^\circ} \right)^*$$

(Note: The denominator $X_s \angle 90^\circ + R_a \angle 0^\circ$ is circled with a red box and labeled "negligible".)

$$= V \left(\frac{E \cos \delta + E \sin \delta j - V}{X_s j} \right)^*$$

$$= \frac{V}{x_s} (E \sin \delta + V_j - E \cos \delta j)^*$$

$$P = \frac{V}{x_s} (E \sin \delta)$$

$$Q = \frac{V}{x_s} (E \cos \delta - V)$$

$$\left. \begin{array}{l} \\ \end{array} \right\} S = P + Qj$$

Per-unit

?

$$\chi_{pu} = \frac{\chi}{\chi_{base}} \times 100 \%$$

$$\chi = V, I, Z, P, Q, S$$

all use
 S_{base}

1-φ

P →

$$V_{base} = V_{nom}$$

V_{nom}, S_{rated}


$$I_{base} = \frac{S_{rated}}{V_{nom}}$$

N →

$$S_{base} = S_{rated}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{V_{base}^2}{S_{base}}$$
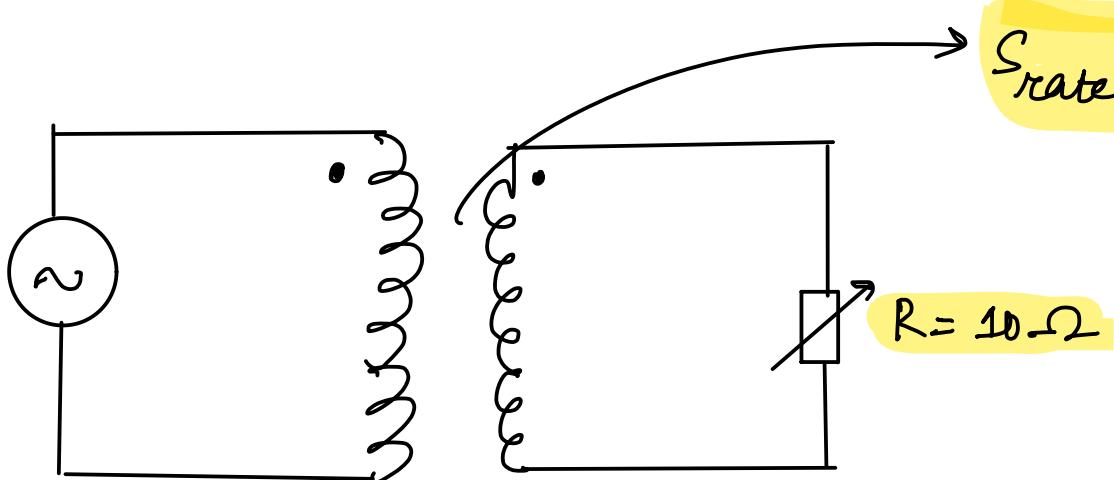
$$P_{pu} = \frac{5 \text{ kW (P)}}{10 \text{ kVA (S}_{\text{base}}\text{)}} = 0.5$$



$$\frac{11}{\sqrt{3}} \text{ kV : } 230$$

$$V_{\text{base}} = \frac{11}{\sqrt{3}} \text{ kV}$$

$$S_{\text{base}} = 50 \text{ kVA}$$


$$V_{\text{base}} = 230 \text{ V}$$

$$S_{\text{base}} = 50 \text{ kVA}$$

$$Z_{\text{base}} = \frac{V_{\text{base}}}{\left(\frac{S_{\text{rated}}}{V_{\text{nom}}} \right)} = \frac{V_{\text{nom}}^2}{S_{\text{rated}}} = 1.058 \Omega$$


$$Z_{pu} = \frac{10}{1.058} = 9.45$$

If we referred this to the primary side:

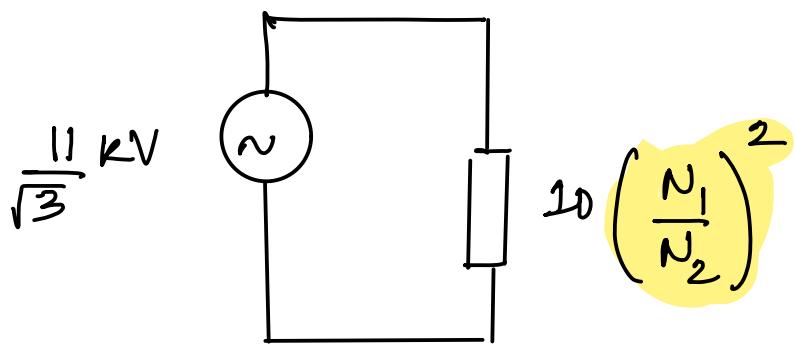


$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{\left(\frac{11}{\sqrt{3}}\right)^2 \times 10^6}{50 \times 10^3}$$

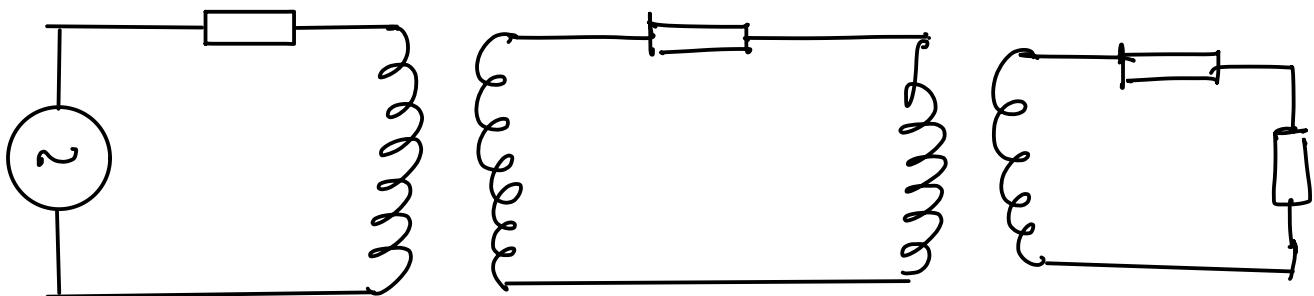? $Z_{pu} = \frac{10 \left(\frac{11}{\sqrt{3}}\right)^2 \left(\frac{1}{230}\right)^2 \times 50 \times 10^6}{\left(\frac{11}{\sqrt{3}}\right)^2 \times 10^3} = 9.45 \Omega$



$\Downarrow pu$

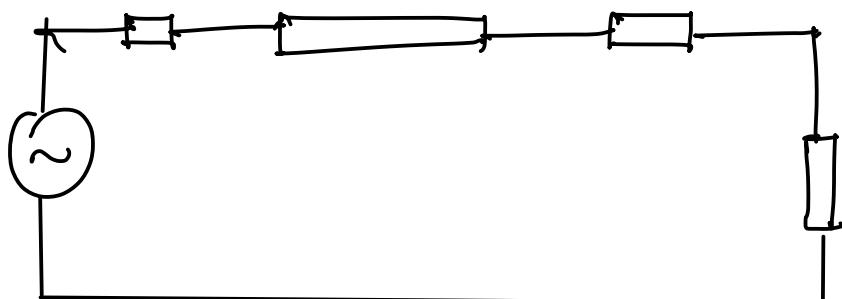

PV in 3φ

$$V_{base} = V_{l-l}^{nom}$$


$$I_{base} = I_l^{rated}$$

$$S_{base} = S^{rated}$$

$$S^{rated} = \sqrt{3} V_{l-l}^{nom} I_l^{rated}$$


$$Z_{base} = \frac{V_{l-l}^{nom^2}}{S^{rated}}$$

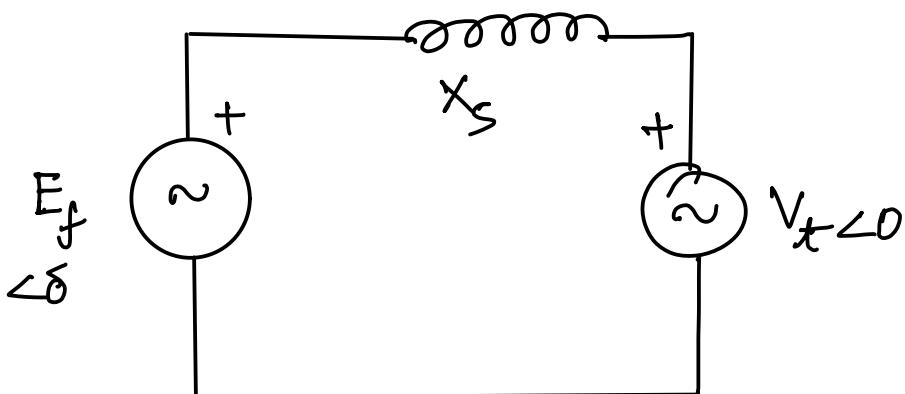
$$= \frac{V_{ph}^{rated}}{I_l^{rated}} = \frac{V_{l-l}^{rated}}{\sqrt{3} I_l^{rated}}$$



$$P = \frac{E_f V_t \sin \delta}{X_s}$$
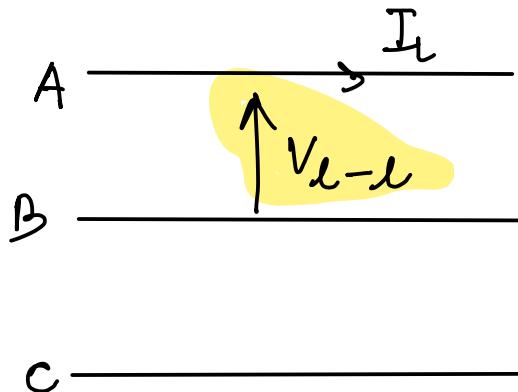
$$Q = \frac{V_t}{X_s} (E \cos \delta - V_t)$$



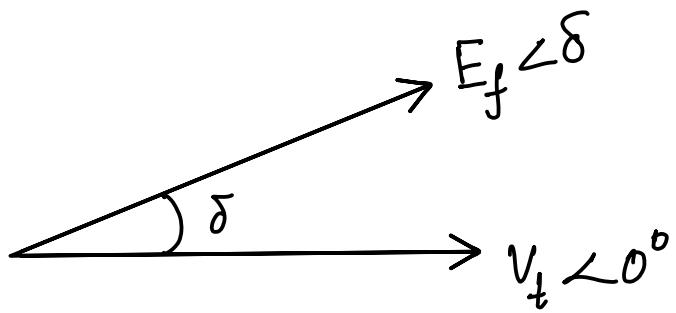

In SPWM, if we have ref $\rightarrow m \sin(\omega t + \delta)$


then we would have got $m V_{dc} \sin(\omega t + \delta)$


- \therefore changing V_{dc} \rightarrow changes E_f
- changing δ \rightarrow changes $\angle E_f$

δ : Power angle

Angle btw 2 voltages. Different from Power factor

Transmission Line

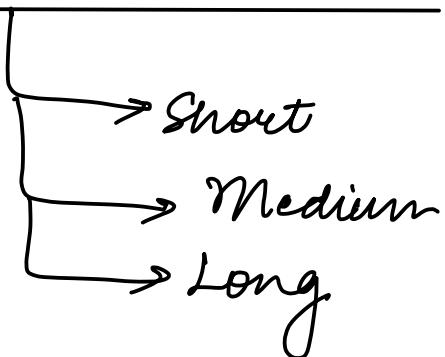

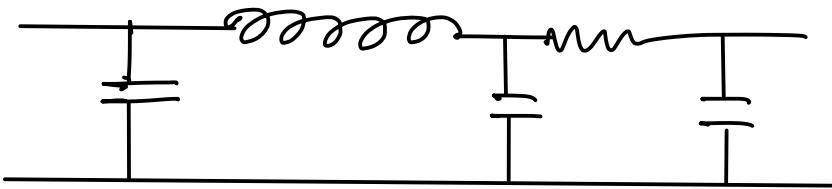


If short transmission line : forget capacitor .




L, R : lumped parameters .

Medium

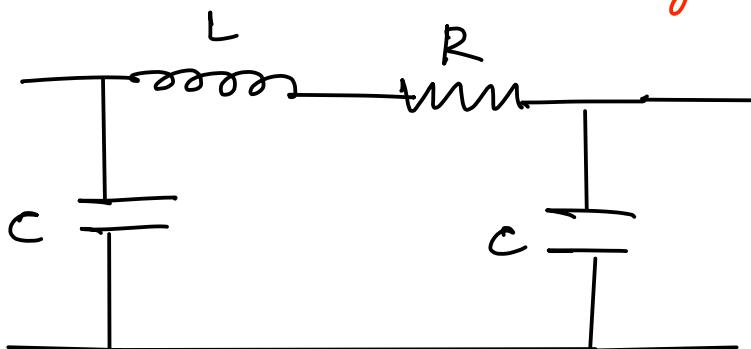($\frac{1}{j\omega C}$ in shunt can be ignored if c is small)



π -model

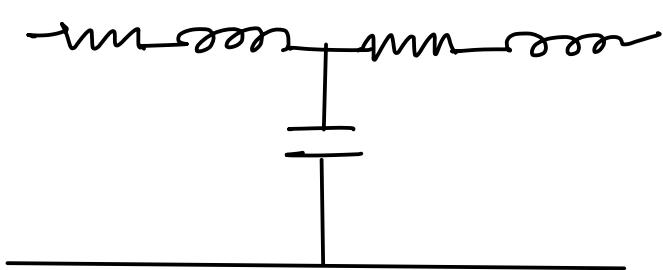

T-model



Long

series combo of π model and T-model

Cable \rightarrow Large C

Line \rightarrow \times

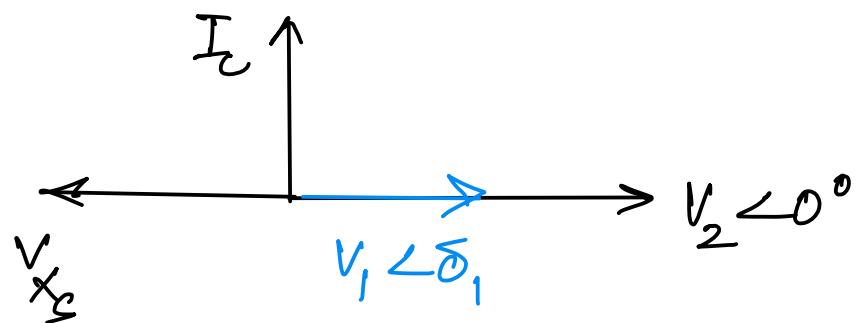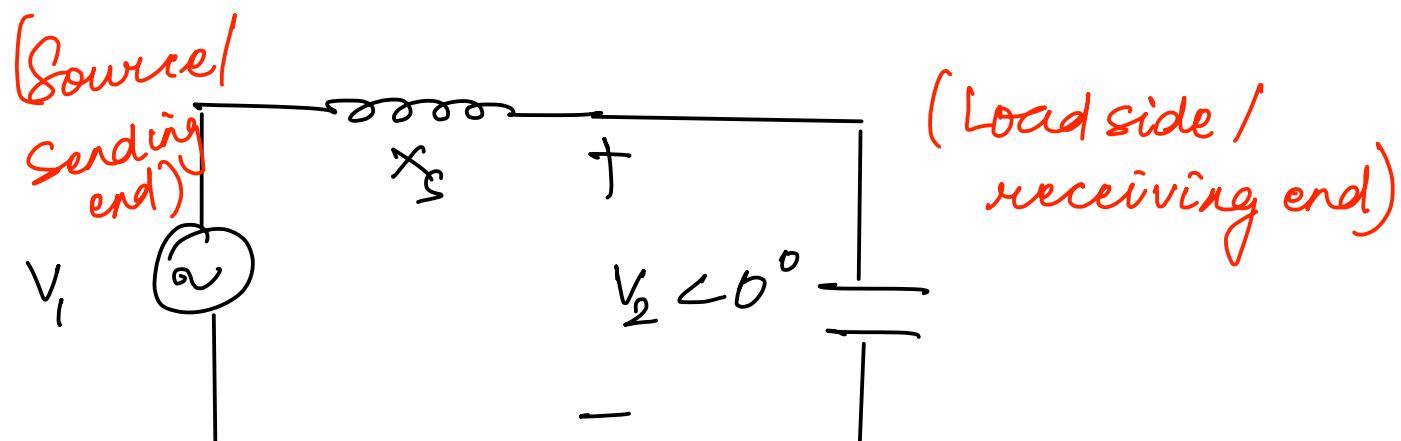Line is preferred over cables while transmitting over large distances .



Ferranti Effect: Load side has more voltage than source side.

HV AC transmission

↓
HV DC transmission (for very long distance transmission)